

Q1

4.4 Find the values of I and V in the circuits shown in Fig. E4.4.

Assuming the diodes are ideal.

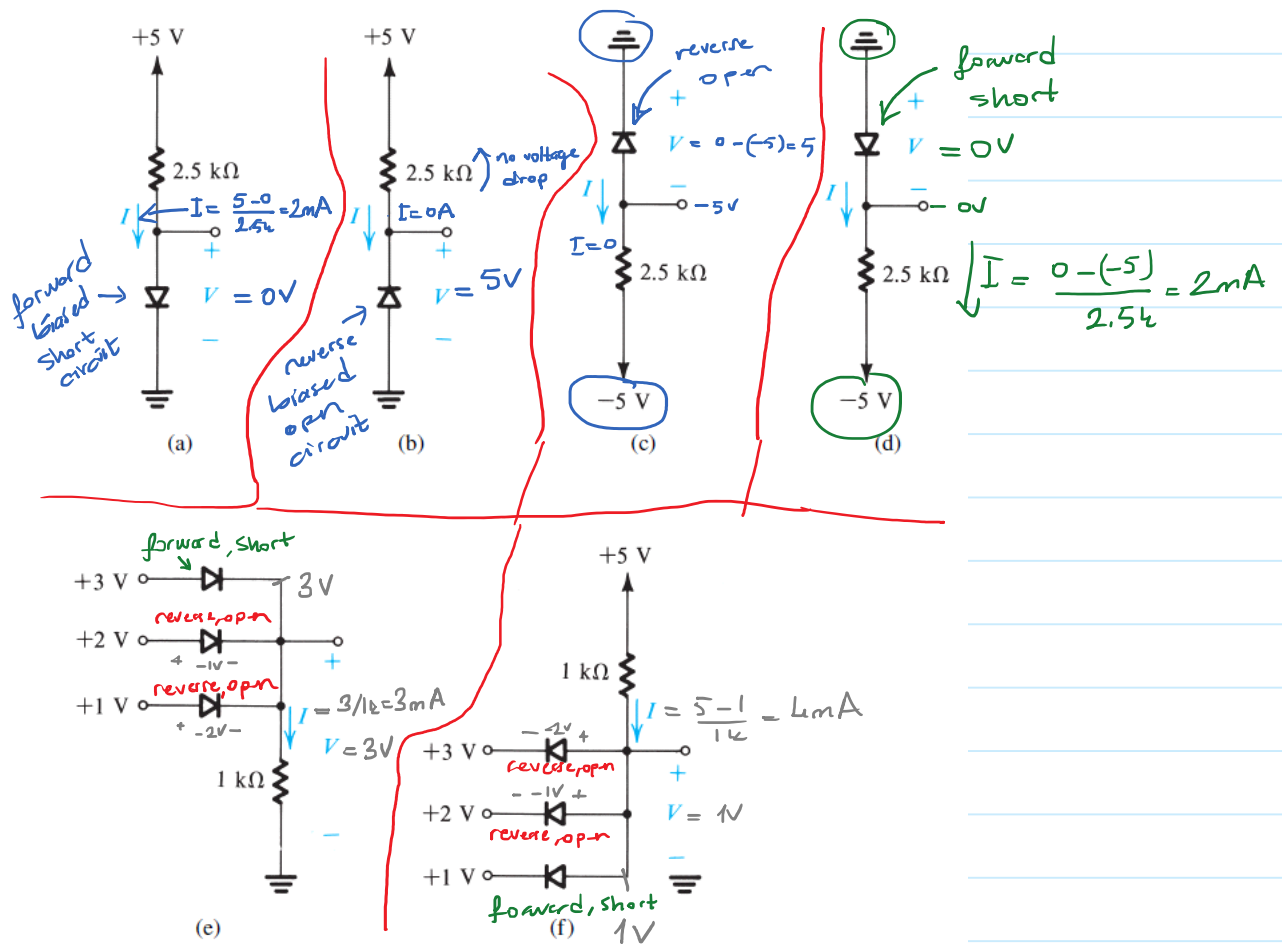


Figure E4.4

Q2


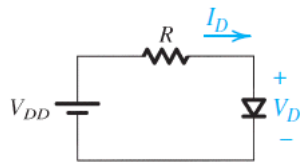
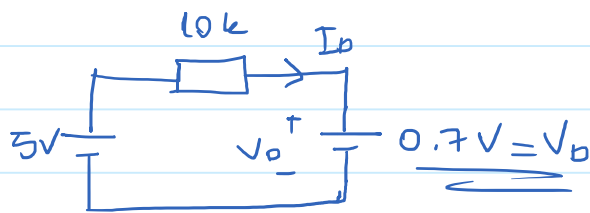


Figure 4.10

For the circuit in Fig. 4.10, find I_D and V_D for the case $V_{DD} = 5\text{ V}$ and $R = 10\text{ k}\Omega$. Assume that the diode has the constant-voltage-drop model with $V_D = 0.7\text{ V}$.

Ans. 0.43 mA , 0.7 V

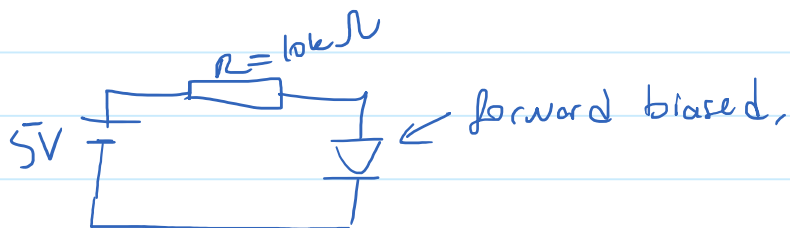

$$I_D = \frac{5 - 0.7}{10\text{ k}} = \underline{\underline{0.43\text{ mA}}}$$

Q3

Uncovered material, canceled!