 



Study Questions - 2

1



2 Refer to chapter 4 Slide 76.

4

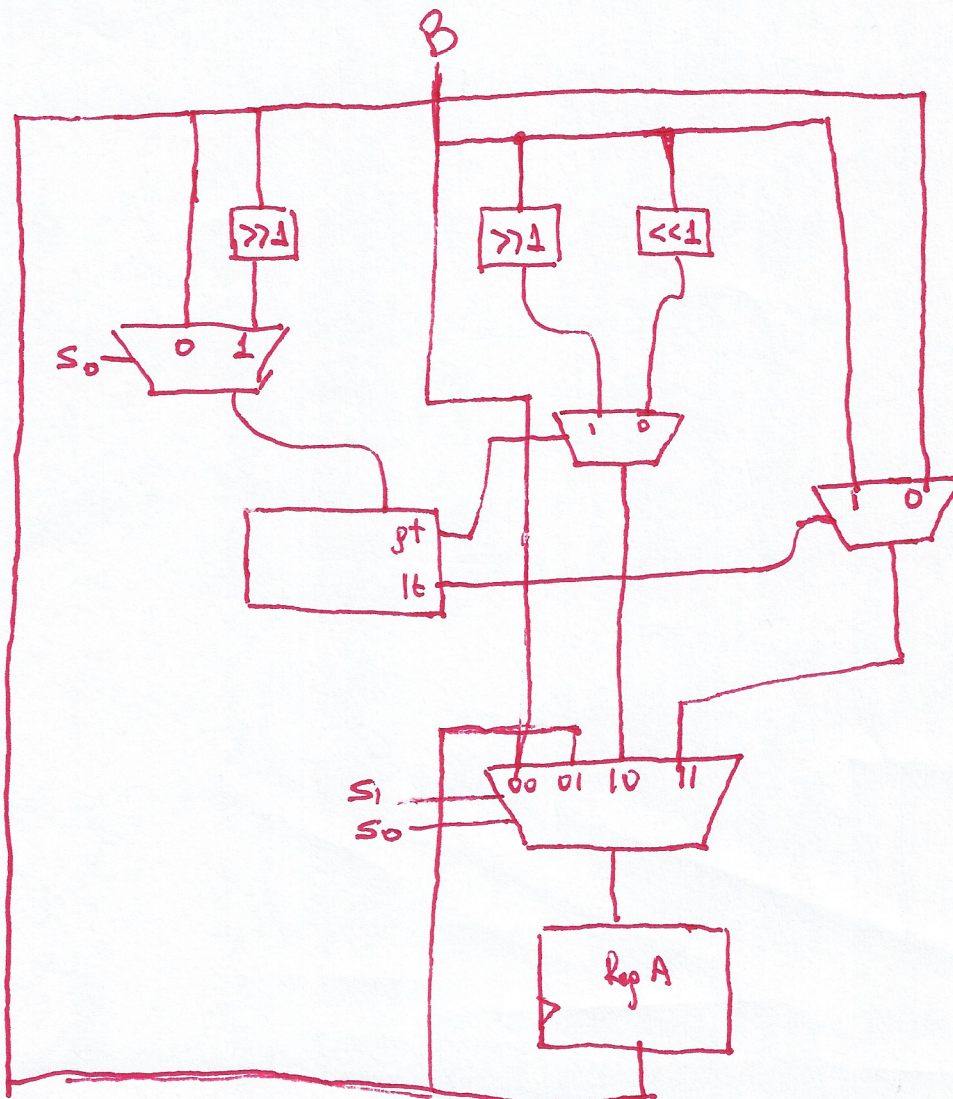


3)

Step 1 - Capture a high-level state machine


Inputs: CT, WT (32 bits); clr (bit)

Outputs: alarm (bit)

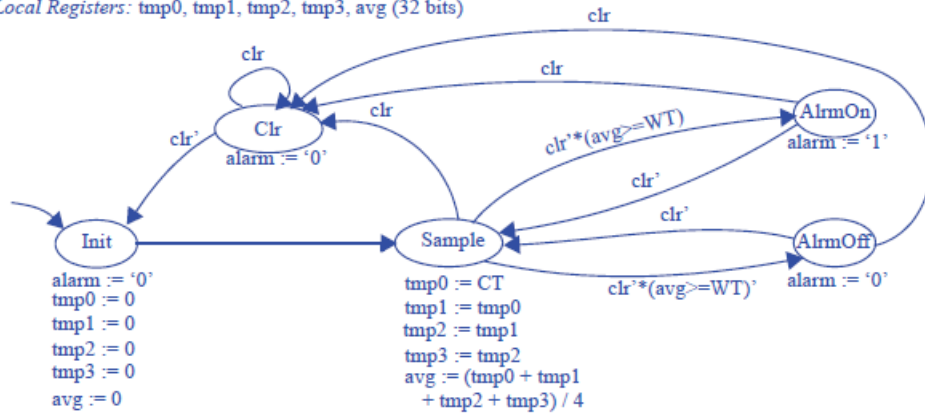Local Registers: tmp0, tmp1, tmp2, tmp3, avg (32 bits)




Step 2A - Create a datapath

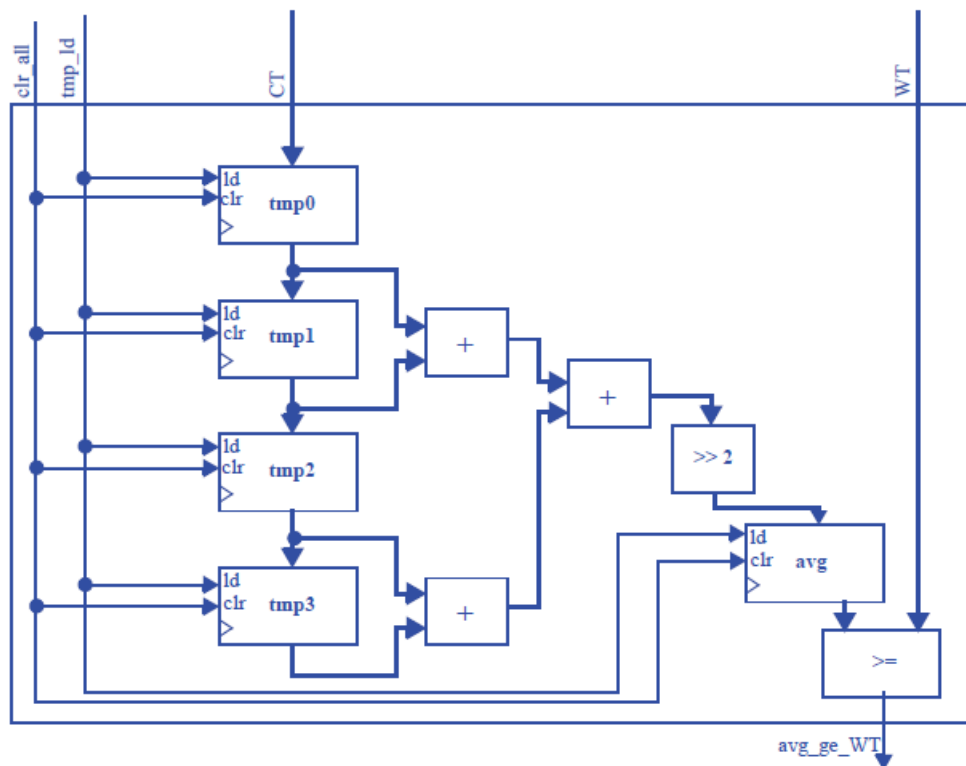

Note: A solution more consistent with the chapter's methodology would use a separate clear and ld signal for each register. In this particular example, a single clr and a single load line happens to work.

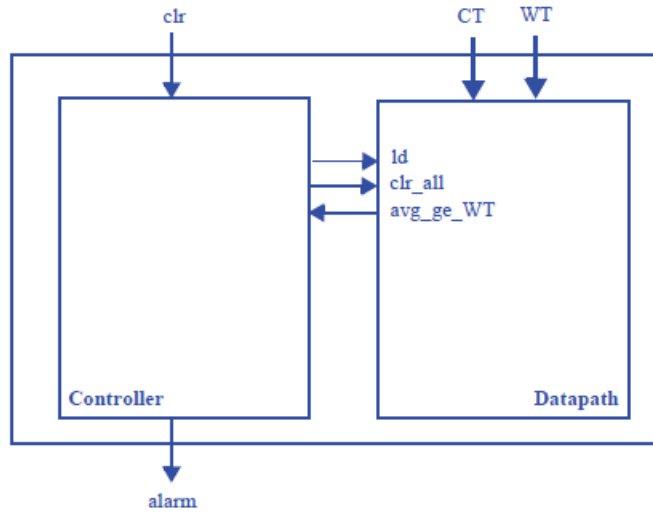Step 2B- Connect the datapath to a controller



Step 2C - Derive the controller's FSM

Inputs: clr, avg_lt_WT

Outputs: alarm, clr_all, ld

