
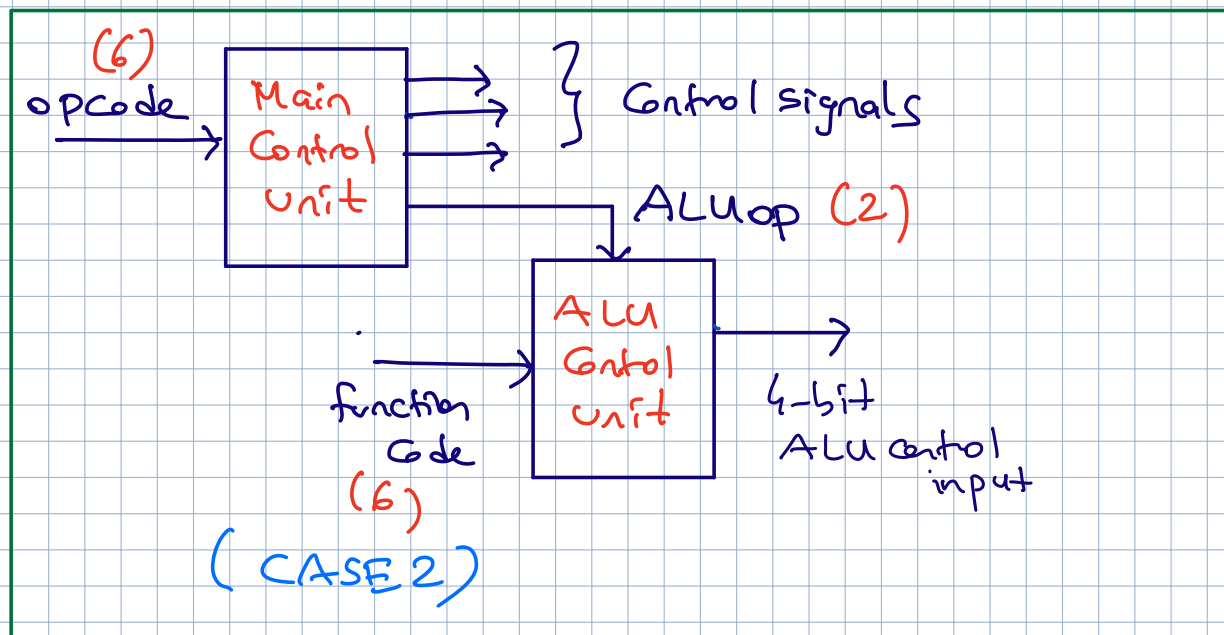

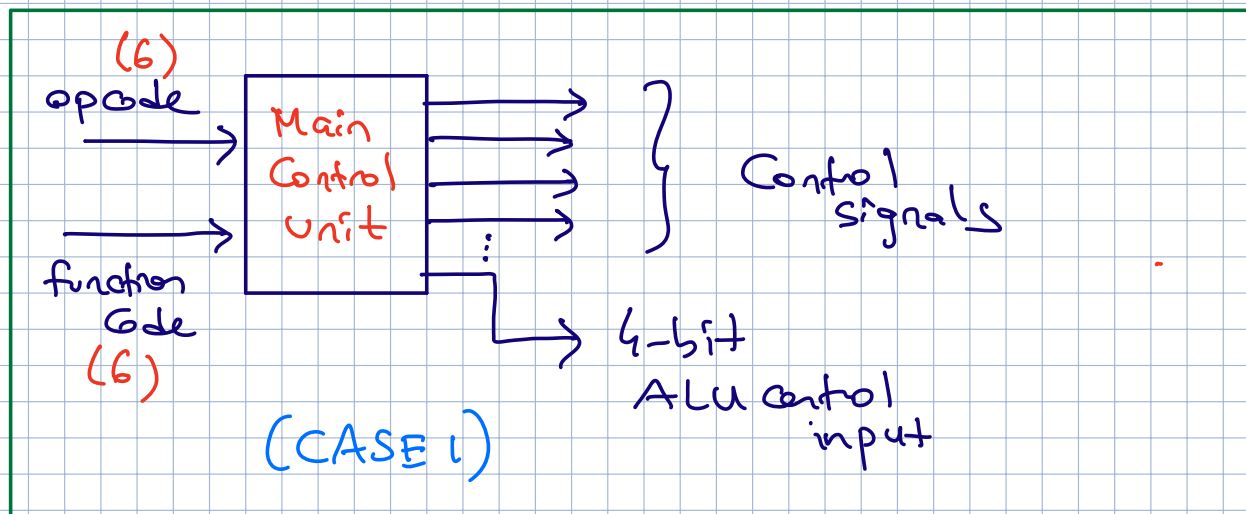
# The ALU Control

Depending on instruction class, ALU will need to perform

- for Lw/sw : Compute memory address calculation
- for R-type : add/sub/and/or/slt
- for branch : Subtraction



## Why multiple level of control?

- \* Reduce size of main control unit
- \* Using several smaller control units increase speed of the control unit

## Multiple Level of Control

4-bit ALU control input generated with a small unit that has inputs.

- { function field of the instr.
- { 2-bit control field (ALUop)

### ALUop

- { 00  $\rightarrow$  load/store (add)
- { 01  $\rightarrow$  branch (subtract)
- { 10  $\rightarrow$  R-type (determine operation encoded in function code)

### Figure 4.12

(How ALU control bits are set depend on ALUop bits and different function codes for R-type instr.)

function codes: add=32    sub=34  
                  and=36    or=37    slt=42

If ALUop=00 or 01  $\Rightarrow$  ALU action is not depend on function code (Do not care)


### Figure 4.13

(The truth table for the 4 ALU control bits)

Inputs: ALUop & function code fields.

ALU does not use "11" encoding  
(so truth table has 1X & X1 instead of 10 & 01)

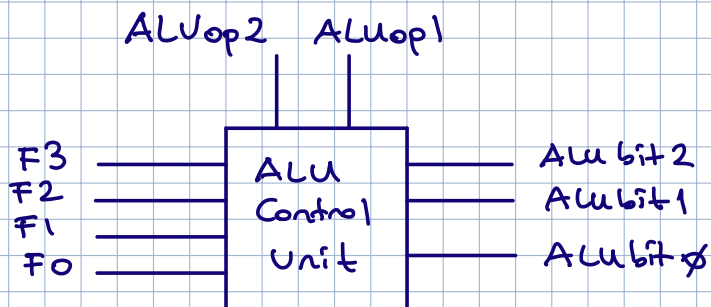
F5 & F4 are always 10  $\Rightarrow$  Don't care



### MAIN CONTROL UNIT (OBSERVATIONS)

- ① opcode is always in  $I[31:26]$
- ② Two registers to be read at positions  $I[25:21]$  &  $I[20:16]$   
(for R-type, Branch, store)
- ③ Base register for Lw/sw:  $I[25:21]$
- ④ 16-bit offset for branch equal, Lw & sw  $\rightarrow I[15:0]$

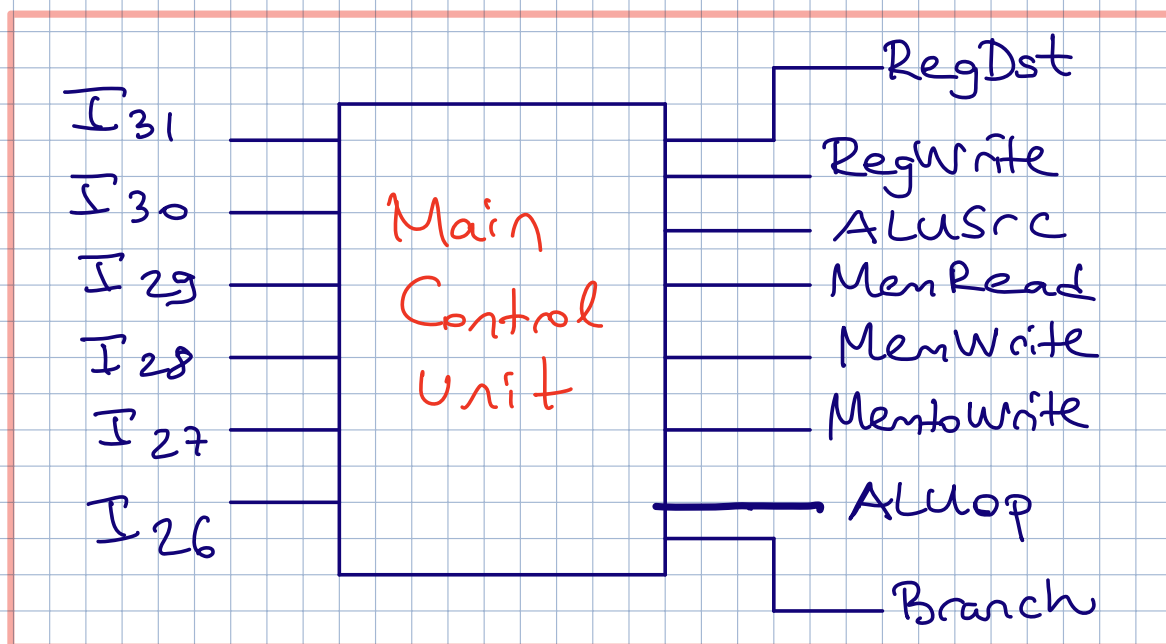- 5) Destination register in two fields.  
For LW  $\Rightarrow$   $I[20:16]$   
For R-type  $\Rightarrow$   $I[15:11]$   
(extra multiplexer required)




(7 control lines (1-bit) & 2-bit ALUop)

Main control unit set all control signals except PCSrc.

PCSrc is set if

 $\left\{ \begin{array}{l} * \text{ instr. is a branch} \\ * \text{ Branch taken is true} \end{array} \right.$  (zero output of ALU is true)




## Finalizing the Control

opcode  
↓

		Op5	Op4	Op3	Op2	Op1	Op0
0	R-format	0	0	0	0	0	0
35	LW	1	0	0	0	1	1
43	SW	1	0	1	0	1	1
4	BEQ	0	0	0	1	0	0

Input signals that correspond to four opcodes that determine the control output settings.

Instruction	RegDst	ALUSrc	Memto-Reg	Reg-Write	Mem-Read	Mem-Write	Branch	ALUOp1	ALUOp0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

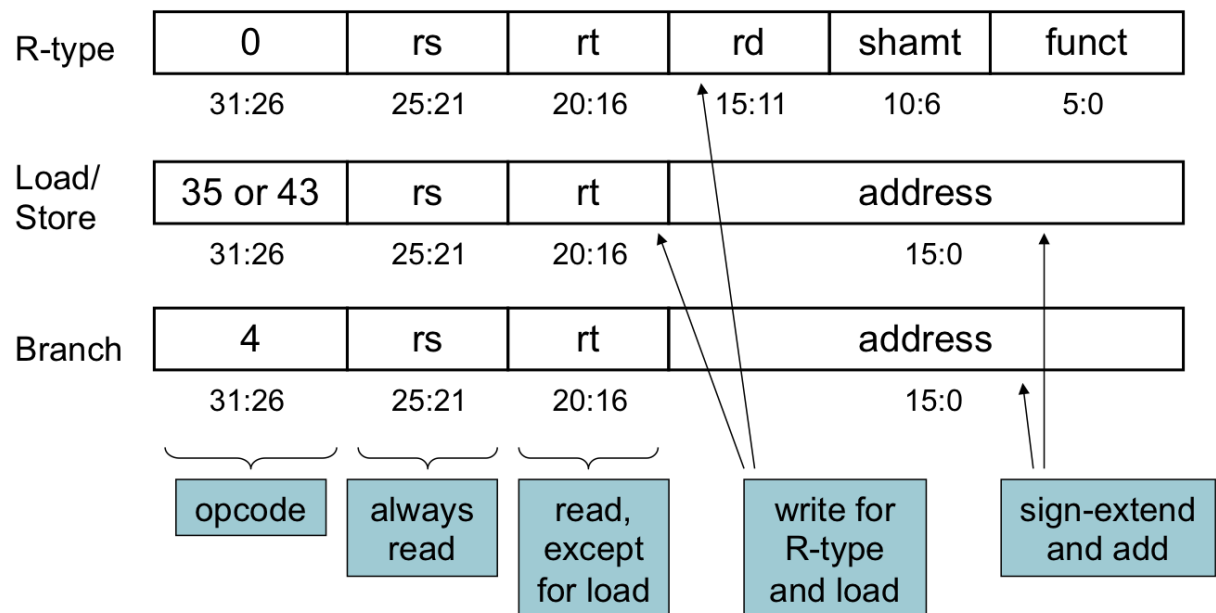

R-type

add \$t1, \$t2, \$t3

- ① Instr is fetched from instr. memory & PC is incremented
- ② \$t2 & \$t3 read from register file  
MCU computes settings of control lines
- ③ ALU operates on data read from register file using function code (I[5:0])
- ④ Result from ALU is written into register file using bits 15:11 of instruction (select \$t1)

Although everything is performed in 1 CC,  
we can think 4 steps to execute instr.

lw

lw \$t1, 2(\$t2)

- ① Instr is fetched from Instr. Memory & PC is incremented
- ② \$t2 value is read from register file
- ③ ALU performs the sum of value read from register file and sign-extended lower 16-bits of Instr.
- ④ ALU result is used as the addr for data memory
- ⑤ Data from memory is written into register file

beg

beg \$t1, \$t2, offset

- ① Instr fetched from memory and PC is incremented
  - ② \$t1, \$t2 read from register file
  - ③ ALU perform a subtract on data values read from register file
- } Branch Decision

(PC+4) added to sign-extended lower 16-bits of instr.

Shifted left by 2 bits

Branch Target Addr.

④ Zero output from ALU is used to decide which address result to store in PC