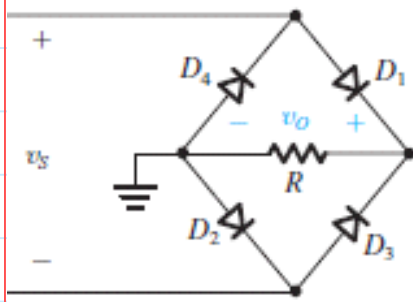



Q1



Draw the transfer characteristic of the given full-wave rectifier.






If $v_s > 2V_D \approx 1.4V$ then $v_o = v_s - 2V_D$

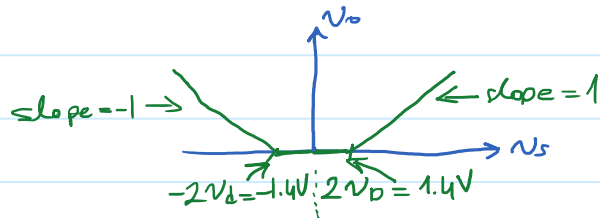If $v_s < -2V_D \approx -1.4V$ then $v_o = v_s + 2V_D$



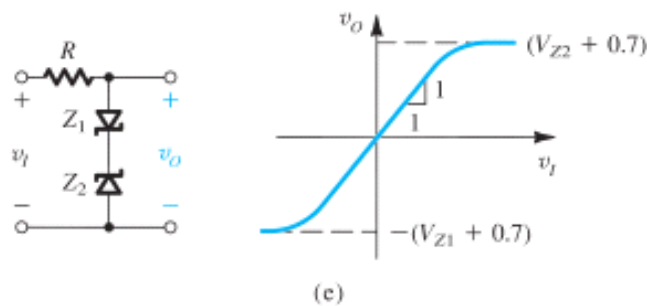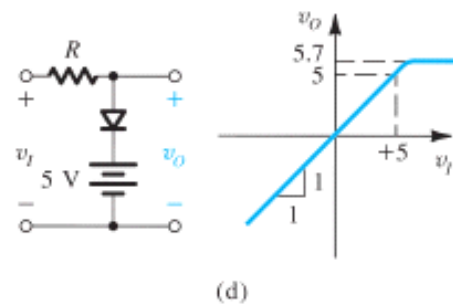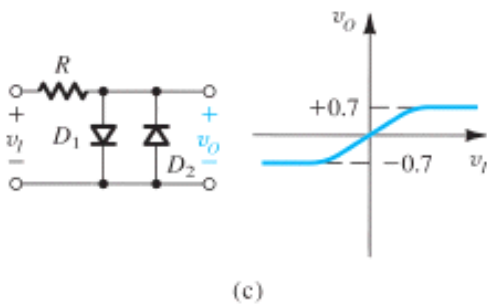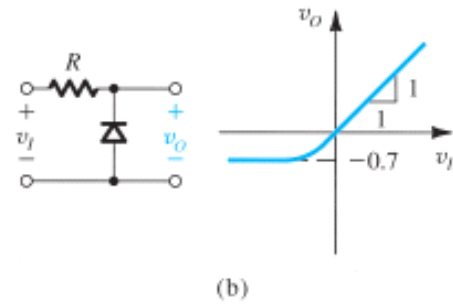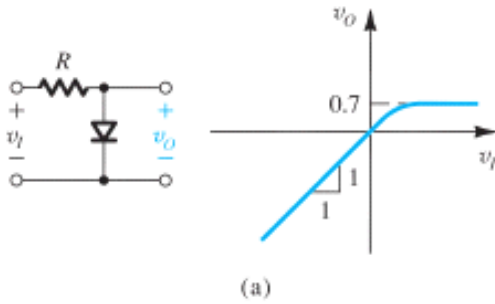Q2

For the given circuits draw the transfer characteristics.



4.90 Sketch and clearly label the transfer characteristic of the circuit in Fig. P4.90 for $-15\text{ V} \leq v_I \leq +15\text{ V}$. Assume that


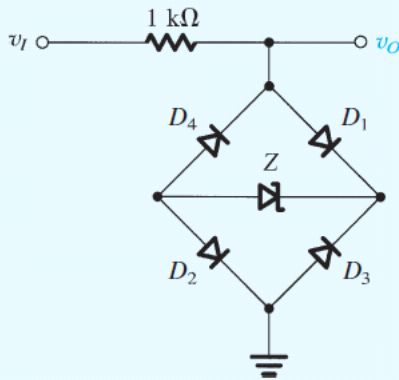


Figure P4.90



Assuming a voltage drop of v_D when the diodes are forward biased.

The zener potential is V_Z .


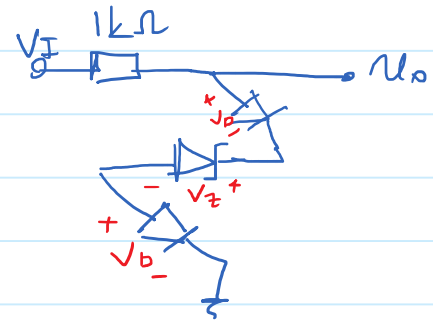
If $v_I > 2v_D + V_Z$
then $v_O = 2v_D + V_Z$



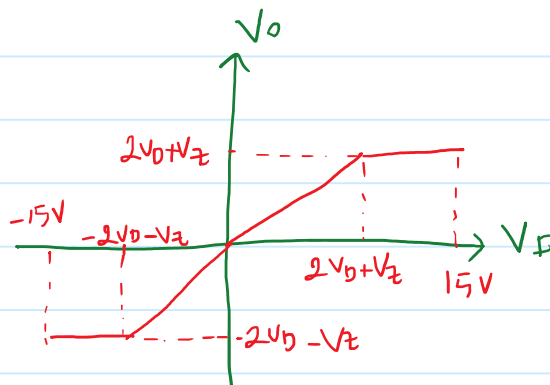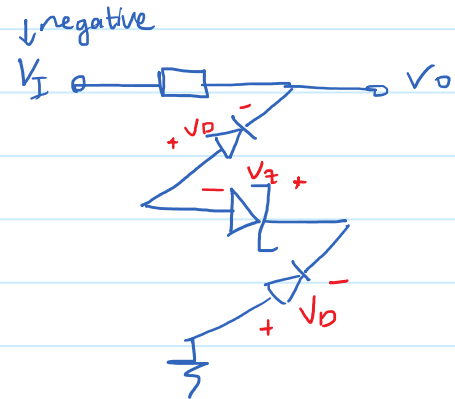If $v_I < -(2v_D + V_Z)$
then $v_O = -2v_D - V_Z$



Q4

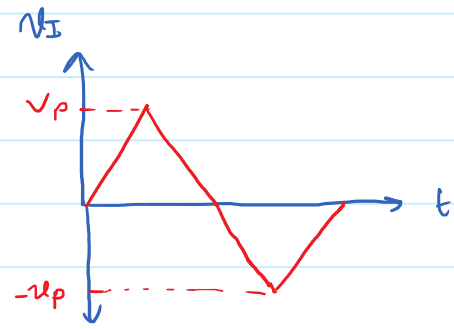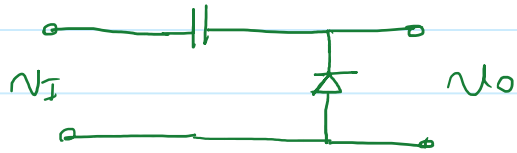

Plot t vs v_o . (Assume the diode is ideal.)

