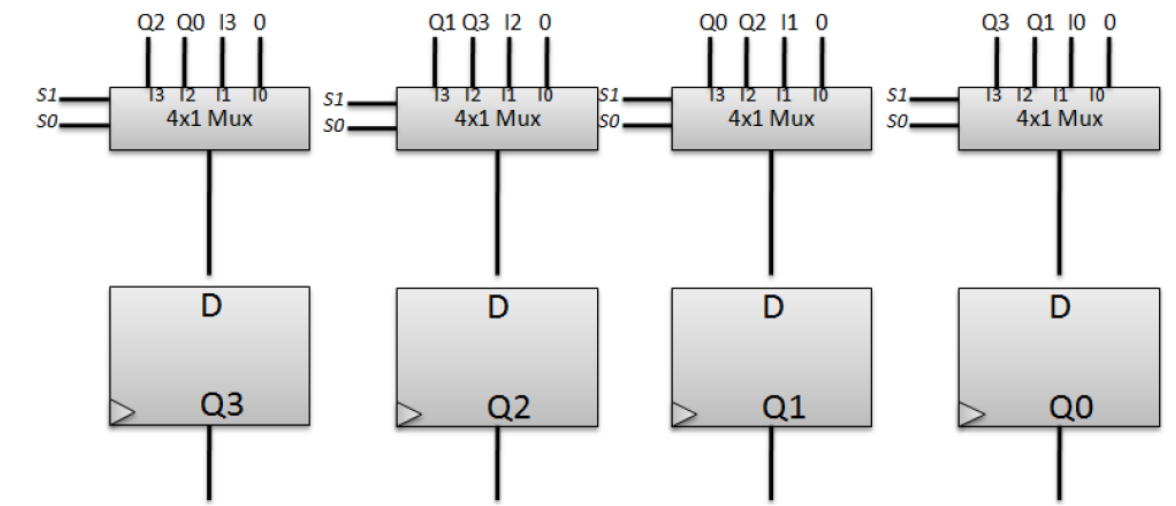


Study Questions II

Q5)

Design a 4-bit register with 2 control inputs s_1 and s_0 , 4 data inputs $I_3..I_0$, and 4 data outputs $Q_3..Q_0$. The function table below shows the configurations for the register. In this question you have to design the circuit inside the “Black Box”.

S_1	S_0	Action
0	0	Clear the contents of the register
0	1	Load I
1	0	Rotate right by one bit
1	1	Rotate left by one bit



Q6) Using **only a 4-bit up** binary counter, you are going to design a circuit that detects odd numbers in a sequence of numbers, its output (denoted by **ODD**) is 1 when the sequence value is an odd number, 0 otherwise. The sequence is defined below in Q3a. You can use any of the following components (**Specify the bit widths, and name all inputs/outputs**):

- 1) Adders
- 2) Shifters
- 3) Comparators
- 4) Multiplexers
- 5) Subtractors

Make sure you answer both parts 6a, and 6b.

6a. Using the 4-bit up binary counter, create a circuit that generates the following sequence:

48 -> 45 -> 42 -> 39 -> 36 -> 33 -> 30 -> 27 -> 24 -> 21 -> 18 -> 15 -> 12 -> 9 -> 6 -> 3 -> 48 -> 45 -> 42

6b. Using the circuit designed in part 6a, modify it so that whenever an odd number is encountered in the sequence generated, your circuit outputs a 1 (ODD signal is 1), otherwise, it outputs a 0.

