
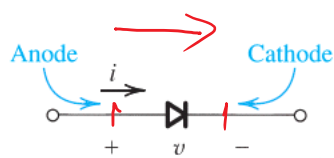


# Reading


Adel S. Sedra and Kenneth C. Smith, **Microelectronic Circuits** 7<sup>th</sup> Edition, *Oxford University Press*, 2014.

- Chapter 4.1, 4.3, 4.4


# Recap-1

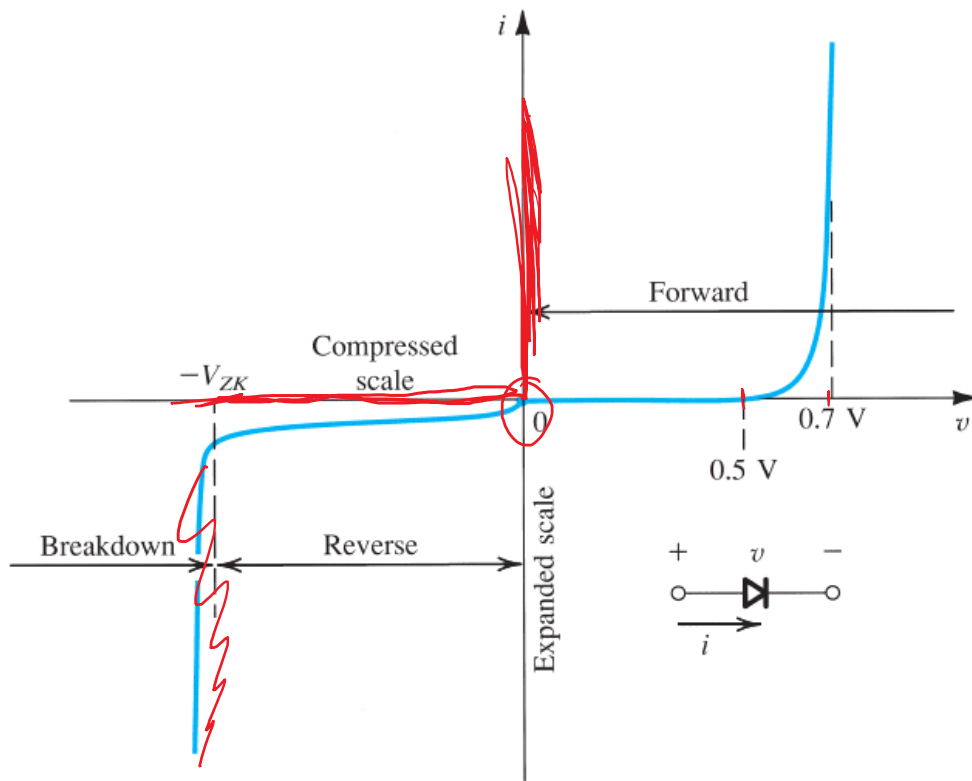

(a)

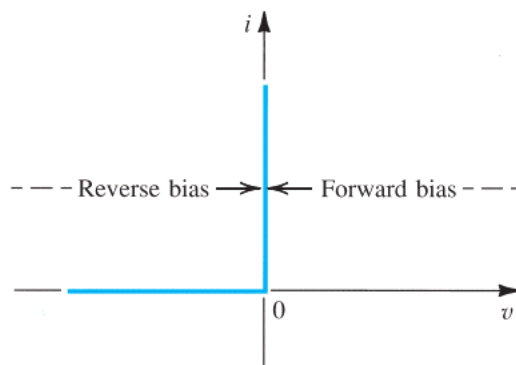


(b)

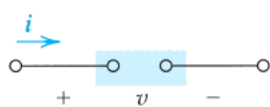

$$v < 0 \Rightarrow i = 0$$

(c)







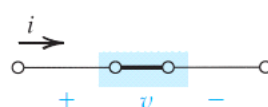


$$i > 0 \Rightarrow v = 0$$





(d)

**Figure 4.1** The ideal diode: (a) diode circuit symbol; (b)  $i-v$  characteristic; (c) equivalent circuit in the reverse direction; (d) equivalent circuit in the forward direction.







## Recap-2

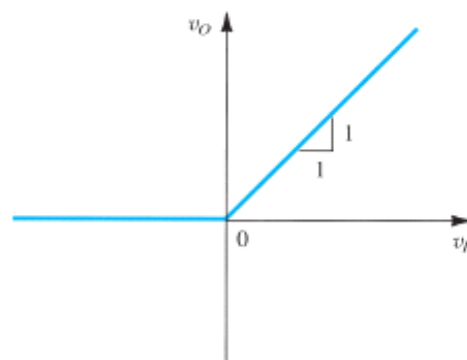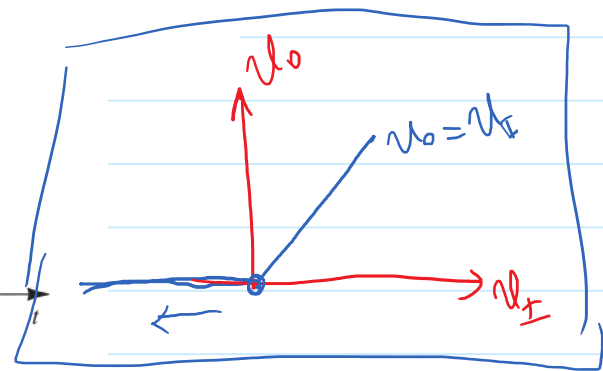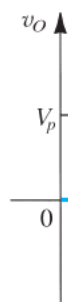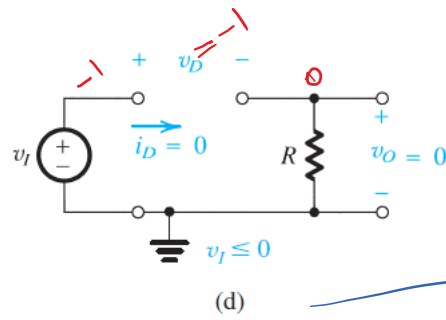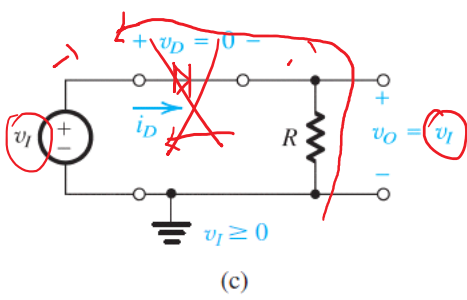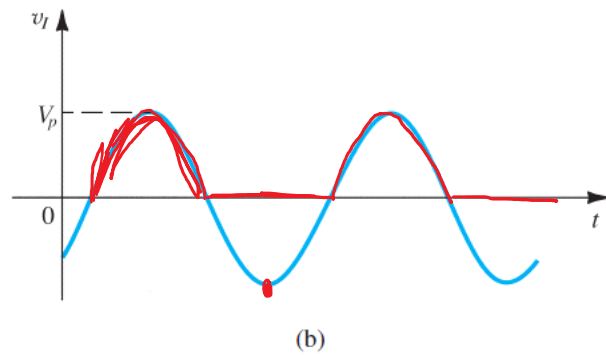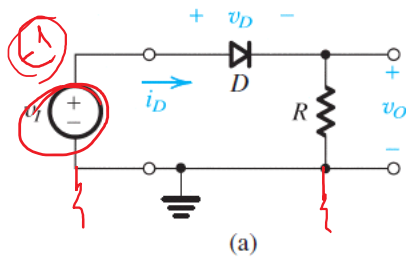

# Constant Voltage Drop Model

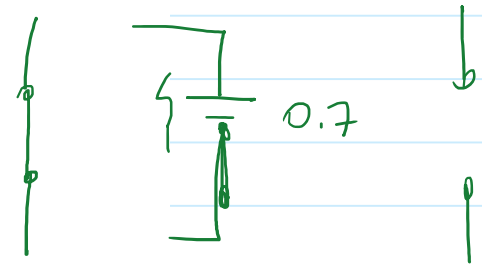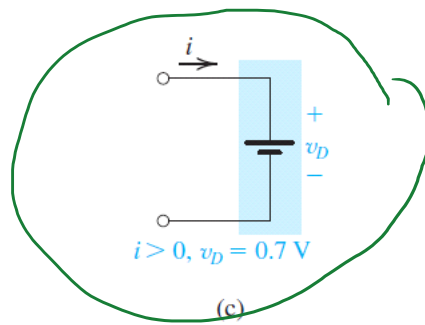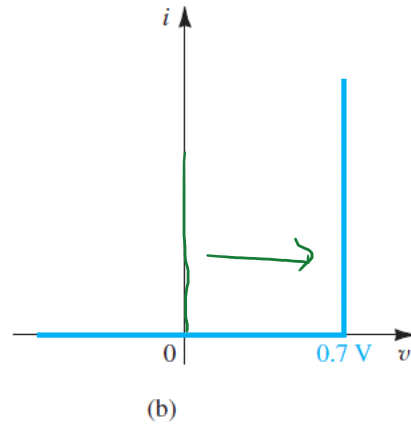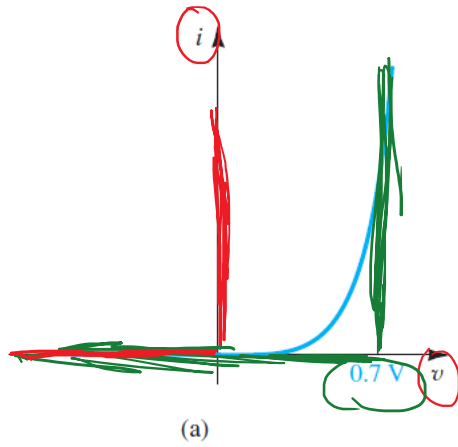

# Example

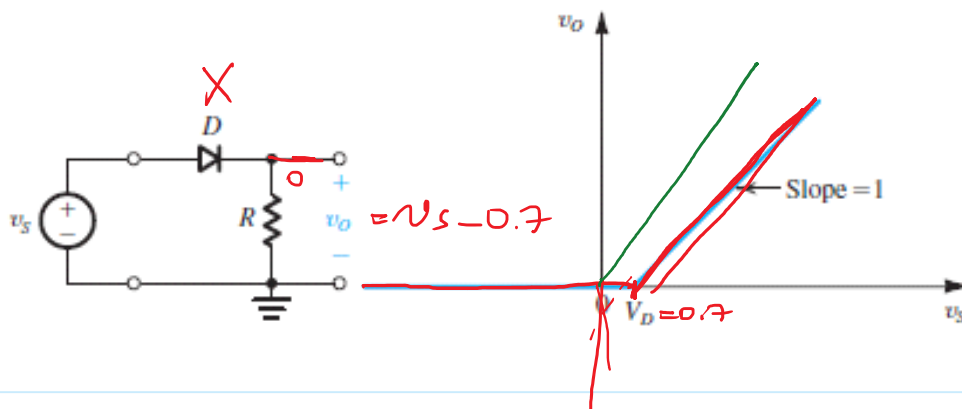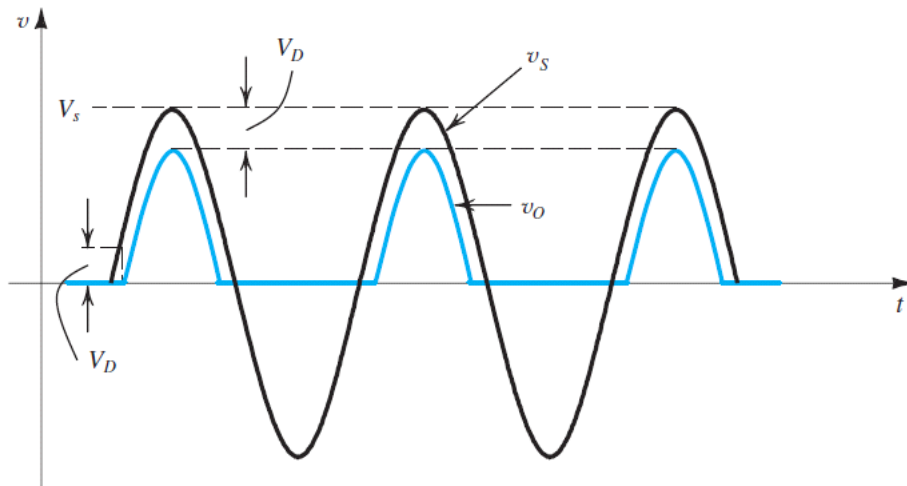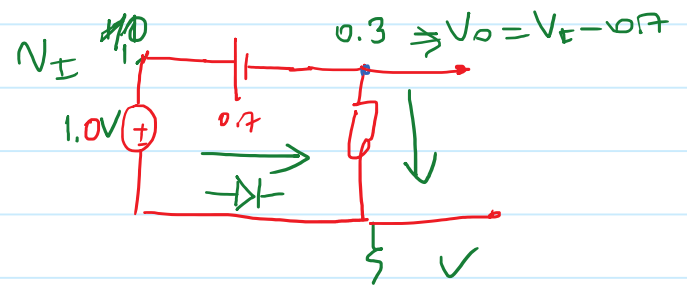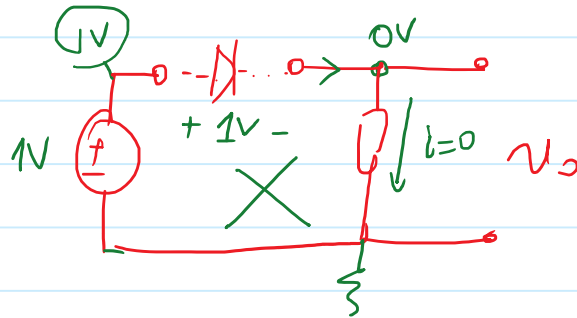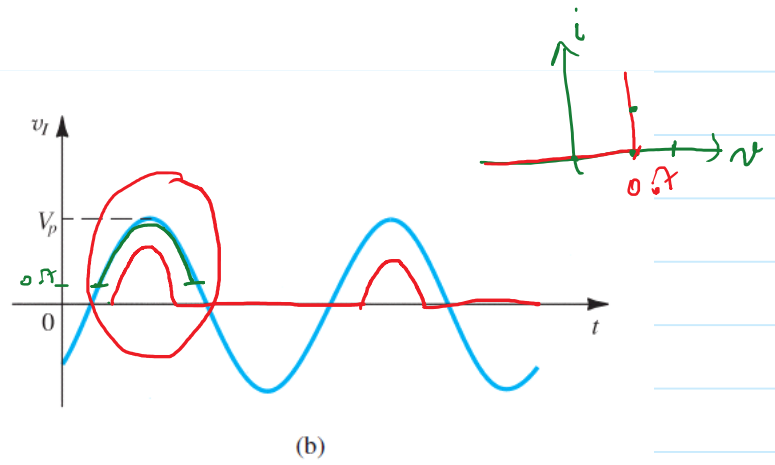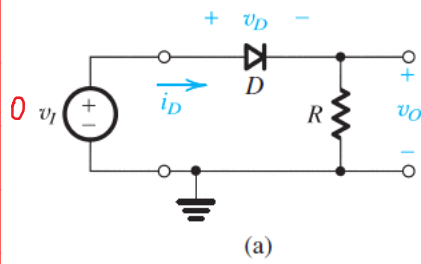





Example



$$2u = 16$$


$$v_o = iR$$

$$\underline{\underline{v_o > 0}}$$



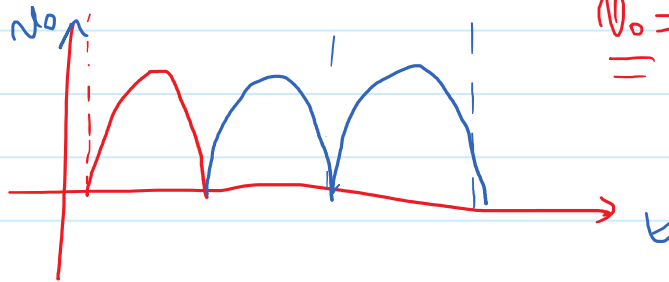
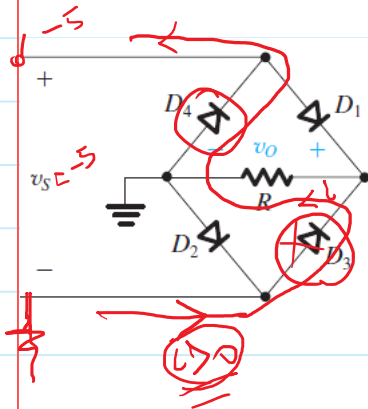
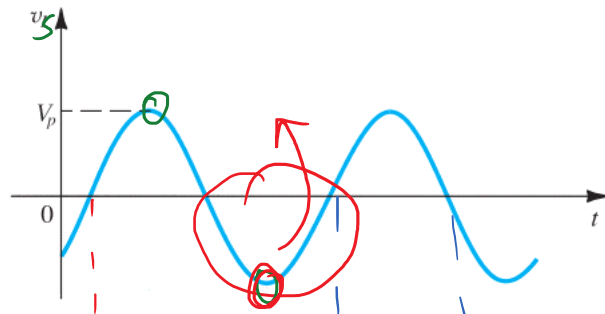
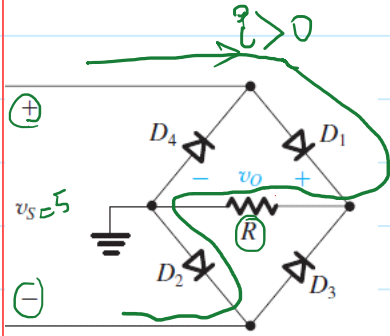


$$\underline{\underline{v_o = iR > 0}}$$



$$\underline{\underline{2 \cdot V_o}}$$

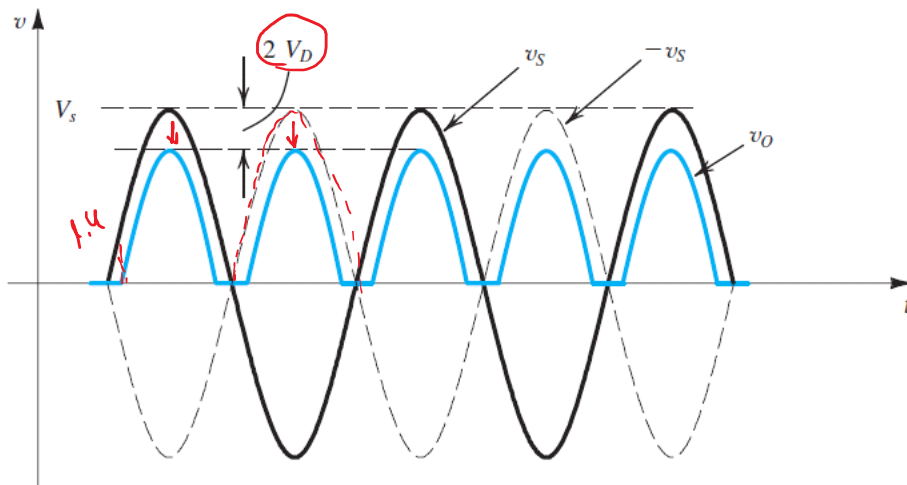



# Reverse Breakdown - Zener Diodes

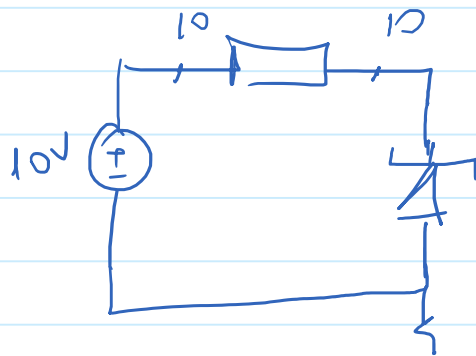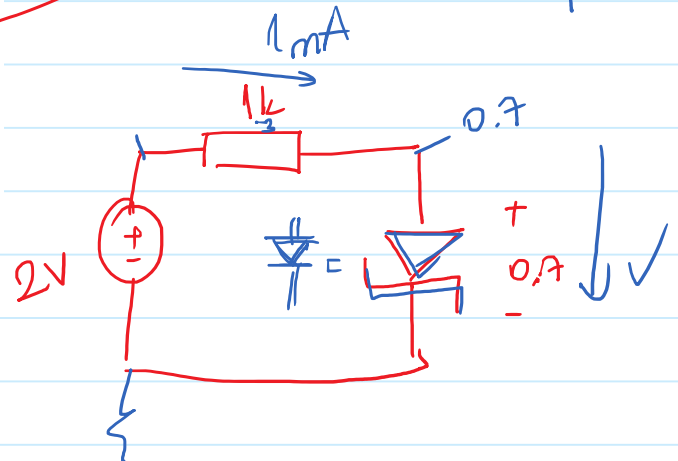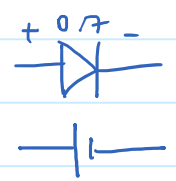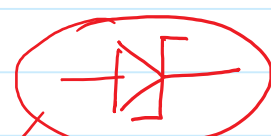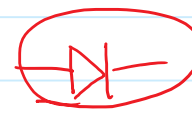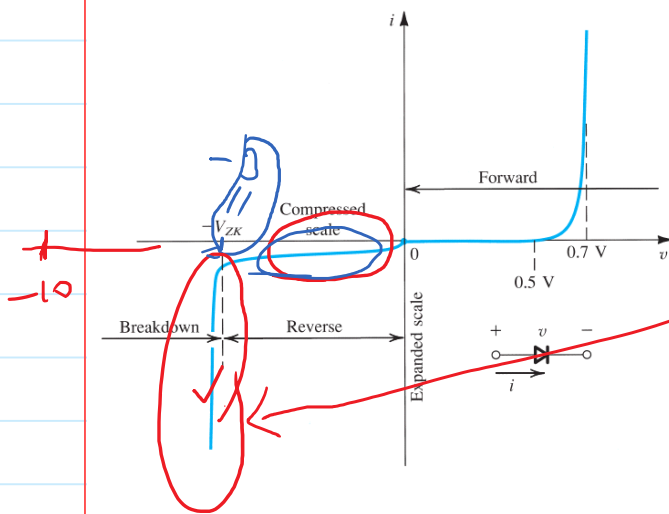

→






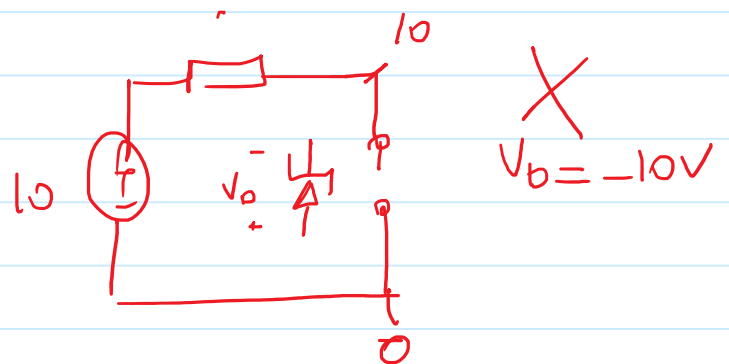
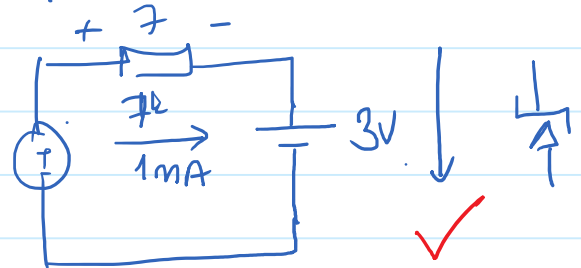


# Limiter Circuits






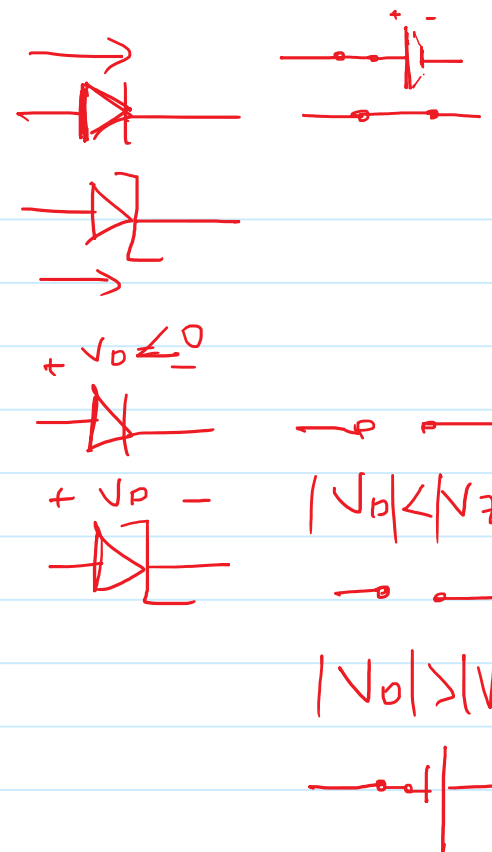
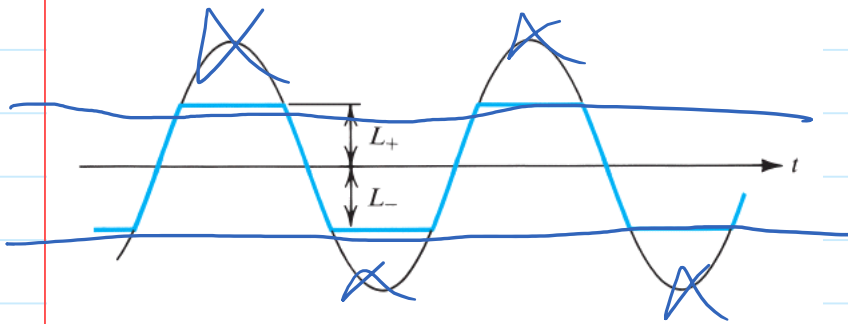







# Example

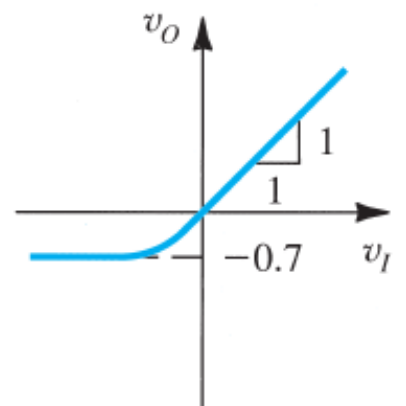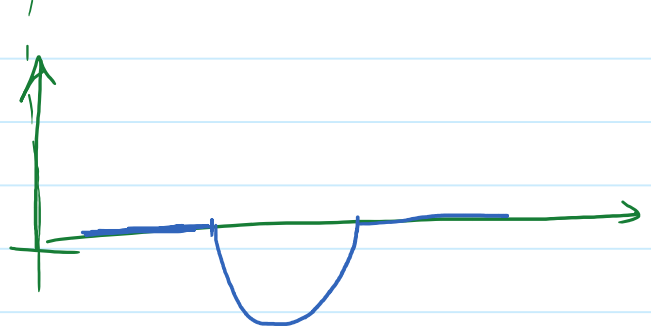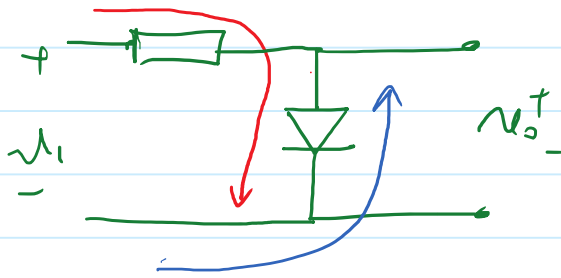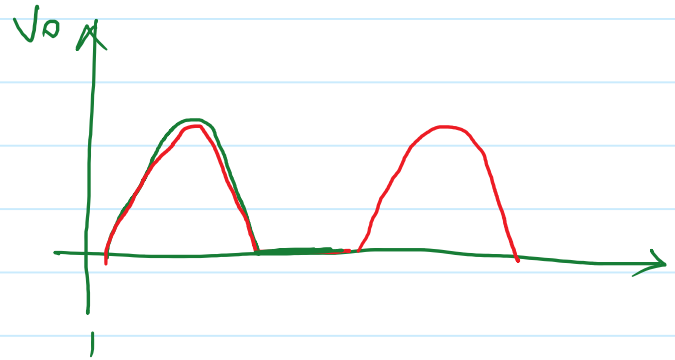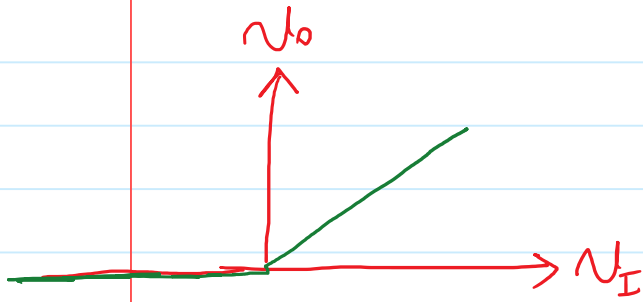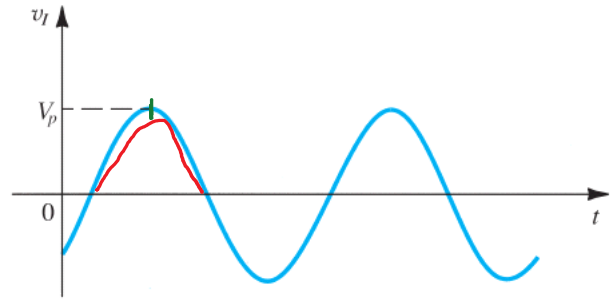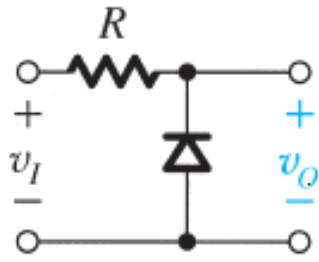





# Example

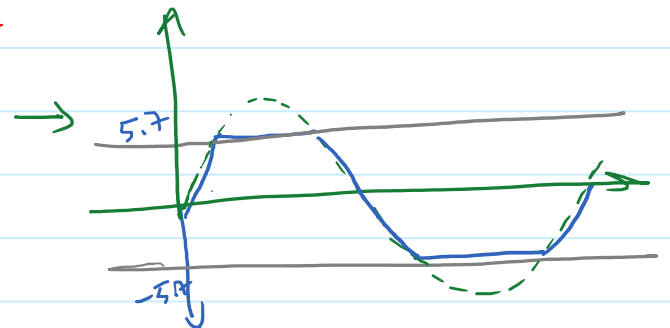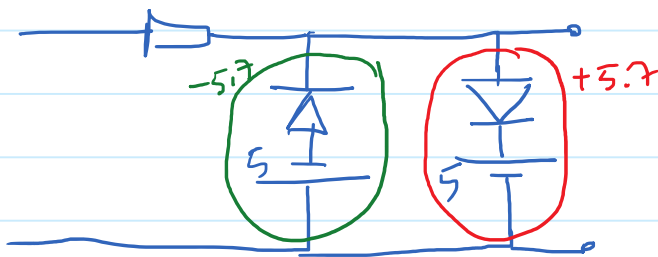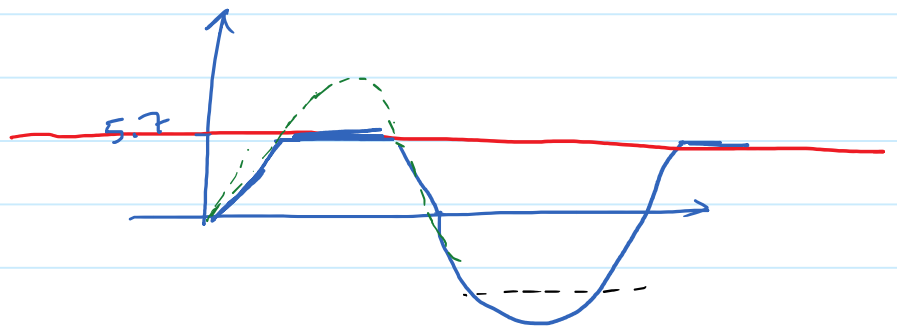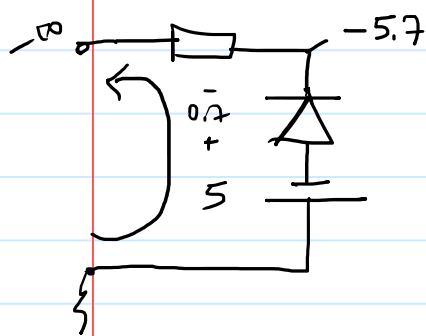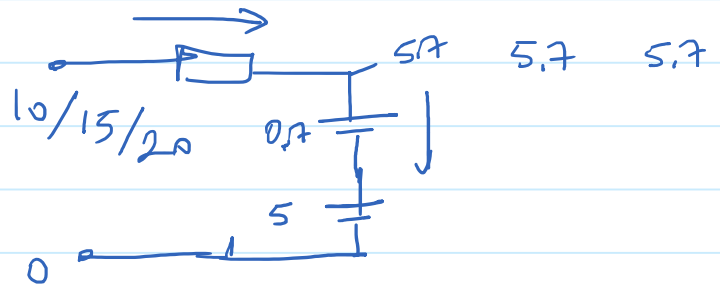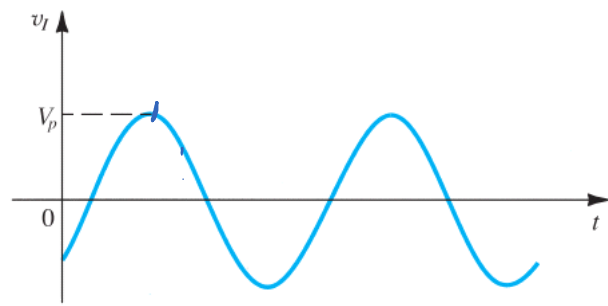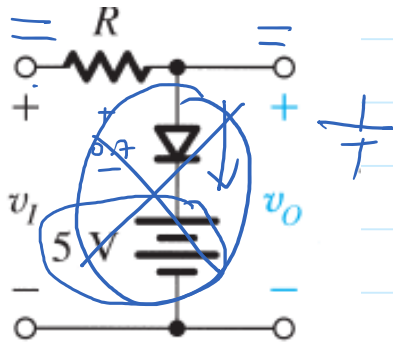


• Zener+

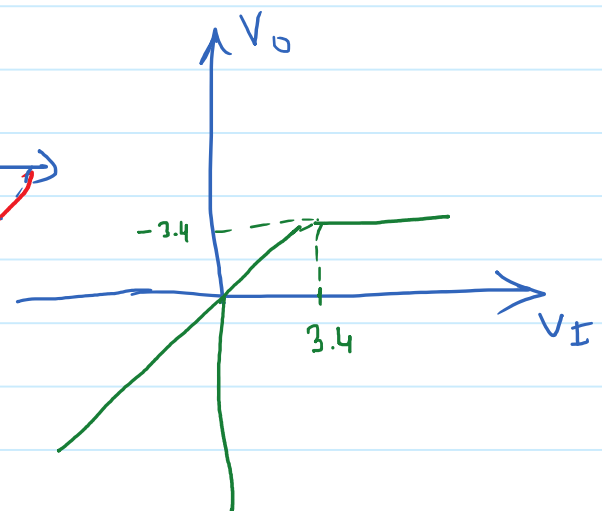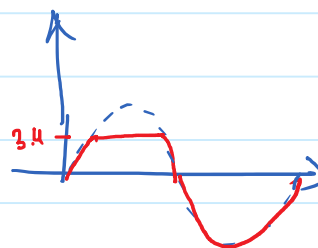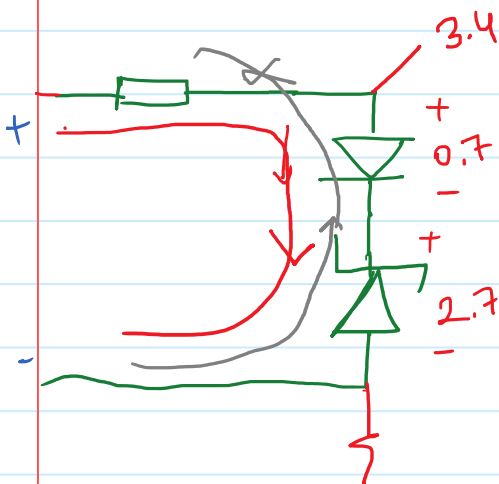





## Example

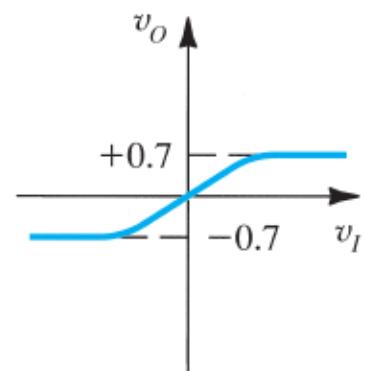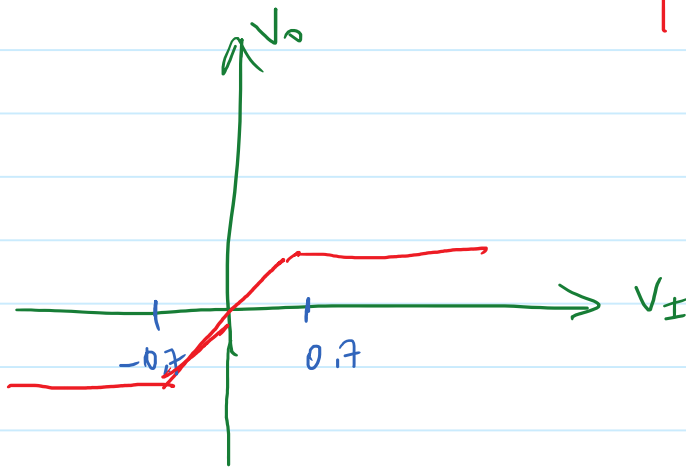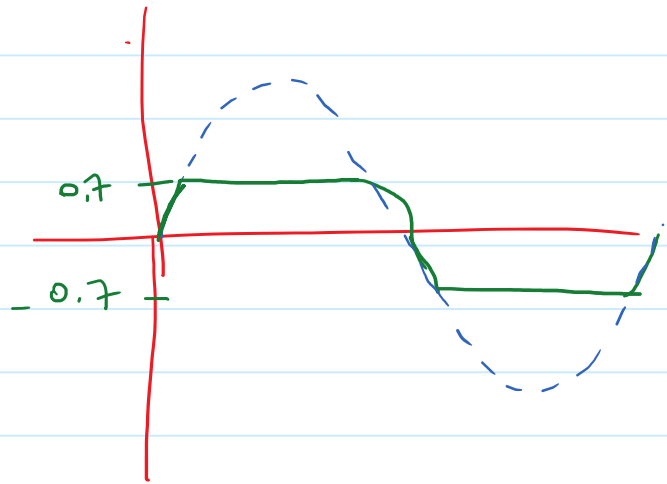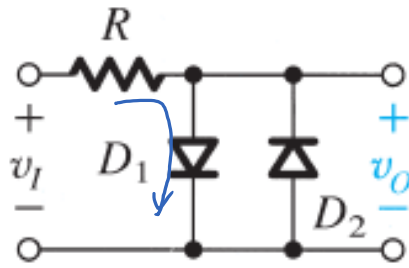




# Example

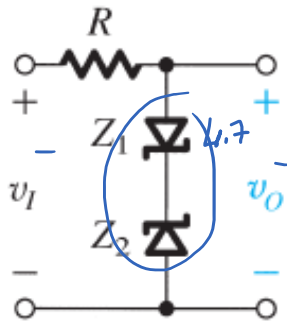





$$V_Z = 4.7$$

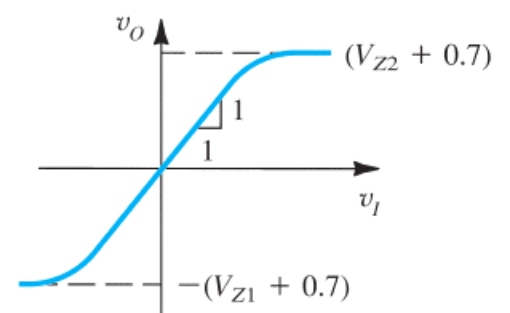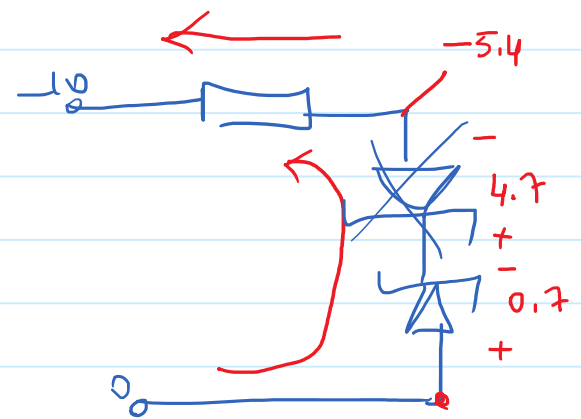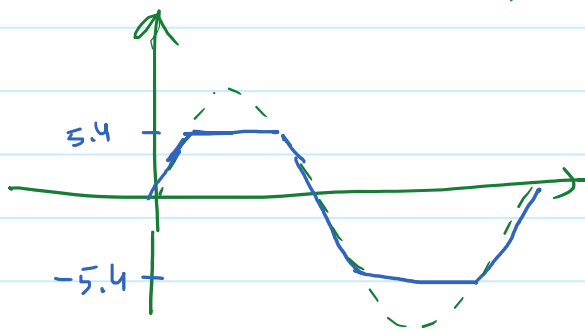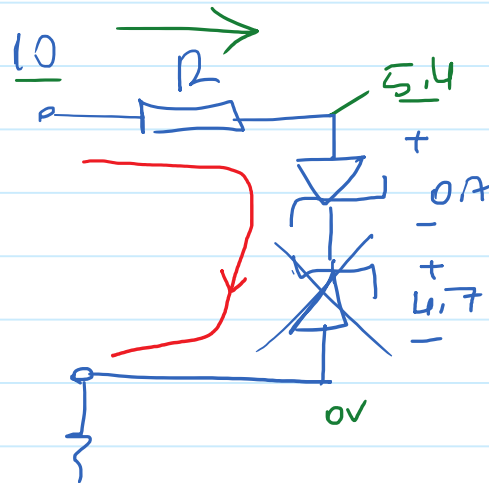

# Review

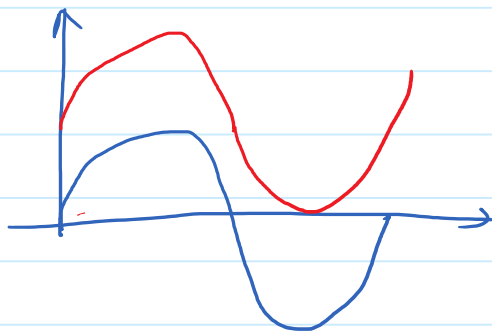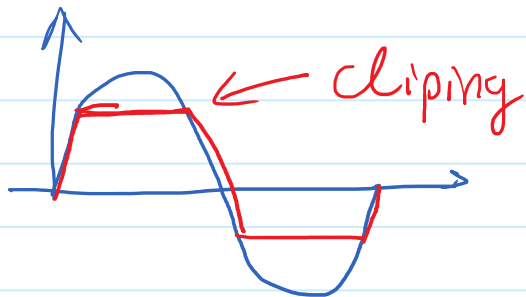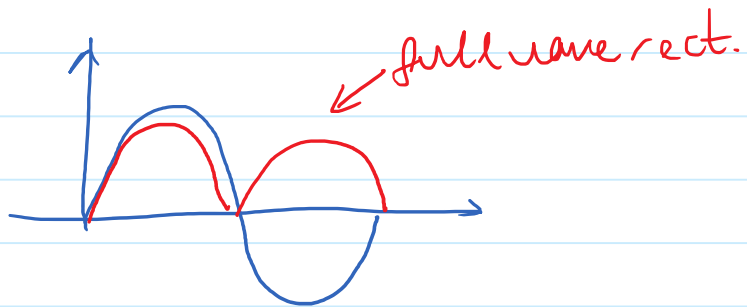

# Clamping Circuit

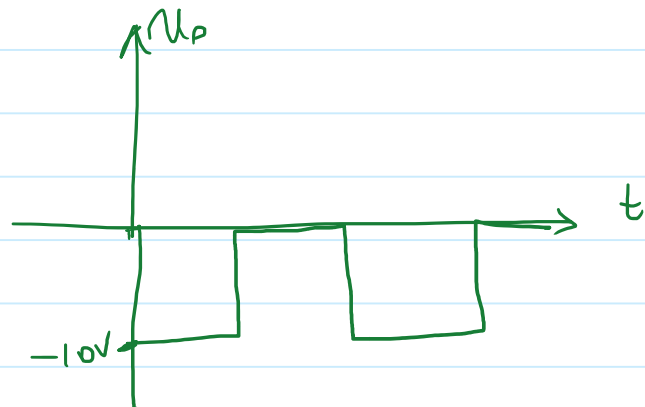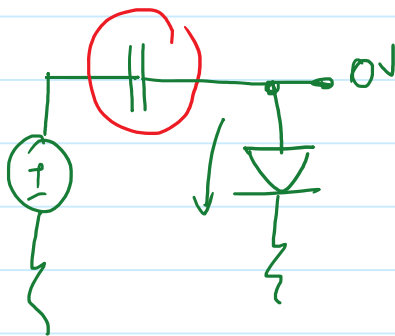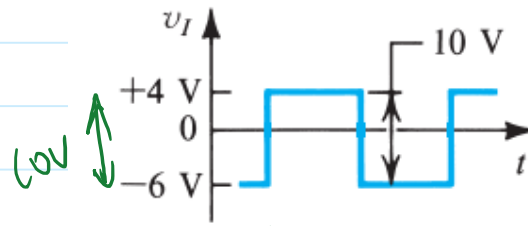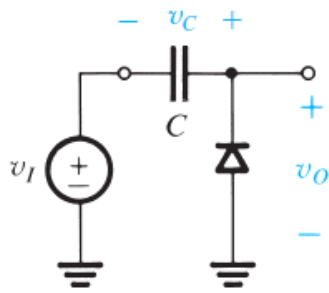

Hobby

