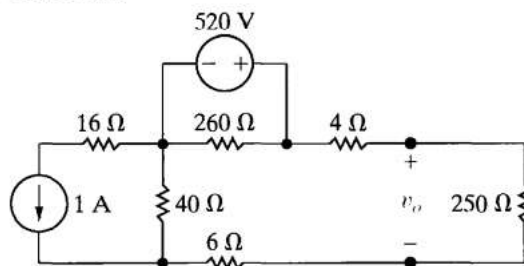



- 4.62** a) Use source transformations to find v_o in the circuit in Fig. P4.62.
 b) Find the power developed by the 520 V source.
 c) Find the power developed by the 1 A current source.
 d) Verify that the total power developed equals the total power dissipated.

PSPICE
MULTISIM


Figure P4.62



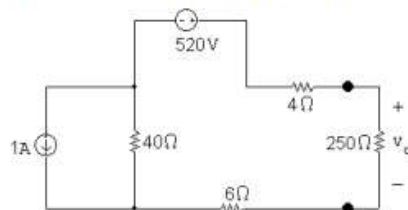
P 4.62 [a] First remove the 16 Ω and 260 Ω resistors:



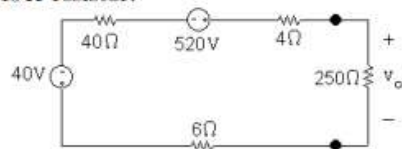Next use a source transformation to convert the 1 A current source and 40 Ω resistor:




which simplifies to

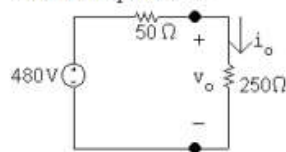

$$\therefore v_o = \frac{250}{300}(480) = 400 \text{ V}$$

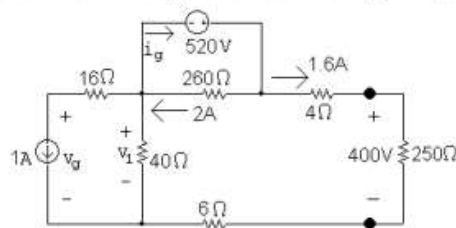[b] Return to the original circuit with $v_o = 400 \text{ V}$:



$$i_g = \frac{520}{260} + 1.6 = 3.6 \text{ A}$$

$$p_{520\text{V}} = -(520)(3.6) = -1872 \text{ W}$$

Therefore, the 520 V source is developing 1872 W.

$$[c] \quad v_1 = -520 + 1.6(4 + 250 + 6) = -104 \text{ V}$$

$$v_g = v_1 - 1(16) = -104 - 16 = -120 \text{ V}$$

$$p_{1\text{A}} = (1)(-120) = -120 \text{ W}$$

Therefore the 1 A source is developing 120 W.

$$[d] \quad \sum p_{\text{dev}} = 1872 + 120 = 1992 \text{ W}$$


$$\sum p_{\text{diss}} = (1)^2(16) + \frac{(104)^2}{40} + \frac{(520)^2}{260} + (1.6)^2(260) = 1992 \text{ W}$$

$$\therefore \sum p_{\text{diss}} = \sum p_{\text{dev}}$$

4.63 Find the Thévenin equivalent with respect to the terminals a,b for the circuit in Fig. P4.63.


PSICE
MULTISIM

Figure P4.63

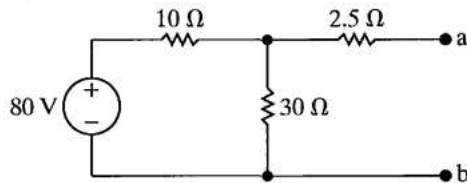

$$P \ 4.63 \quad v_{\text{Th}} = \frac{30}{40}(80) = 60 \text{ V}$$

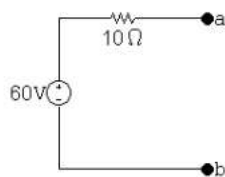
$$R_{\text{Th}} = 2.5 + \frac{(30)(10)}{40} = 10 \Omega$$




4.64 Find the Norton equivalent with respect to the terminals a,b in the circuit in Fig. P4.64.

PSICE
MULTISIM


Figure P4.64

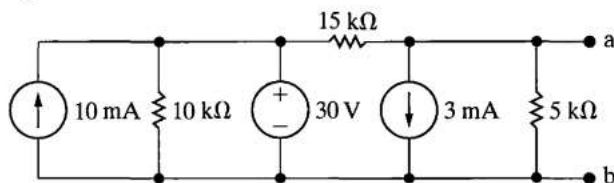

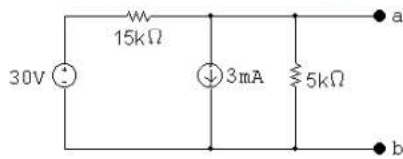
P 4.64 First we make the observation that the 10 mA current source and the $10\text{ k}\Omega$ resistor will have no influence on the behavior of the circuit with respect to the terminals a,b. This follows because they are in parallel with an ideal voltage source. Hence our circuit can be simplified to



or

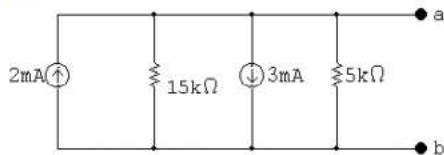


Therefore the Norton equivalent is

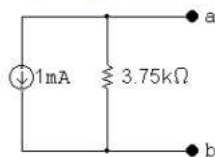


4.66 Find the Thévenin equivalent with respect to the terminals a,b for the circuit in Fig. P4.66.

PSPICE
MULTISIM

Figure P4.66

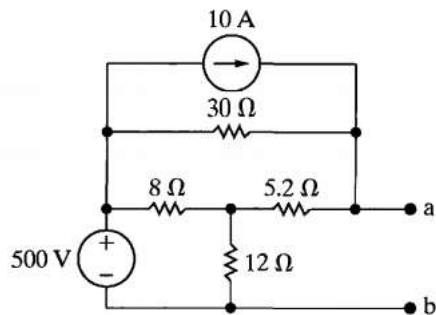

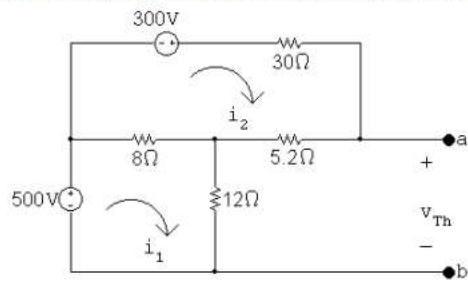P 4.66 After making a source transformation the circuit becomes




$$500 = 20i_1 - 8i_2$$

$$300 = -8i_1 + 43.2i_2$$

$$\therefore i_1 = 30 \text{ A and } i_2 = 12.5 \text{ A}$$

$$v_{Th} = 12i_1 + 5.2i_2 = 425 \text{ V}$$

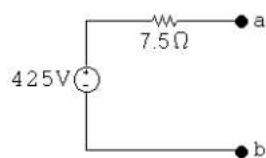
$$R_{Th} = (8 \parallel 12 + 5.2) \parallel 30 = 7.5 \Omega$$






4.68 Determine i_o and v_o in the circuit shown in Fig. P4.68 when R_o is a resistor from Appendix H whose value is less than 100Ω .

PSPICE
MULTISIM

Figure P4.68

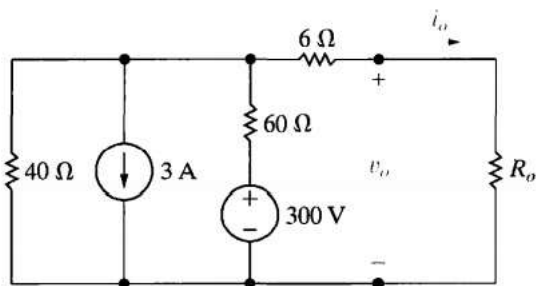

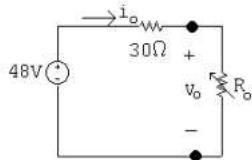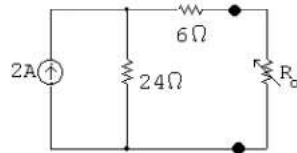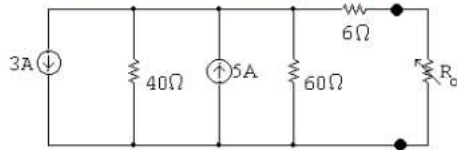P 4.68 First, find the Thévenin equivalent with respect to R_o .





$R_o(\Omega)$	$i_o(\text{A})$	$v_o(\text{V})$
10	1.2	12
15	1.067	16
22	0.923	20.31
33	0.762	25.14
47	0.623	29.30
68	0.490	33.31

4.73 Find the Norton equivalent with respect to the terminals a,b for the circuit seen in Fig. P4.73.

PSPICE
MULTISIM

Figure P4.73

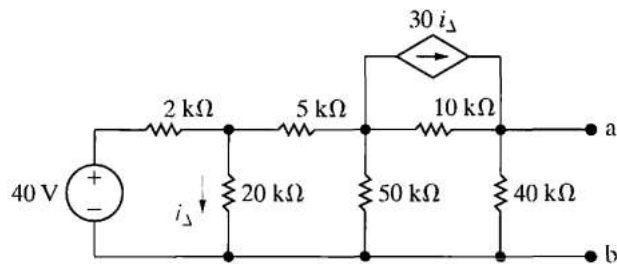

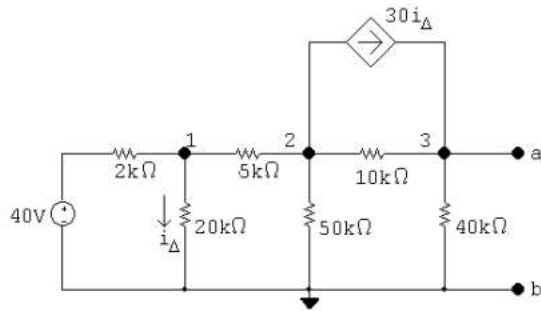

The node voltage equations are:

$$\frac{v_1 - 40}{2000} + \frac{v_1}{20,000} + \frac{v_1 - v_2}{5000} = 0$$

$$\frac{v_2 - v_1}{5000} + \frac{v_2}{50,000} + \frac{v_2 - v_3}{10,000} + 30\frac{v_1}{20,000} = 0$$

$$\frac{v_3 - v_2}{10,000} + \frac{v_3}{40,000} - 30\frac{v_1}{20,000} = 0$$


In standard form:

$$v_1 \left(\frac{1}{2000} + \frac{1}{20,000} + \frac{1}{5000} \right) + v_2 \left(-\frac{1}{5000} \right) + v_3(0) = \frac{40}{2000}$$

$$v_1 \left(-\frac{1}{5000} + \frac{30}{20,000} \right) + v_2 \left(\frac{1}{5000} + \frac{1}{50,000} + \frac{1}{10,000} \right) + v_3 \left(-\frac{1}{10,000} \right) = 0$$

$$v_1 \left(-\frac{30}{20,000} \right) + v_2 \left(-\frac{1}{10,000} \right) + v_3 \left(\frac{1}{10,000} + \frac{1}{40,000} \right) = 0$$

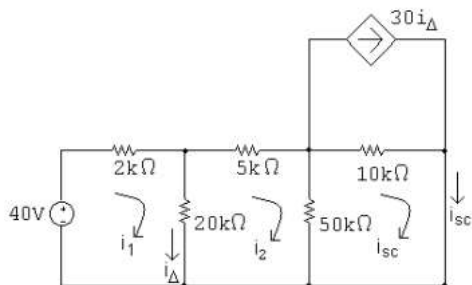Solving, $v_1 = 24 \text{ V}$; $v_2 = -10 \text{ V}$; $v_3 = 280 \text{ V}$
 $V_{\text{Th}} = v_3 = 280 \text{ V}$



The mesh current equations are:

$$-40 + 2000i_1 + 20,000(i_1 - i_2) = 0$$

$$5000i_2 + 50,000(i_2 - i_{sc}) + 20,000(i_2 - i_1) = 0$$

$$50,000(i_{sc} - i_2) + 10,000(i_{sc} - 30i_{\Delta}) = 0$$

The constraint equation is:

$$i_{\Delta} = i_1 - i_2$$

Put these equations in standard form:

$$i_1(22,000) + i_2(-20,000) + i_{sc}(0) + i_{\Delta}(0) = 40$$


$$i_1(-20,000) + i_2(75,000) + i_{sc}(-50,000) + i_{\Delta}(0) = 0$$

$$i_1(0) + i_2(-50,000) + i_{sc}(60,000) + i_{\Delta}(-300,000) = 0$$

$$i_1(-1) + i_2(1) + i_{sc}(0) + i_{\Delta}(1) = 0$$


Solving, $i_1 = 13.6 \text{ mA}$; $i_2 = 12.96 \text{ mA}$; $i_{sc} = 14 \text{ mA}$; $i_{\Delta} = 640 \mu\text{A}$
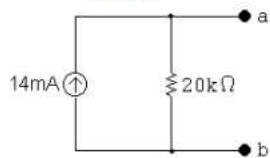
$$R_{Th} = \frac{280}{0.014} = 20 \text{ k}\Omega$$




- 4.78** Find the Norton equivalent with respect to the terminals a,b for the circuit seen in Fig. P4.78.

Figure P4.78

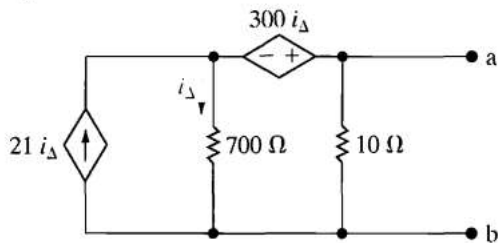

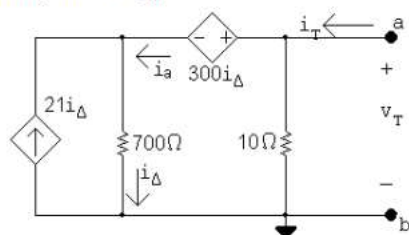P 4.78 $V_{Th} = 0$ since there are no independent sources in the circuit. Thus we need only find R_{Th} .



$$i_T = \frac{v_T}{10} + i_a$$


$$i_a = i_\Delta - 21i_\Delta = -20i_\Delta$$

$$i_\Delta = \frac{v_T - 300i_\Delta}{700}, \quad 1000i_\Delta = v_T$$

$$\therefore i_T = \frac{v_T}{10} - 20 \frac{v_T}{1000} = 0.08v_T$$

$$\frac{v_T}{i_T} = 1/0.08 = 12.5 \Omega$$

$$\therefore R_{Th} = 12.5 \Omega$$

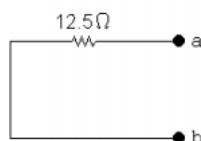


4.79 The variable resistor in the circuit in Fig. P4.79 is adjusted for maximum power transfer to R_o .


PSpice
MULTISIM

- Find the value of R_o .
- Find the maximum power that can be delivered to R_o .
- Find a resistor in Appendix H closest to the value in part (a). How much power is delivered to this resistor?

Figure P4.79

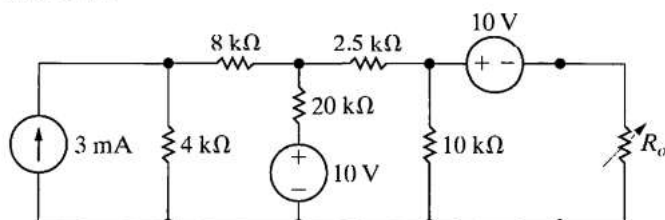

P 4.79 [a]

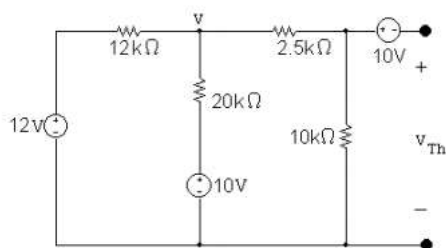


$$\frac{v - 12}{12,000} + \frac{v - 10}{20,000} + \frac{v}{12,500} = 0$$

Solving, $v = 7.03125 \text{ V}$

$$v_{10k} = \frac{10,000}{12,500}(7.03125) = 5.625 \text{ V}$$

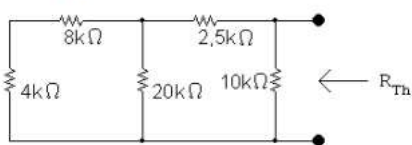
$$\therefore V_{Th} = v - 10 = -4.375 \text{ V}$$



$$R_{Th} = [(12,000 \parallel 20,000) + 2500] = 5 \text{ k}\Omega$$

$$R_o = R_{Th} = 5 \text{ k}\Omega$$

[b]

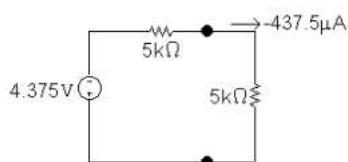

$$p_{\max} = (-437.5 \times 10^{-6})^2(5000) = 957 \mu\text{W}$$

[c] The resistor closest to $5 \text{ k}\Omega$ from Appendix H has a value of $4.7 \text{ k}\Omega$. Use voltage division to find the voltage drop across this load resistor, and use the voltage to find the power delivered to it:

$$v_{4.7k} = \frac{4700}{4700 + 5000}(-4.375) = -2.12 \text{ V}$$

$$p_{4.7k} = \frac{(-2.12)^2}{4700} = 956.12 \mu\text{W}$$

The percent error between the maximum power and the power delivered to the best resistor from Appendix H is


$$\% \text{ error} = \left(\frac{956}{957} - 1 \right) (100) = -0.1\%$$

4.87 The variable resistor (R_L) in the circuit in Fig. P4.87 is adjusted for maximum power transfer to R_L .

PSPICE
MULTISIM


- Find the numerical value of R_L .
- Find the maximum power transferred to R_L .

Figure P4.87

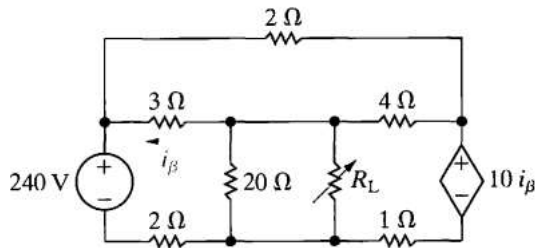

P 4.87 [a] Find the Thévenin equivalent with respect to the terminals of R_L .

Open circuit voltage:

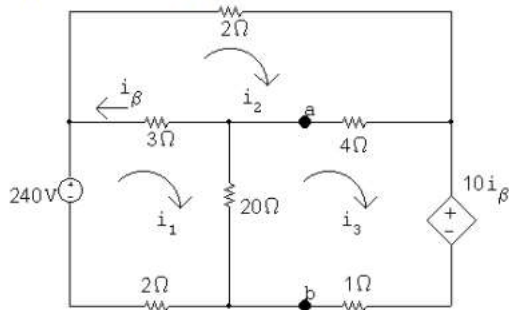

The mesh current equations are:

$$-240 + 3(i_1 - i_2) + 20(i_1 - i_3) + 2i_1 = 0$$

$$2i_2 + 4(i_2 - i_3) + 3(i_2 - i_1) = 0$$

$$10i_β + 1i_3 + 20(i_3 - i_1) + 4(i_3 - i_2) = 0$$

The dependent source constraint equation is:

$$i_β = i_2 - i_1$$

Place these equations in standard form:

$$i_1(3 + 20 + 2) + i_2(-3) + i_3(-20) + i_β(0) = 240$$


$$i_1(-3) + i_2(2 + 4 + 3) + i_3(-4) + i_β(0) = 0$$

$$i_1(-20) + i_2(-4) + i_3(1 + 20 + 4) + i_β(10) = 0$$

$$i_1(-1) + i_2(1) + i_3(0) + i_β(-1) = 0$$

Solving, $i_1 = 99.6 \text{ A}$; $i_2 = 78 \text{ A}$; $i_3 = 100.8 \text{ A}$; $i_β = 21.6 \text{ A}$
 $V_{Th} = 20(i_1 - i_3) = -24 \text{ V}$

Short-circuit current:

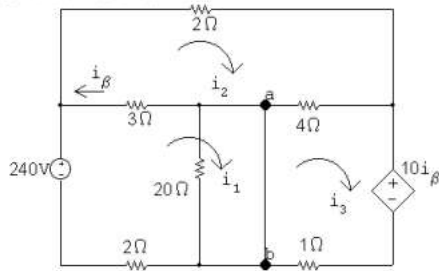

The mesh current equations are:

$$-240 + 3(i_1 - i_2) + 2i_1 = 0$$

$$2i_2 + 4(i_2 - i_3) + 3(i_2 - i_1) = 0$$

$$10i_β + 1i_3 + 4(i_3 - i_2) = 0$$

The dependent source constraint equation is:

$$i_β = i_2 - i_1$$

Place these equations in standard form:

$$i_1(3 + 2) + i_2(-3) + i_3(0) + i_β(0) = 240$$


$$i_1(-3) + i_2(2 + 4 + 3) + i_3(-4) + i_β(0) = 0$$

$$i_1(0) + i_2(-4) + i_3(4 + 1) + i_β(10) = 0$$

$$i_1(-1) + i_2(1) + i_3(0) + i_β(-1) = 0$$

Solving, $i_1 = 92 \text{ A}$; $i_2 = 73.33 \text{ A}$; $i_3 = 96 \text{ A}$; $i_β = 18.67 \text{ A}$
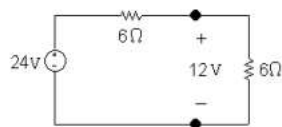
$$i_{sc} = i_1 - i_3 = -4 \text{ A}; \quad R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{-24}{-4} = 6 \Omega$$




$$R_L = R_{Th} = 6 \Omega$$

$$[b] \quad p_{max} = \frac{12^2}{6} = 24 \text{ W}$$


4.96 Use the principle of superposition to find the voltage v in the circuit of Fig. P4.96.

PSPICE
MULTISIM

Figure P4.96

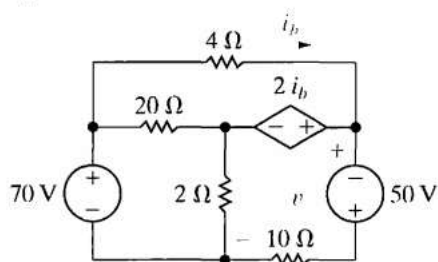

P 4.96 70-V source acting alone:

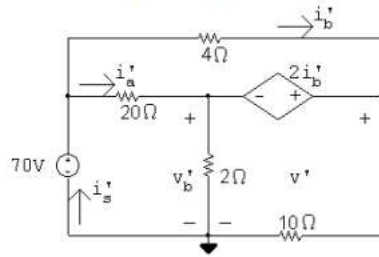

$$v' = 70 - 4i'_b$$

$$i'_s = \frac{v'_b}{2} + \frac{v'}{10} = i'_a + i'_b$$

$$70 = 20i'_a + v'_b$$

$$i'_a = \frac{70 - v'_b}{20}$$

$$\therefore i'_b = \frac{v'_b}{2} + \frac{v'}{10} - \frac{70 - v'_b}{20} = \frac{11}{20}v'_b + \frac{v'}{10} - 3.5$$

$$v' = v'_b + 2i'_b$$

$$\therefore v'_b = v' - 2i'_b$$

$$\therefore i'_b = \frac{11}{20}(v' - 2i'_b) + \frac{v'}{10} - 3.5 \quad \text{or} \quad i'_b = \frac{13}{42}v' - \frac{70}{42}$$


$$v' = v'_b + 2i'_b$$

$$\therefore v'_b = v' - 2i'_b$$

$$\therefore i'_b = \frac{11}{20}(v' - 2i'_b) + \frac{v'}{10} - 3.5 \quad \text{or} \quad i'_b = \frac{13}{42}v' - \frac{70}{42}$$

$$\therefore v' = 70 - 4\left(\frac{13}{42}v' - \frac{70}{42}\right) \quad \text{or} \quad v' = \frac{3220}{94} = \frac{1610}{47} \text{ V} = 34.255 \text{ V}$$

50-V source acting alone:

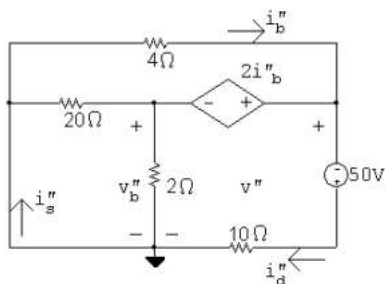

$$v'' = -4i''_b$$

$$v'' = v_b'' + 2i_b''$$

$$v'' = -50 + 10i_d''$$

$$\therefore i_d'' = \frac{v'' + 50}{10}$$

$$i_s'' = \frac{v_b''}{2} + \frac{v'' + 50}{10}$$

$$i_b'' = \frac{v_b''}{20} + i_s'' = \frac{v_b''}{20} + \frac{v_b''}{2} + \frac{v'' + 50}{10} = \frac{11}{20}v_b'' + \frac{v'' + 50}{10}$$

$$v_b'' = v'' - 2i_b''$$

$$\therefore i_b'' = \frac{11}{20}(v'' - 2i_b'') + \frac{v'' + 50}{10} \quad \text{or} \quad i_b'' = \frac{13}{42}v'' + \frac{100}{42}$$


$$\text{Thus, } v'' = -4\left(\frac{13}{42}v'' + \frac{100}{42}\right) \quad \text{or} \quad v'' = -\frac{200}{47} \text{ V} = -4.255 \text{ V}$$

$$\text{Hence, } v = v' + v'' = \frac{1610}{47} - \frac{200}{47} = \frac{1410}{47} = 30 \text{ V}$$


4.97 Use the principle of superposition to find v_o in the circuit in Fig. P4.97.

PSPICE
MULTISIM

Figure P4.97

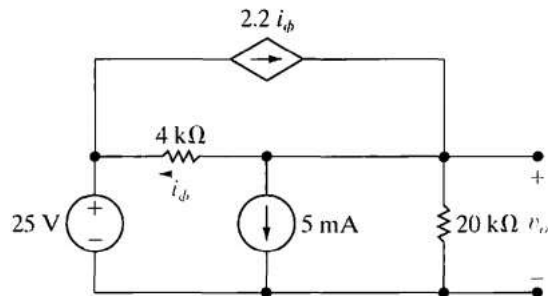

P 4.97 Voltage source acting alone:

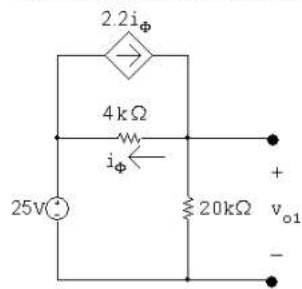


$$\frac{v_{o1} - 25}{4000} + \frac{v_{o1}}{20,000} - 2.2 \left(\frac{v_{o1} - 25}{4000} \right) = 0$$

Simplifying $5v_{o1} - 125 + v_{o1} - 11v_{o1} + 275 = 0$

$$\therefore v_{o1} = 30 \text{ V}$$

Current source acting alone:

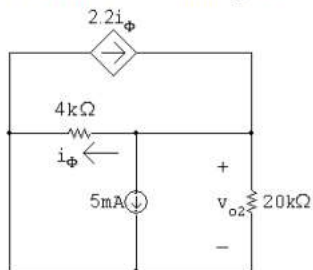

$$\frac{v_{o2}}{4000} + \frac{v_{o2}}{20,000} + 0.005 - 2.2 \left(\frac{v_{o2}}{4000} \right) = 0$$

Simplifying $5v_{o2} + v_{o2} + 100 - 11v_{o2} = 0$

$$\therefore v_{o2} = 20 \text{ V}$$


$$v_o = v_{o1} + v_{o2} = 30 + 20 = 50 \text{ V}$$

CHAPTER 5

5.2 Find i_o in the circuit in Fig. P5.2 if the op amp is ideal.

PSICE
MULTISIM

Figure P5.2

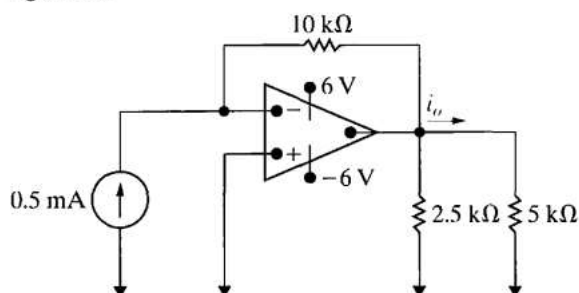

P 5.2 $v_o = -(0.5 \times 10^{-3})(10,000) = -5 \text{ V}$


$$\therefore i_o = \frac{v_o}{5000} = \frac{-5}{5000} = -1 \text{ mA}$$

5.3 The op amp in the circuit in Fig. P5.3 is ideal.

PSICE
MULTISIM

- Calculate v_o if $v_a = 4 \text{ V}$ and $v_b = 0 \text{ V}$.
- Calculate v_o if $v_a = 2 \text{ V}$ and $v_b = 0 \text{ V}$.
- Calculate v_o if $v_a = 2 \text{ V}$ and $v_b = 1 \text{ V}$.
- Calculate v_o if $v_a = 1 \text{ V}$ and $v_b = 2 \text{ V}$.
- Calculate v_o if $v_a = 1.5 \text{ V}$ and $v_b = 4 \text{ V}$.
- If $v_b = 1.6 \text{ V}$, specify the range of v_a such that the amplifier does not saturate.

Figure P5.3

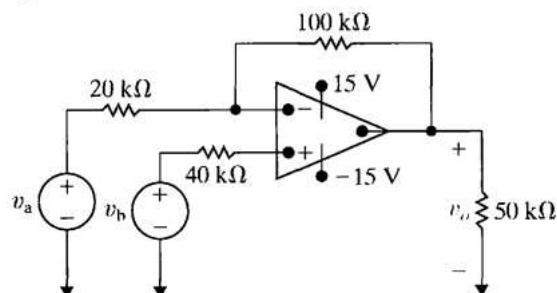

P 5.3 $\frac{v_b - v_a}{20,000} + \frac{v_b - v_o}{100,000} = 0$, therefore $v_o = 6v_b - 5v_a$

[a] $v_a = 4 \text{ V}$, $v_b = 0 \text{ V}$, $v_o = -15 \text{ V}$ (sat)

[b] $v_a = 2 \text{ V}$, $v_b = 0 \text{ V}$, $v_o = -10 \text{ V}$

[c] $v_a = 2 \text{ V}$, $v_b = 1 \text{ V}$, $v_o = -4 \text{ V}$

[d] $v_a = 1 \text{ V}$, $v_b = 2 \text{ V}$, $v_o = 7 \text{ V}$


[e] $v_a = 1.5 \text{ V}$, $v_b = 4 \text{ V}$, $v_o = 15 \text{ V}$ (sat)

[f] If $v_b = 1.6 \text{ V}$, $v_o = 9.6 - 5v_a = \pm 15$

$\therefore -1.08 \text{ V} \leq v_a \leq 4.92 \text{ V}$

5.4 Find i_L (in microamperes) in the circuit in Fig. P5.4.

PSPICE
MULTISIM **Figure P5.4**

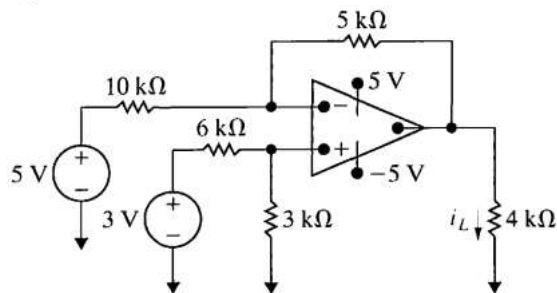

P 5.4 $v_p = \frac{3000}{3000 + 6000}(3) = 1 \text{ V} = v_n$

$$\frac{v_n - 5}{10,000} + \frac{v_n - v_o}{5000} = 0$$

$$(1 - 5) + 2(1 - v_o) = 0$$


$$v_o = -1.0 \text{ V}$$

$$i_L = \frac{v_o}{4000} = -\frac{1}{4000} = -250 \times 10^{-6}$$

$$i_L = -250 \mu\text{A}$$

- 5.5** A voltmeter with a full-scale reading of 10 V is used to measure the output voltage in the circuit in Fig. P5.5. What is the reading of the voltmeter? Assume the op amp is ideal.

Figure P5.5

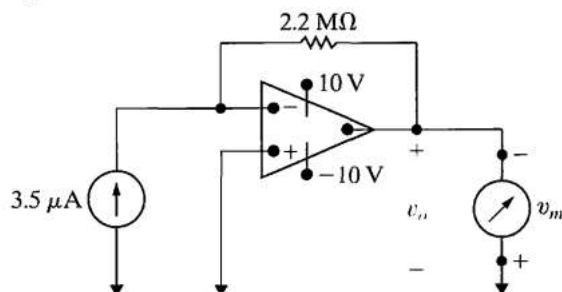


- P 5.5 Since the current into the inverting input terminal of an ideal op-amp is zero, the voltage across the $2.2 \text{ M}\Omega$ resistor is $(2.2 \times 10^6)(3.5 \times 10^{-6})$ or 7.7 V. Therefore the voltmeter reads 7.7 V.

- 5.6** The op amp in the circuit in Fig. P5.6 is ideal. Calculate the following:

- v_1
- v_o
- i_2
- i_o

Figure P5.6

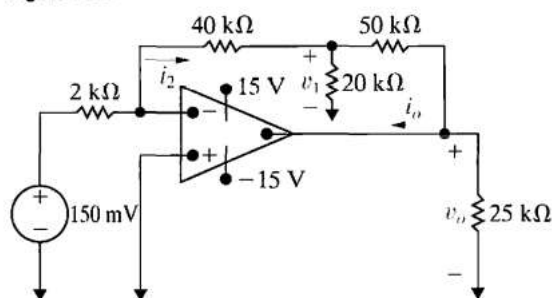


- P 5.6 [a] $i_2 = \frac{150 \times 10^{-3}}{2000} = 75 \mu\text{A}$
 $v_1 = -40 \times 10^3 i_2 = -3 \text{ V}$
 [b] $\frac{v_1}{20,000} + \frac{v_1}{40,000} + \frac{v_1 - v_o}{50,000} = 0$
 $\therefore v_o = 4.75 v_1 = -14.25 \text{ V}$
 [c] $i_2 = 75 \mu\text{A}$, (from part [a])
 [d] $i_o = \frac{-v_o}{25,000} + \frac{v_1 - v_o}{50,000} = 795 \mu\text{A}$

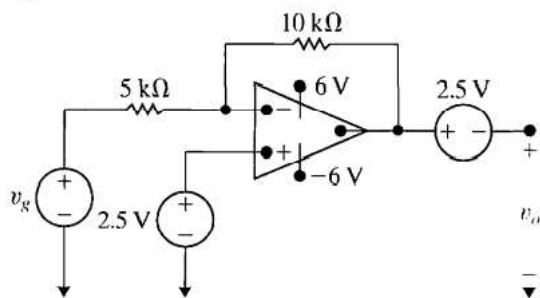5.7 A circuit designer claims the circuit in Fig. P5.7 will produce an output voltage that will vary between ± 5 as v_g varies between 0 and 5 V. Assume the op amp is ideal.

PRACTICAL
PERSPECTIVE
PSICE
MULTISIM

- Draw a graph of the output voltage v_o as a function of the input voltage v_g for $0 \leq v_g \leq 5$ V.
- Do you agree with the designer's claim?




P 5.7 [a] First, note that $v_n = v_p = 2.5$ V

Let v_{o1} equal the voltage output of the op-amp. Then

$$\frac{2.5 - v_g}{5000} + \frac{2.5 - v_{o1}}{10,000} = 0, \quad \therefore v_{o1} = 7.5 - 2v_g$$

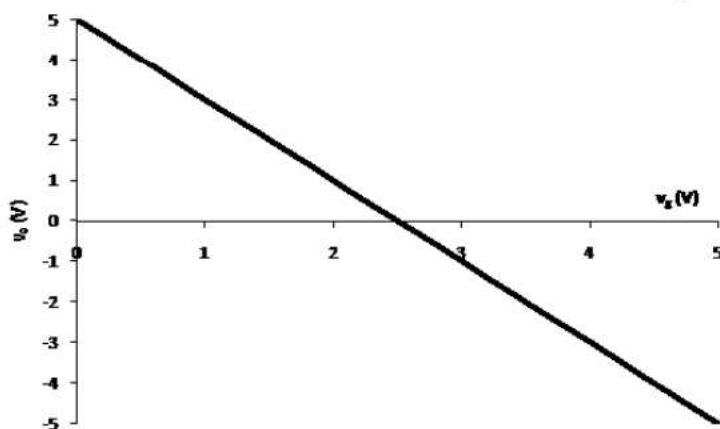Also note that $v_{o1} - 2.5 = v_o$, $\therefore v_o = 5 - 2v_g$



[b] Yes, the circuit designer is correct!