

On my honor, I have neither given nor received any unauthorized and or inappropriate assistance for this exam. The work done on this exam is totally my own. I understand by school code, violation of these principles will lead to a zero grade and is subject to harsh discipline issues.

Question

Q2)
$$\frac{d^2 V_c(t)}{dt^2} + \frac{R}{L} \cdot \frac{dV_c(t)}{dt} + \frac{1}{LC} \cdot V_c(t) = \frac{V_g}{LC}$$

$$\frac{d^2 V_c(t)}{dt^2} + \frac{R}{10 \cdot 10^{-3}} \cdot \frac{dV_c(t)}{dt} + \frac{1}{(10 \cdot 10^{-3})(10^{-6})} \cdot V_c(t) = \frac{10}{(10 \cdot 10^{-3})(10^{-6})}$$

$$\frac{d^2 V_c(t)}{dt^2} + 100 R \cdot \frac{dV_c(t)}{dt} + 10^8 V_c(t) = 10^9 \quad R = 200 \Omega$$

$$\frac{d^2 V_c(t)}{dt^2} + 20000 R \cdot \frac{dV_c(t)}{dt} + 10^8 V_c(t) = 10^9$$

= 0

$$s^2 + 20000 s + 10^8 = 0 \quad s = -10000$$

$$V_c(t) = K_1 \cdot e^{-10000 t} + 10$$

$$V_c(0) = K_1 \cdot e^{-10000 \cdot 0} + 10 = 0$$


$$K_1 = -10$$

$$= 10^{-6} [-10000 K_1 \cdot e^{-10000 t}] = 0$$

$$V_c(t) = (10 - 10 \cdot e^{-10000 t}) \cdot V$$

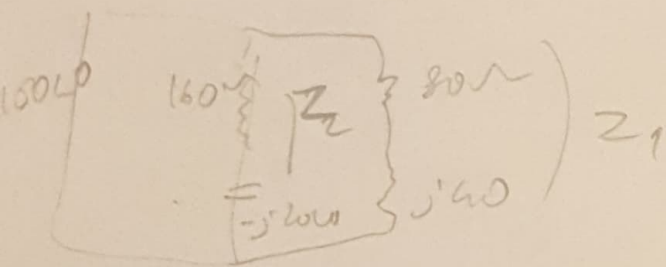Q5) $X_C = \frac{-j}{\omega C} = \frac{-j \cdot 10^6}{2000 \cdot 5} = -j100 \Omega$

$X_L = j\omega L = j(2000 \cdot 25 \cdot 10^{-3}) = j48 \Omega$



$Z_1 = 80 + j48$


$Z_2 = 160 - j200$

$$P_1 = \frac{(150\angle 0)(80 + j48)}{160 - j200 + 80 + j48} = \frac{(150)(\sqrt{80^2 + 48^2} \angle \tan^{-1}(\frac{48}{80}))}{240 - j152}$$

$$= \frac{(150)(93.3 \angle 43.83^\circ)}{245.56 \angle -12.22^\circ} = 57 \angle 56.05^\circ$$

$V_o = (P_1)(160) = (57 \angle 56.05^\circ)(160) = 9120 \angle 56.05^\circ$

$V_o = 9120 \cos(2000t + 56.05^\circ)$

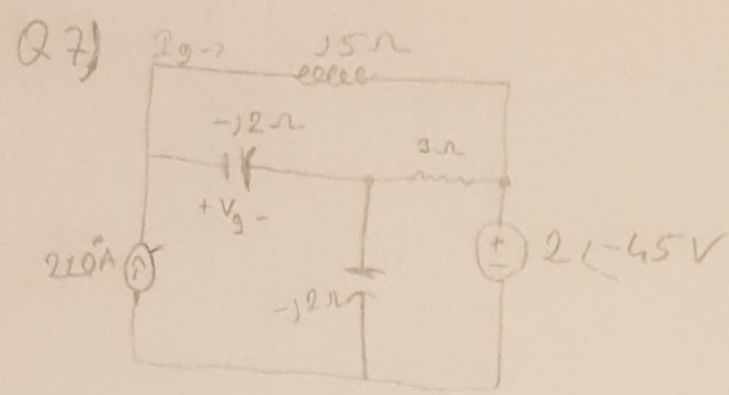

$$-2\angle 0^\circ + \frac{V_1 - 2\angle -45^\circ}{j5} + \frac{V_1 - V_2}{-j2} = 0$$

$$V_1 \left[\frac{1}{j5} - \frac{1}{j2} \right] + V_2 \left[\frac{1}{j2} \right] = 2\angle 0^\circ + \frac{2\angle -45^\circ}{j5}$$

$$\frac{V_2 - V_1}{-j2} + \frac{V_2}{-j2} + \frac{V_2 - 2\angle -45^\circ}{3} = 0$$

$$V_1 [0.5j] + V_2 [1.0541 \angle 71.565^\circ] = \frac{2}{3} \angle -45^\circ$$

$$V_1 = -1.3253 + j(-3.62) \quad V_2 = -0.2295 + j1.2622$$

$$V_g = V_1 - V_2 = -1.3253 - j3.62 - (-0.2295 + j1.2622)$$

$$V_g = -1.0958 - j4.8822$$

$$V_g = 5 \angle -102.65^\circ \text{ V}$$

Hüseyin Karam
Mican

150119629