

Q1


Student ID \rightarrow xx ... $\overbrace{\quad 4 \quad 3 \quad 2 \quad 1}^{\text{last four digits}}$

$\downarrow \quad \downarrow \quad \downarrow^{\text{fixed}}$

$$V_I = (3 + 1) - 20 = -16$$

$V_I = \boxed{?}$ Write only the answer, no calculations!!!

Q2

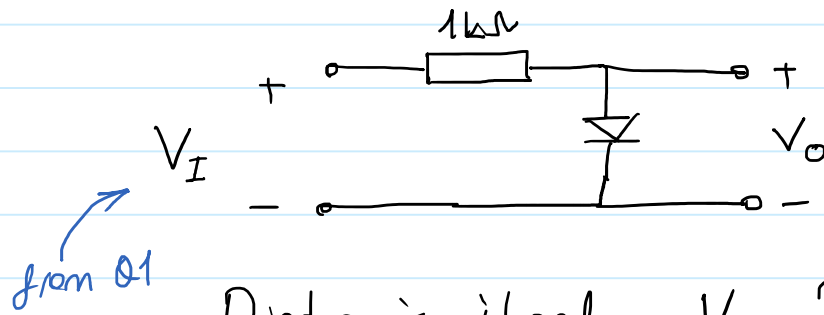


Diodes is ideal. $V_O = ?$

$V_I < 0$ thus the diode will be off.


$$\underline{\underline{V_O = V_I}}$$

Q3

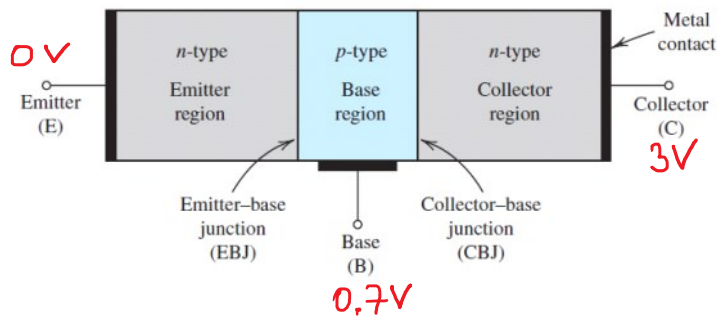

In which region the BJT is operating?
cutoff/active/saturation

Table 6.1 BJT Modes of Operation		
Mode	EBJ	CBJ
Cutoff	Reverse	Reverse
Active	Forward	Reverse
Saturation	Forward	Forward

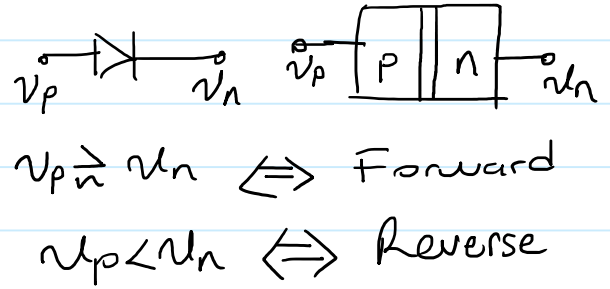

$$v_p \geq v_n \Leftrightarrow \text{Forward}$$


$$v_p < v_n \Leftrightarrow \text{Reverse}$$

$$(EBJ) \quad v_B - v_E = v_p - v_n = 0.7 \quad \text{Forward}$$

$$(CBJ) \quad v_B - v_C = v_p - v_n = -2.3 \quad \text{Reverse}$$


Active Mode

Q3

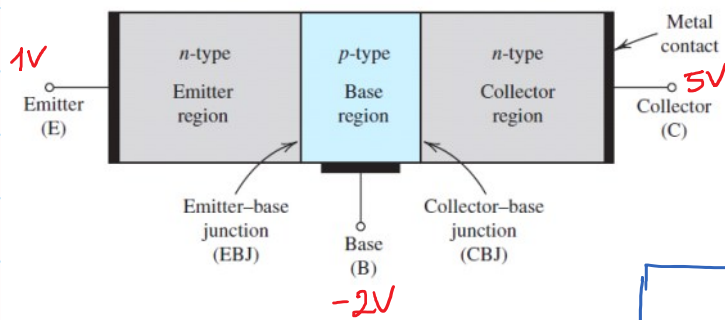

In which region the BJT is operating?
cutoff/active/saturation

Mode	EBJ	CBJ
Cutoff	Reverse	Reverse
Active	Forward	Reverse
Saturation	Forward	Forward

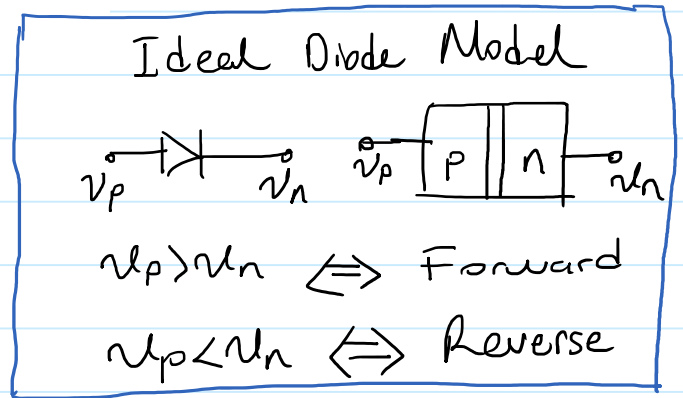


EBJ $V_B - V_E = -2 - 1 = -3$ Reverse

CBJ $V_B - V_C = -2 - 5 = -7$ Reverse


Cutoff

Q3

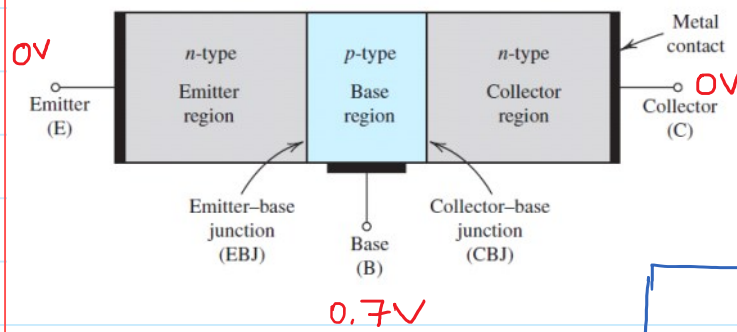

In which region the BJT is operating?
cutoff/active/saturation

Table 6.1 BJT Modes of Operation		
Mode	EBJ	CBJ
Cutoff	Reverse	Reverse
Active	Forward	Reverse
Saturation	Forward	Forward

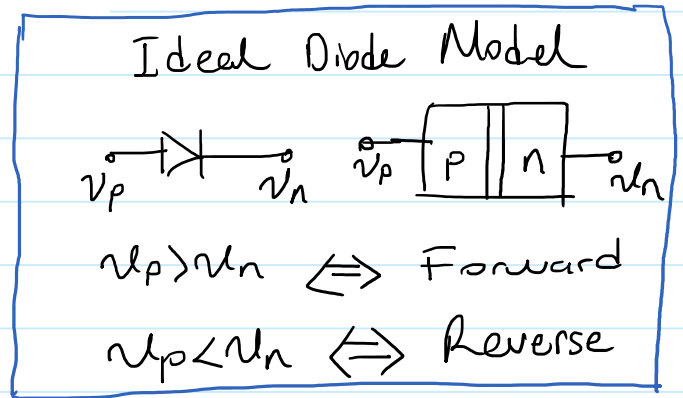

EBJ $V_B - V_E = V_p - V_n = 0.7 \Rightarrow \text{Forward}$

CBJ $V_B - V_C = V_p - V_n = 0.7 \Rightarrow \text{Forward}$
Saturation