

MIDTERM #2

Aug. 14, 2014

Total Time Allowed: 1.5 hours

1. Closed book exam.
2. You can use a calculator. NO cell phone or computer.
3. If you put down the wrong answer, partial credits will be given only if you show the correct steps.
4. Points will be taken off for answers without units.


Name: _____

Student ID: _____

Signature: _____

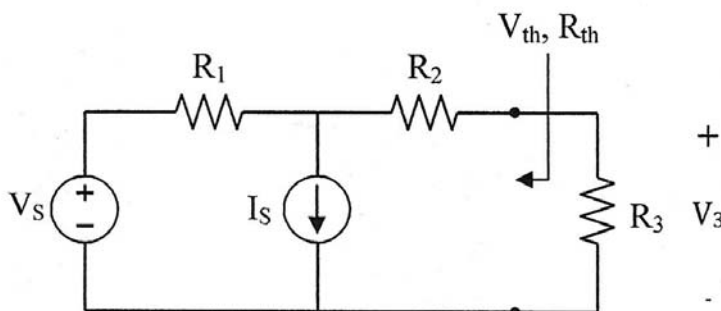QUESTIONS

1- For the circuit given below, calculate V_3 using Thevenin and Norton equivalent circuits.



Circuit Parameters



$$V_S = 18 \text{ V}$$

$$I_S = 6 \text{ mA}$$


$$R_1 = 2 \text{ k}\Omega$$

$$R_2 = 4 \text{ k}\Omega$$

$$R_3 = 6 \text{ k}\Omega$$

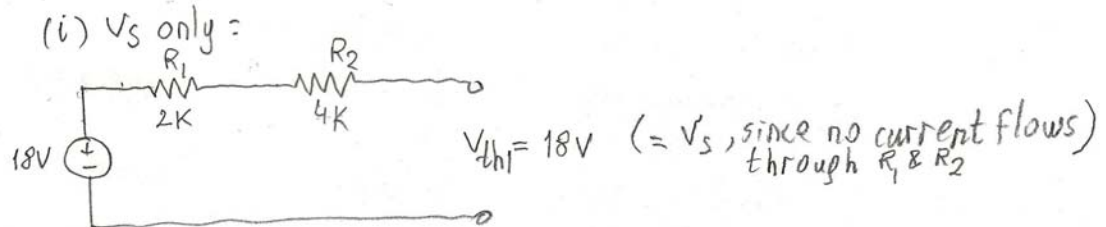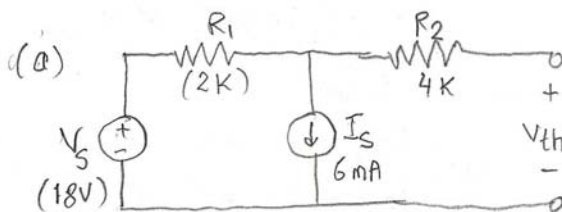

(ii) I_s only:

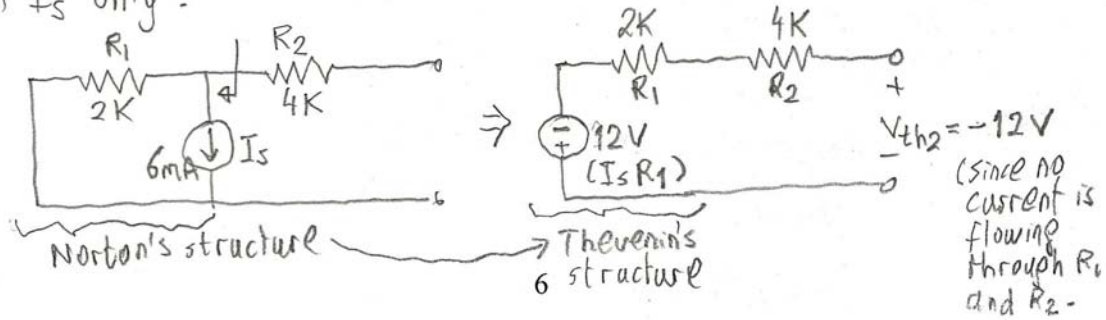


$$\text{Then } V_{th} = 18 - 12 = 6V$$

$$R_{th} = 2K + 4K = 6K$$



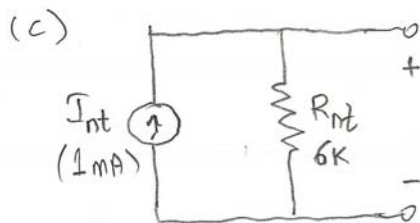
$$V_3 = \frac{R_3}{R_3 + R_{th}} \cdot V_{th} = \frac{6}{12} \cdot 6V = 3V$$



$$I_{nt} = \frac{V_{th}}{R_{th}} = \frac{6V}{6K} = 1mA$$

$$R_{nt} = R_{th} = 6K$$

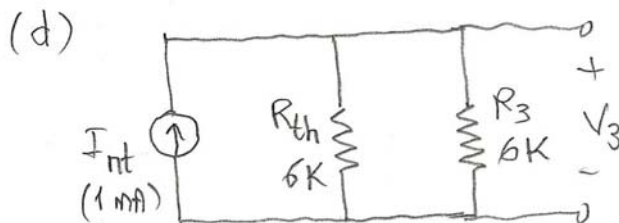


$$V_3 = I_{nt} (R_{th} \parallel R_3)$$

$$= (1mA)(6K \parallel 6K)$$

$$= 1mA \cdot 3K = 3V$$

(e) 18K, 120K, 150K, 180K

$R = 90K$?

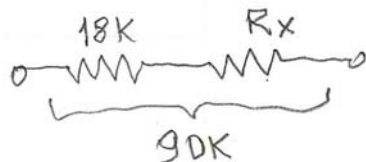


$$R_x = 90 - 18 = 72K$$

$$120K \parallel 150K = 66.67K$$

$$150K \parallel 180K = 81.82K$$

$$120K \parallel 180K = 72K$$

Then

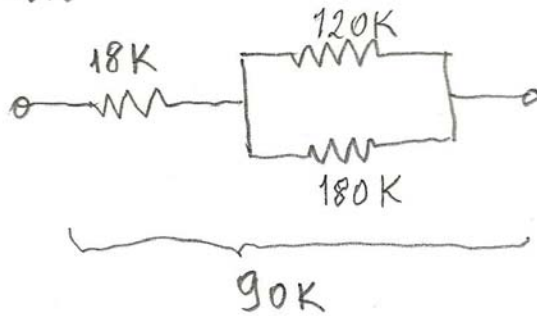


(18K), (120K), (150K), (180K)

2- The op-amp in the circuit is ideal.

a) What op-amp circuit configuration is this?

b) Find v_o in terms of v_s .

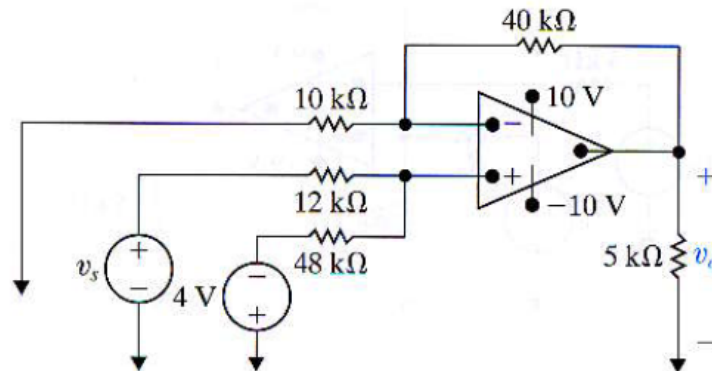c) Find the range of values for v_s such that v_o does not saturate and the op amp remains in its linear region of operation.



P 5.19 [a] This circuit is an example of a non-inverting summing amplifier.

[b] Write a KCL equation at v_p and solve for v_p in terms of v_s :

$$\frac{v_p - v_s}{12,000} + \frac{v_p + 4}{48,000} = 0$$

$$4v_p - 4v_s + v_p + 4 = 0 \quad \text{so} \quad v_p = 4v_s/5 - 4/5$$

Now write a KCL equation at v_n and solve for v_o :

$$\frac{v_n}{10,000} + \frac{v_n - v_o}{40,000} = 0 \quad \text{so} \quad v_o = 5v_n$$

Since we assume the op amp is ideal, $v_n = v_p$. Thus,


$$v_o = 5(4v_s/5 - 4/5) = 4v_s - 4$$

[c] $4v_s - 4 = 10 \quad \text{so} \quad v_s = 3.5 \text{ V}$


$$4v_s - 4 = -10 \quad \text{so} \quad v_s = -1.5 \text{ V}$$

Thus, $-1.5 \text{ V} \leq v_s \leq 3.5 \text{ V}$.

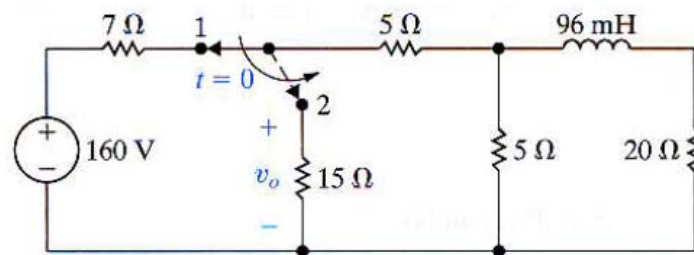3- The switch in the circuit has been in position 1 for a long time. At $t = 0$, the switch moves instantaneously to position 2. Find $v_o(t)$ for $t \geq 0^+$. Find the power and energy stored in the 20Ω resistor?




P 7.11 $t < 0$:

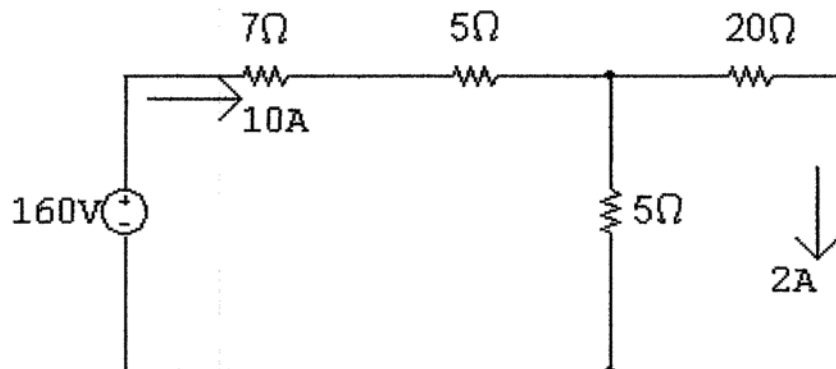

$$i_L(0^+) = 2 \text{ A}$$

$t > 0$:

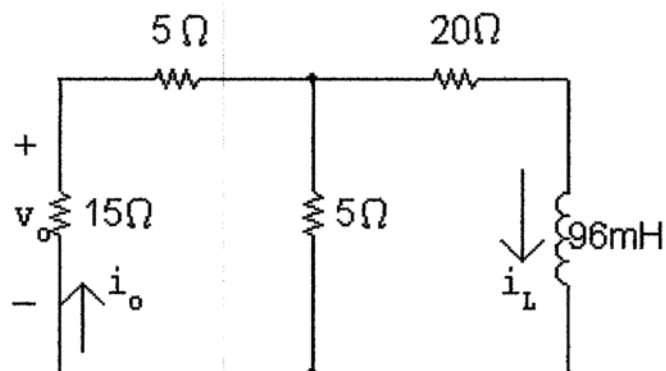

$$R_e = \frac{(20)(5)}{25} + 20 = 24 \Omega$$

$$\tau = \frac{L}{R_e} = \frac{96}{24} \times 10^{-3} = 4 \text{ ms}; \quad \frac{1}{\tau} = 250$$

$$\therefore i_L = 2e^{-250t} \text{ A}$$

$$\therefore i_o = \frac{5}{25}i_L = 0.4e^{-250t} \text{ A}$$

$$v_o = -15i_o = -6e^{-250t} \text{ V}, \quad t \geq 0^+$$

$$\text{P 7.12} \quad p_{20\Omega} = 20i_L^2 = 20(4)(e^{-250t})^2 = 80e^{-500t} \text{ W}$$

$$w_{20\Omega} = \int_0^\infty 80e^{-500t} dt = 80 \left. \frac{e^{-500t}}{-500} \right|_0^\infty = 160 \text{ mJ}$$