

# **Chapter 4**

## **Building the Processor**

### **Part A**

# Introduction


- CPU performance factors
  - Instruction count
    - Determined by ISA and compiler
  - CPI and Cycle time
    - Determined by CPU hardware

## What will be covered ?

- Building the ALU
- Two MIPS implementations
  - A simplified version (datapath and control)
  - A more realistic pipelined version (datapath and control)
- Advanced Issues
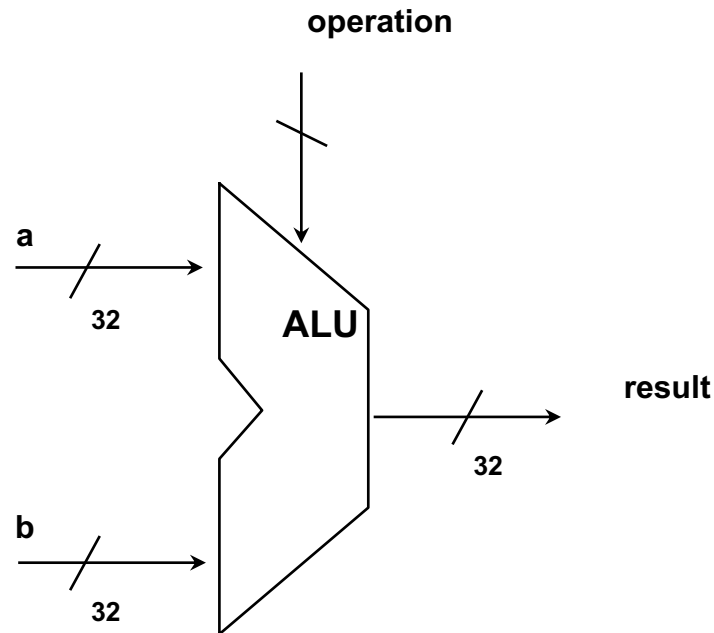
# Building the ALU (Chapter 4)


- Review Boolean Logic and build the ALU we'll need



- (Material from Appendix B - Reading Assignment)
 
# Review: The Multiplexor

- Selects one of the inputs to be the output, based on a control input




we call this a 2-input mux  
even though it has 3 inputs!

- Lets build our ALU using a MUX:
 
# Different Implementations



- Not easy to decide the “best” way to build something
  - *Don't want too many inputs to a single gate*
  - *Don't want to have to go through too many gates*
- Let's look at a 1-bit ALU for addition:



$$c_{out} = a b + a c_{in} + b c_{in}$$
$$sum = a \text{ xor } b \text{ xor } c_{in}$$

- How could we build a 1-bit ALU for add, and, and or?
- How could we build a 32-bit ALU?


# Building a 32 bit ALU

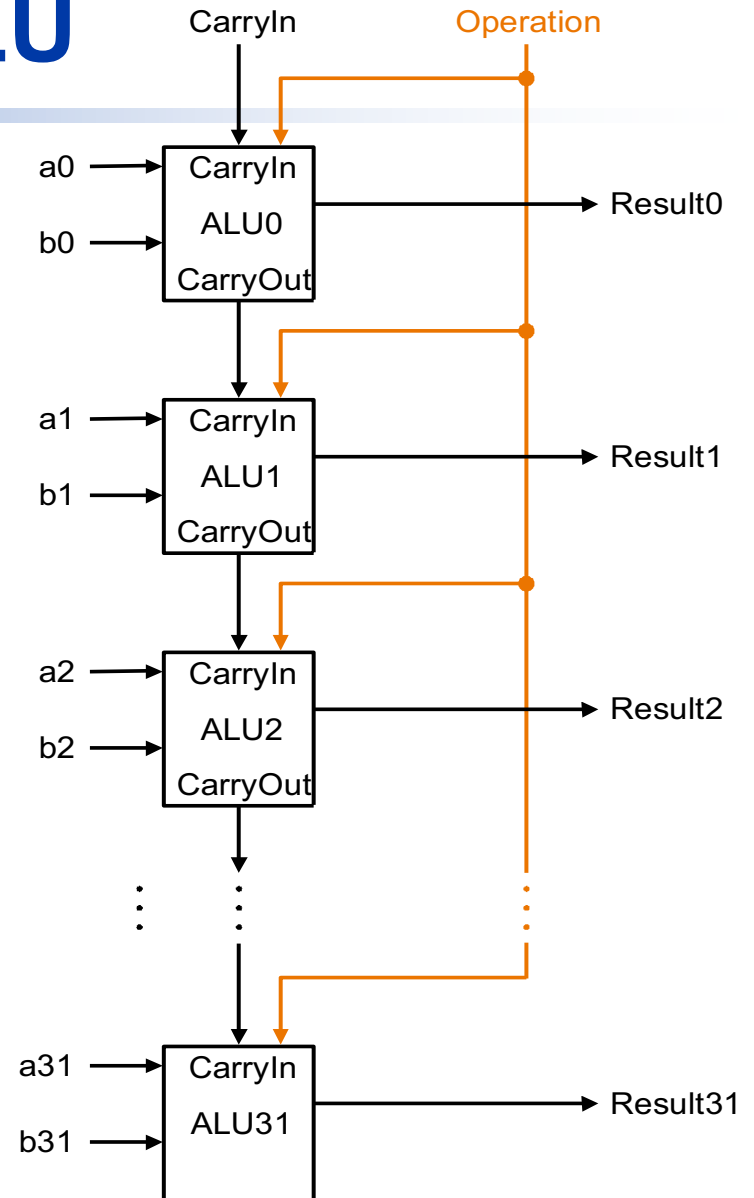 

# What about subtraction ( $a - b$ ) ?


- Two's complement approach: just negate b and add.
- How do we negate?

■ A very clever solution:

 
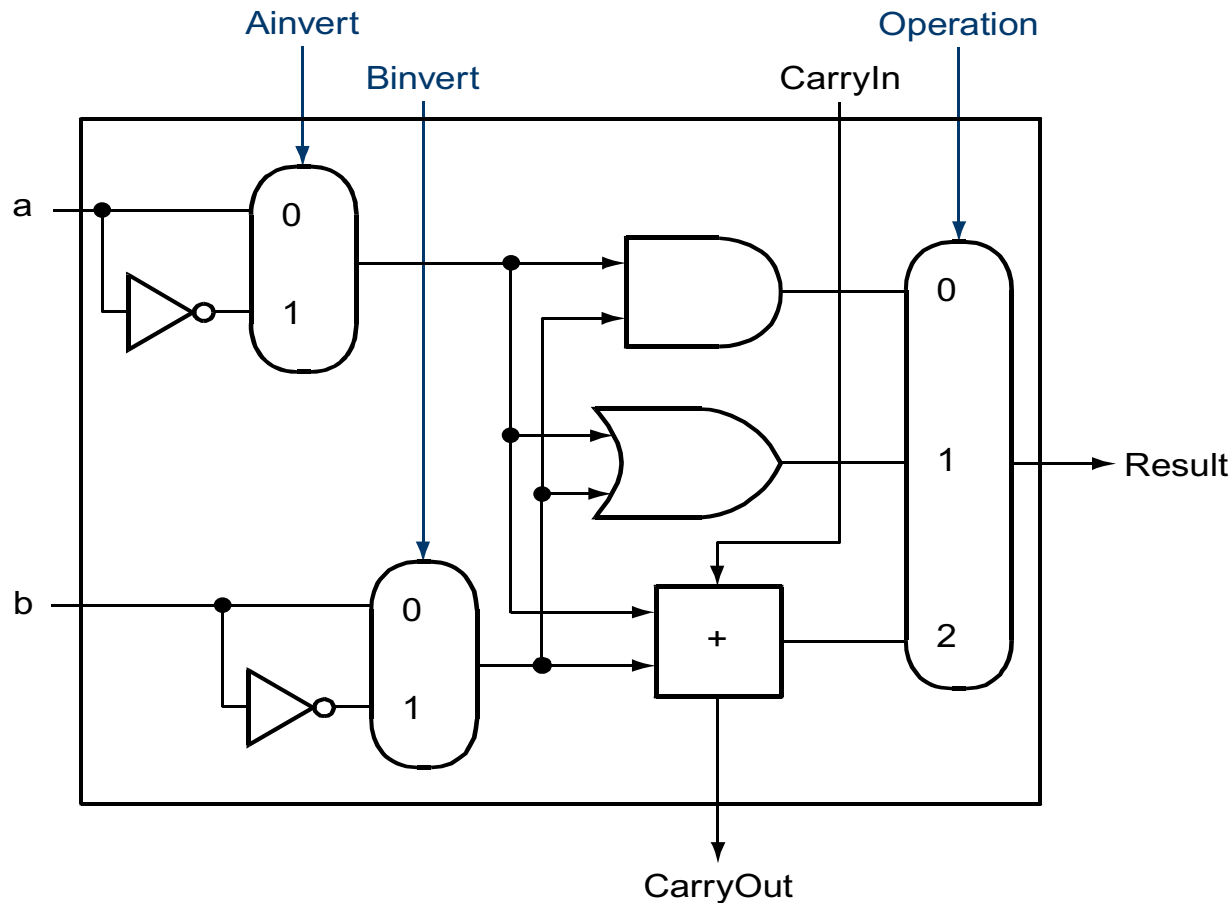
# Adding a NOR function

- Can also choose to invert a. How do we get “a NOR b” ?







# Tailoring the ALU to the MIPS

- Need to support the set-on-less-than instruction (slt)
  - remember: slt is an arithmetic instruction
  - produces a 1 if  $rs < rt$  and 0 otherwise
  - use subtraction:  $(a-b) < 0$  implies  $a < b$
- Need to support test for equality (beq \$t5, \$t6, \$t7)
  - use subtraction:  $(a-b) = 0$  implies  $a = b$

# Supporting slt

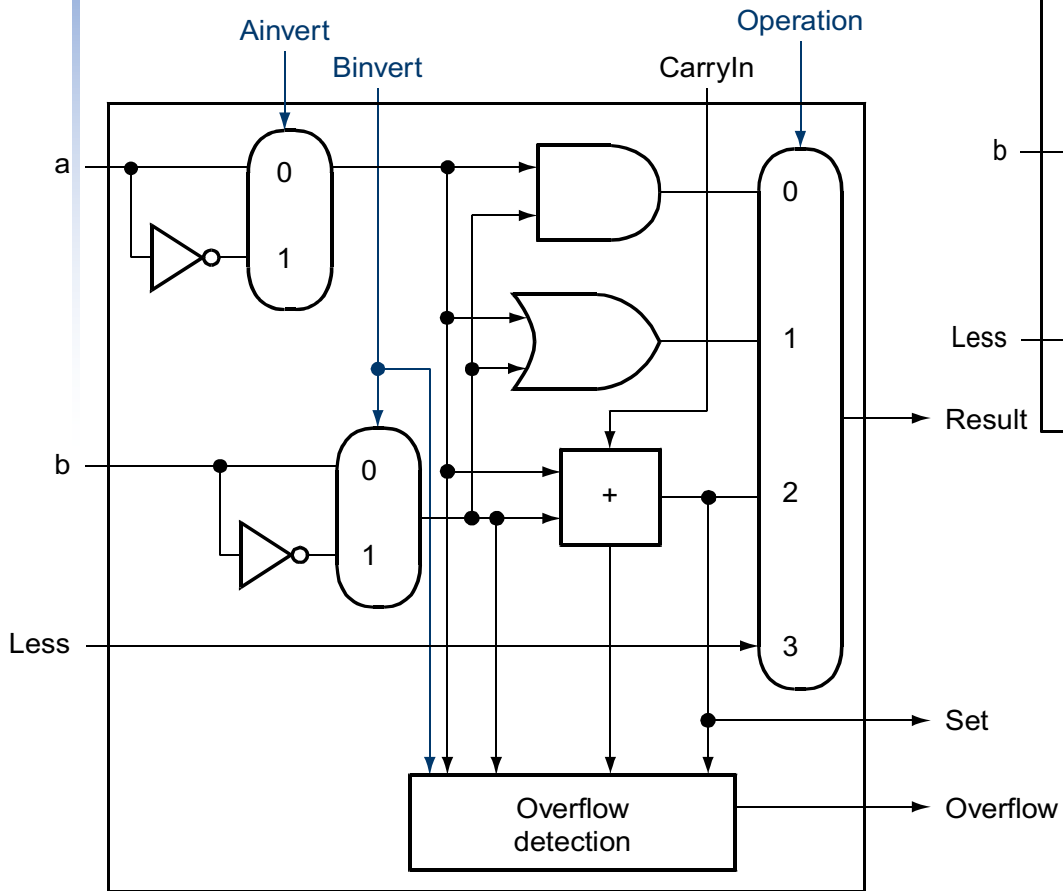


Use this ALU for most significant bit

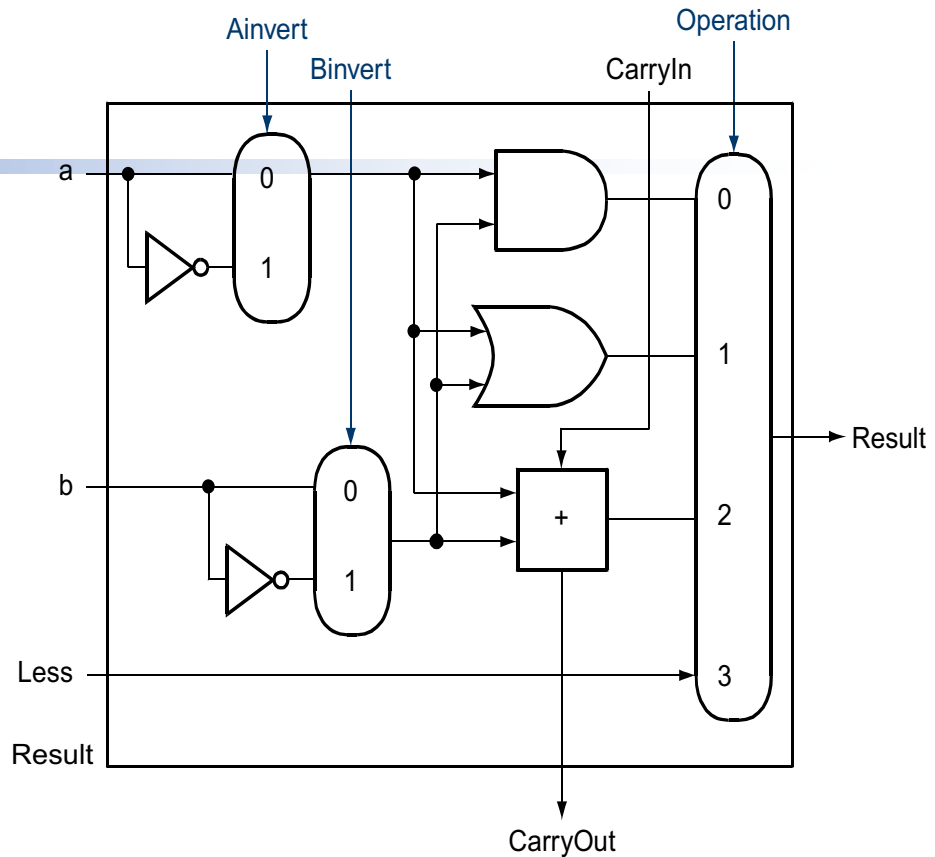

Use this ALU for all other bits

# slt

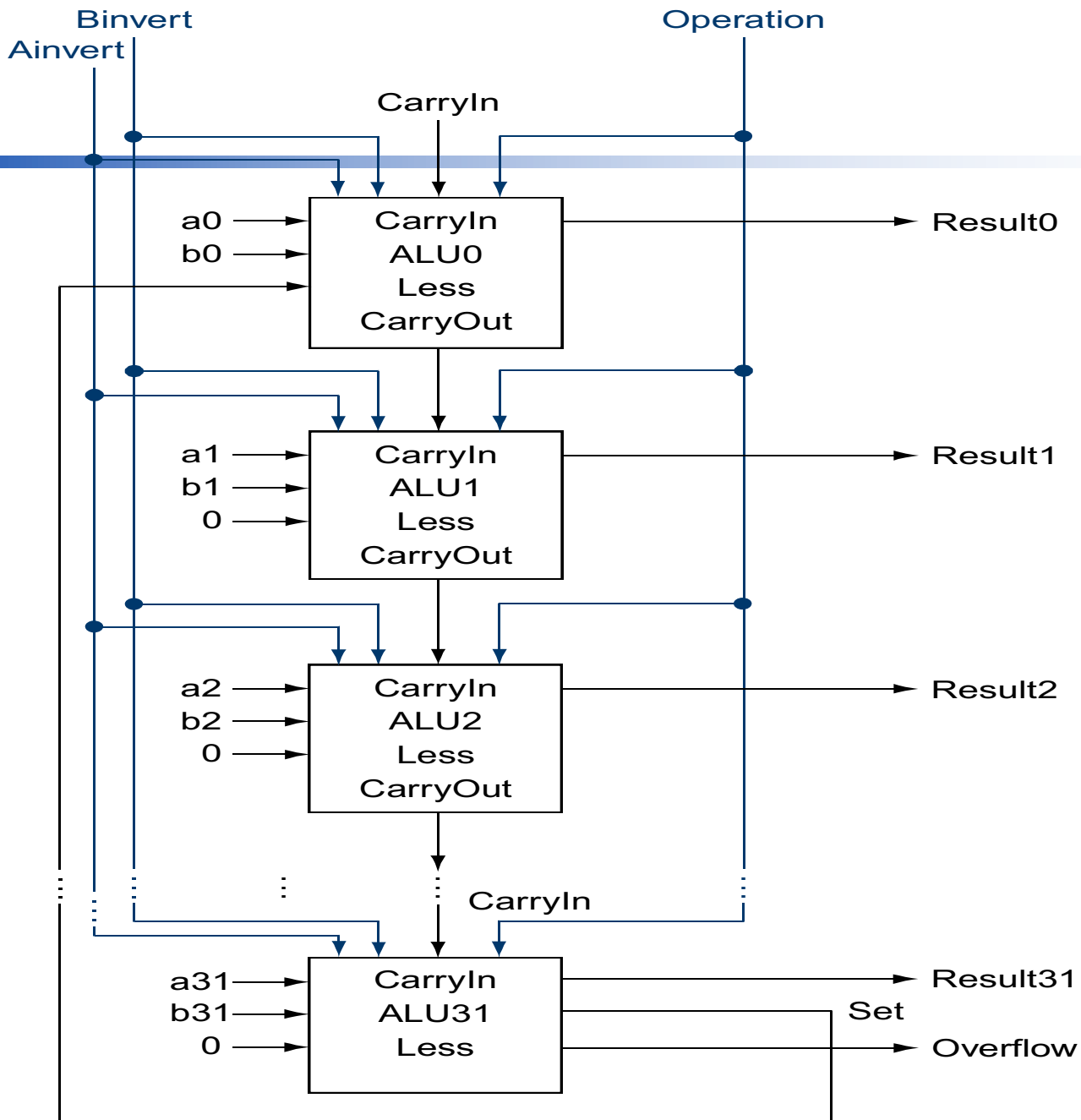

# Test for equality

- Notice control lines:

0000 = and

0001 = or


0010 = add

0110 = subtract

0111 = slt

1100 = NOR

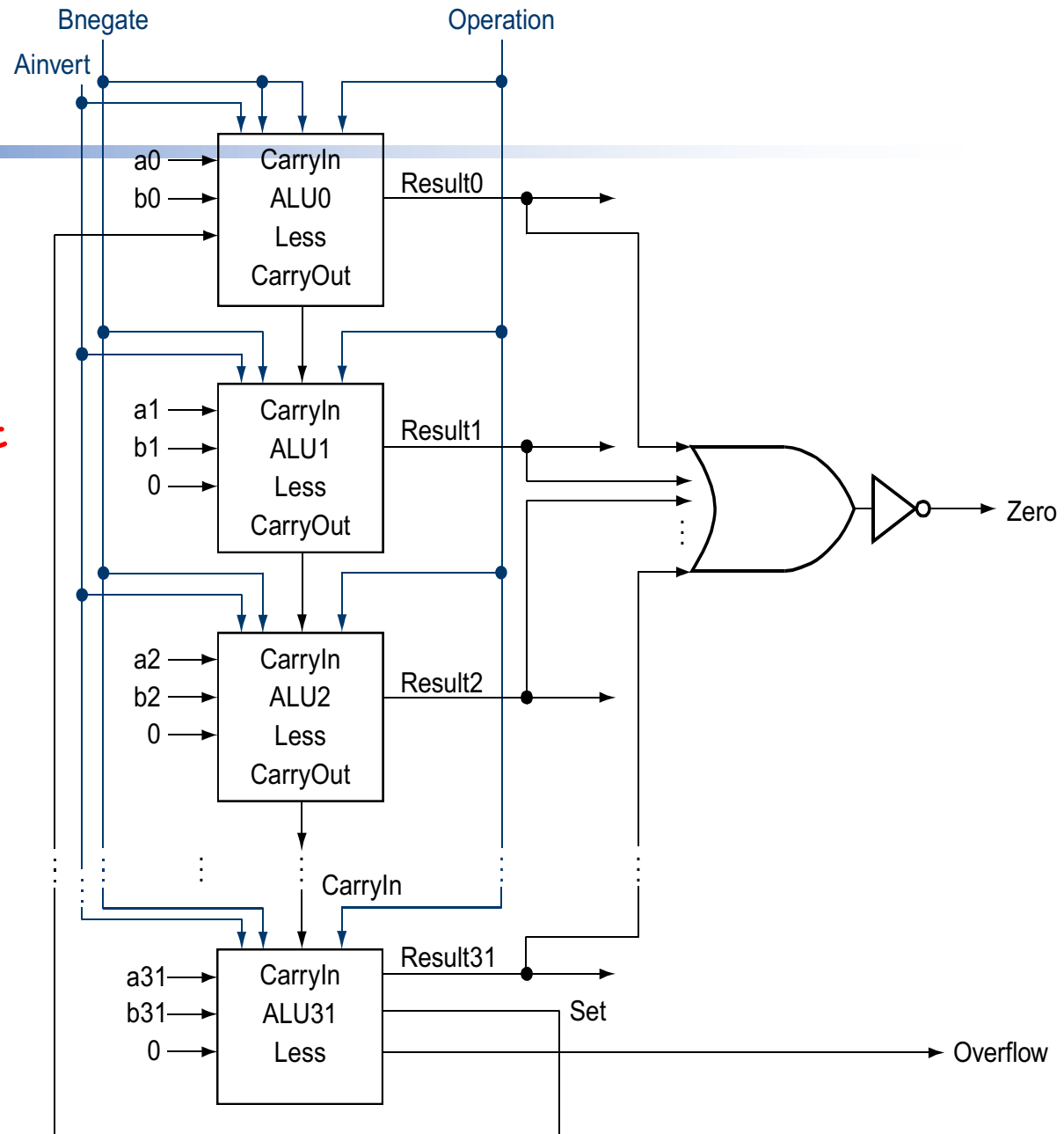•**Note:** zero is a 1 when  
the result is zero!



# Review on ALU Design

- **We can build an ALU to support the MIPS instruction set**
  - key idea: use multiplexor to select the output we want
  - we can efficiently perform subtraction using two's complement
  - we can replicate a 1-bit ALU to produce a 32-bit ALU
- **Important points about hardware**
  - all of the gates are always working
  - the speed of a gate is affected by # of inputs to the gate
  - the speed of a circuit is affected by the number of gates in series (on the “critical path” or the “deepest level of logic”)
- **Our primary focus:** comprehension, however,
  - Clever changes to organization can improve performance (similar to using better algorithms in software)


# The Processor: Datapath & Control

- We're ready to look at an implementation of the MIPS
- Simplified to contain only:
  - memory-reference instructions: **lw, sw**
  - arithmetic-logical instructions: **add, sub, and, or, slt**
  - control flow instructions: **beq, j**
- We will examine two MIPS implementations
  - A simplified version
  - A more realistic pipelined version

# Generic Implementation


- use PC to supply instruction address
- get the instruction from memory
- read registers
- use the instruction to decide exactly what to do
- Depending on instruction class, all instructions use the ALU after reading the registers
  - Arithmetic result
  - Memory address for load/store
  - Branch (comparison)
- Access data memory for load/store
- Arithmetic-logical: write data from ALU to register
- $PC \leftarrow \text{target address}$  **or**  $PC + 4$

# CPU Overview

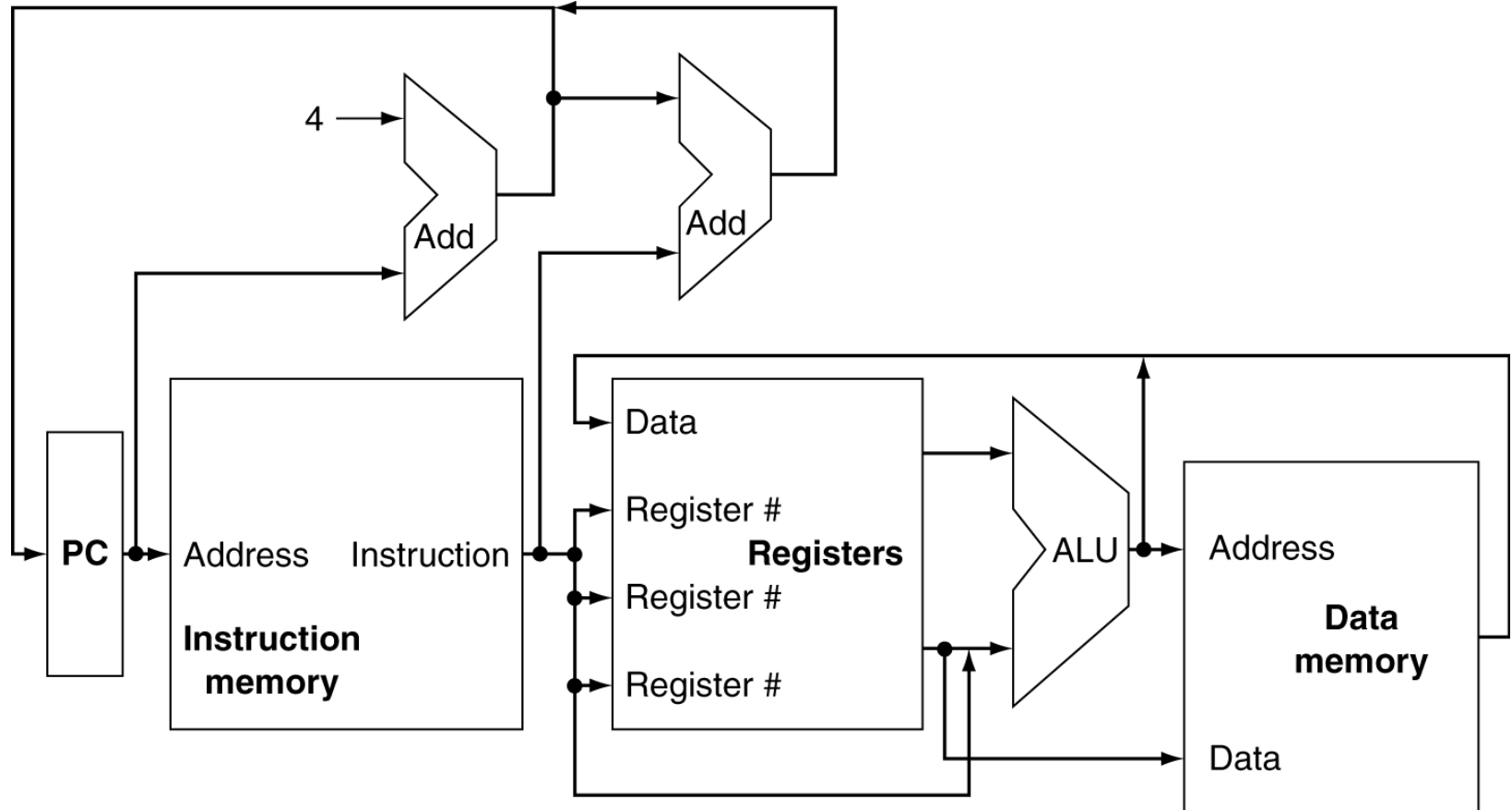




# Multiplexers

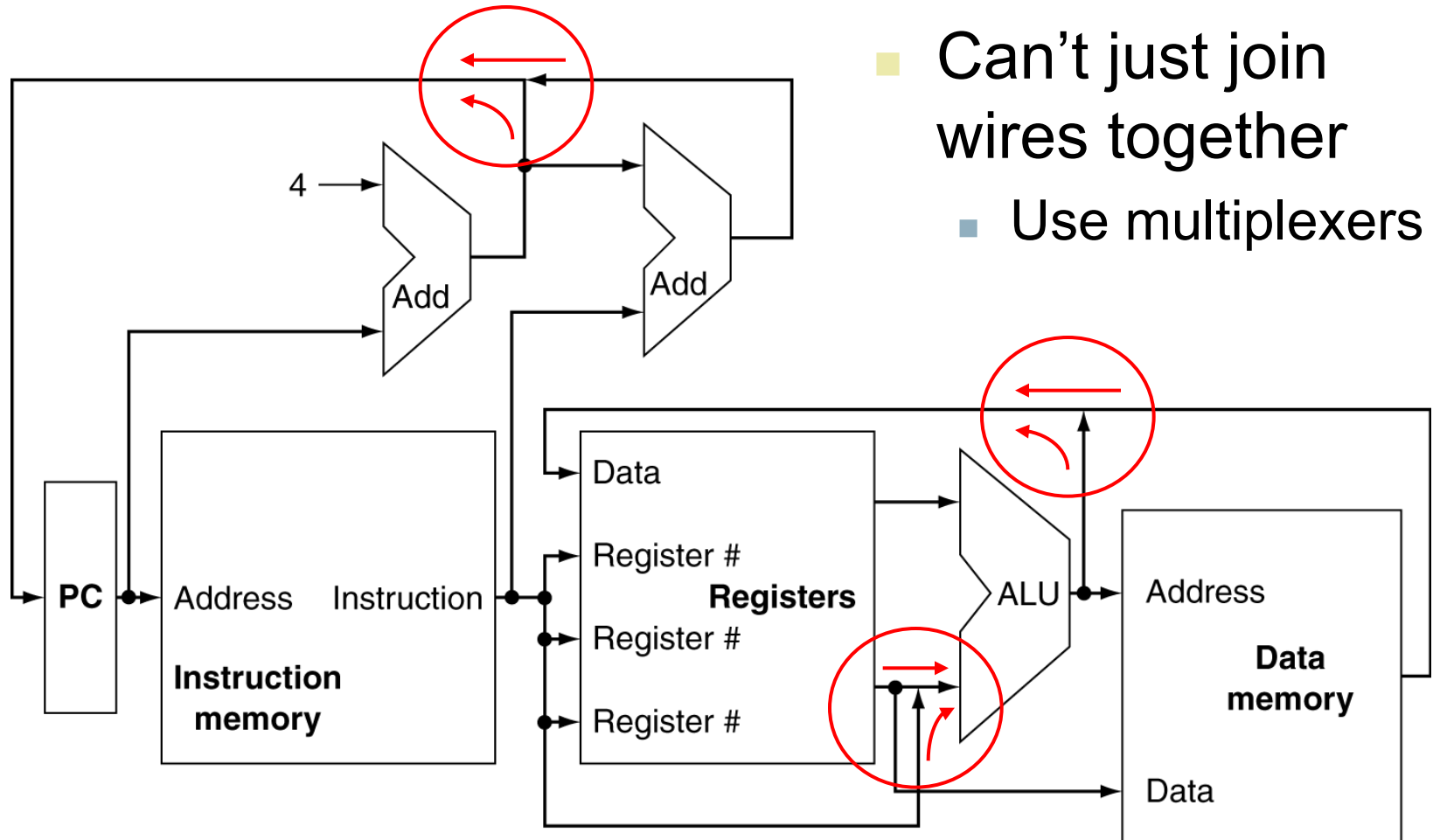

- Can't just join wires together
  - Use multiplexers

# Control

 


# Logic Design Basics

- Information encoded in binary
  - Low voltage = 0, High voltage = 1
  - One wire per bit
  - Multi-bit data encoded on multi-wire buses
- Combinational element
  - Operate on data
  - Output is a function of input
- State (sequential) elements
  - Store information

# Combinational Elements


- AND-gate

- $Y = A \& B$

 


- Multiplexer

- $Y = S ? I1 : I0$

 


- Adder

- $Y = A + B$

 


- Arithmetic/Logic Unit

- $Y = F(A, B)$

 


 
# Sequential Elements

- Unclocked vs. Clocked
- Clocks used in synchronous logic
  - when should an element that contains state be updated?



 
 
# Clocking Methodology

- A clocking methodology defines when signals can be read and written
- **Edge-triggered clocking** = all state changes occur on a clock edge
  - Positive edge-triggered (change on rising clock edge)
- All signals propagate from “State Element 1” through “combinational logic” and to “State Element 2” in the time of one clock cycle
- An edge-triggered methodology allows us to *read* the content of a register, *send* the value through some combinational logic, and *write* that register in the same clock cycle.



 
 
# Sequential Elements

- Register: stores data in a circuit
  - Uses a clock signal to determine when to update the stored value
  - Edge-triggered: update when Clk changes from 0 to 1


  
# Sequential Elements

- Register with write control
  - Only updates on clock edge when write control input is 1
  - Used when stored value is required later







# Latches and Flip-flops

- Output is equal to the stored value inside the element
- Change of state (value) is based on the clock
  - **Latches**: whenever the inputs change, and the clock is asserted (**assert = signal is logically high or true**)
  - **Flip-flop**: state changes only on a clock edge (edge-triggered methodology)
- Do not show a write control signal when a state element is written on every clock edge.
  - If it is not updated on every clock, than a separate control signal
  
# D-latch



- Two inputs:
  - the data value to be stored (D)
  - the clock signal (C) indicating when to read & store D
- Two outputs:
  - the value of the internal state (Q) and it's complement



Assume that output Q is initially false and D changes first.  
When C is asserted, latch is open  
→ Q assumes value of D input.

# D flip-flop

- Output changes only on the clock edge

 
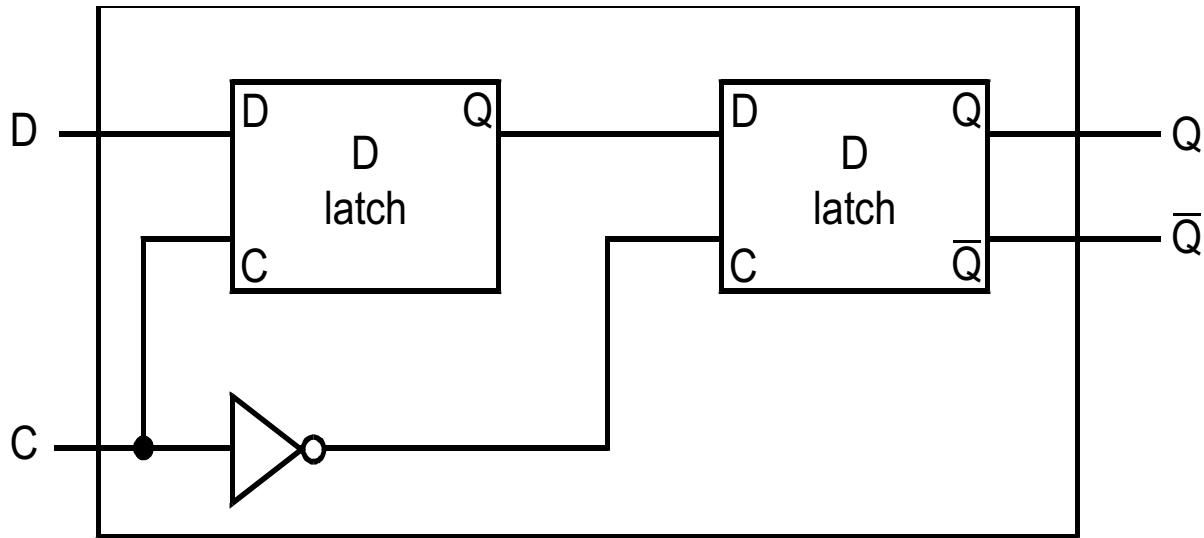


**\*\* Falling-edge trigger**

When C changes from asserted to deasserted, Q stores the value of D.


# Register File

- Built using D flip-flops

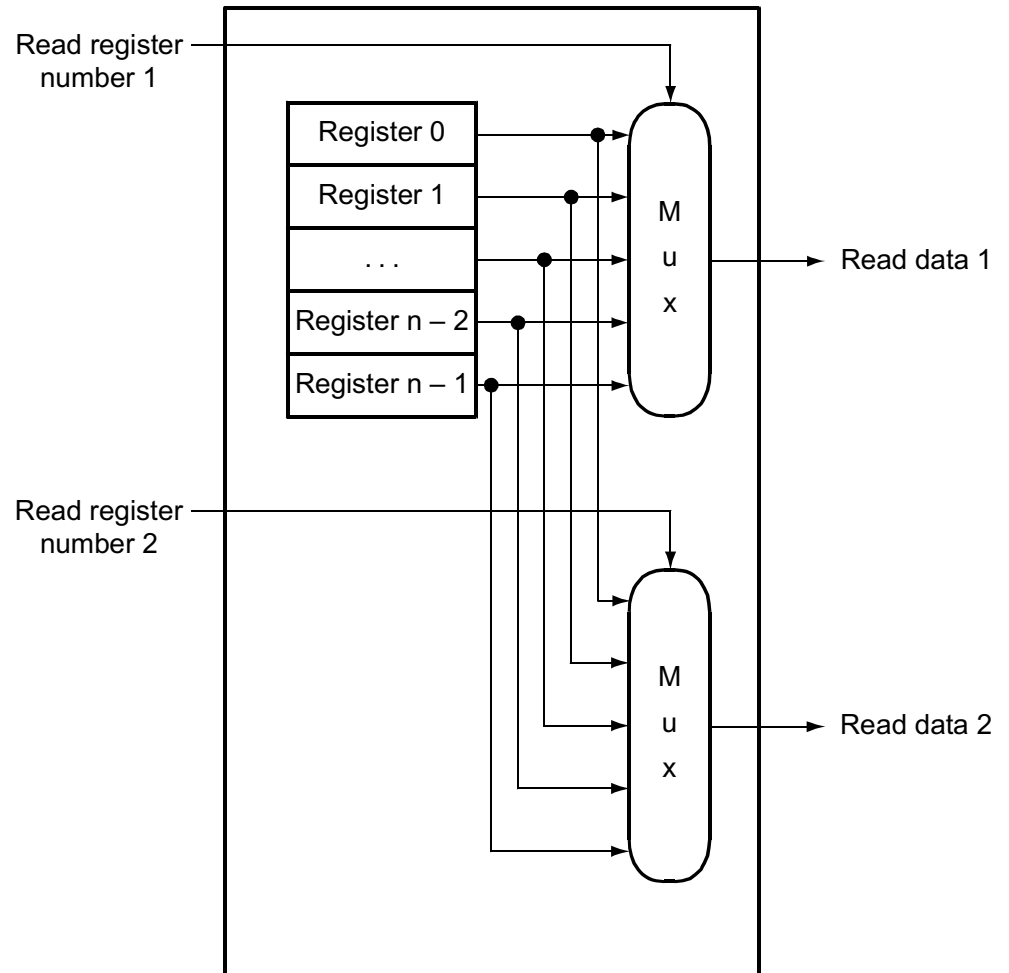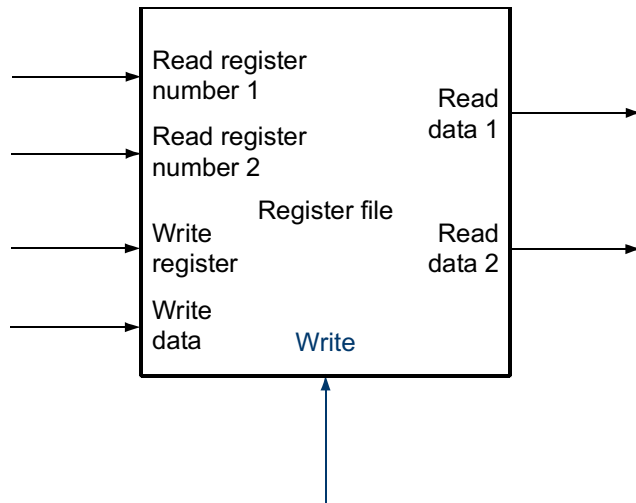


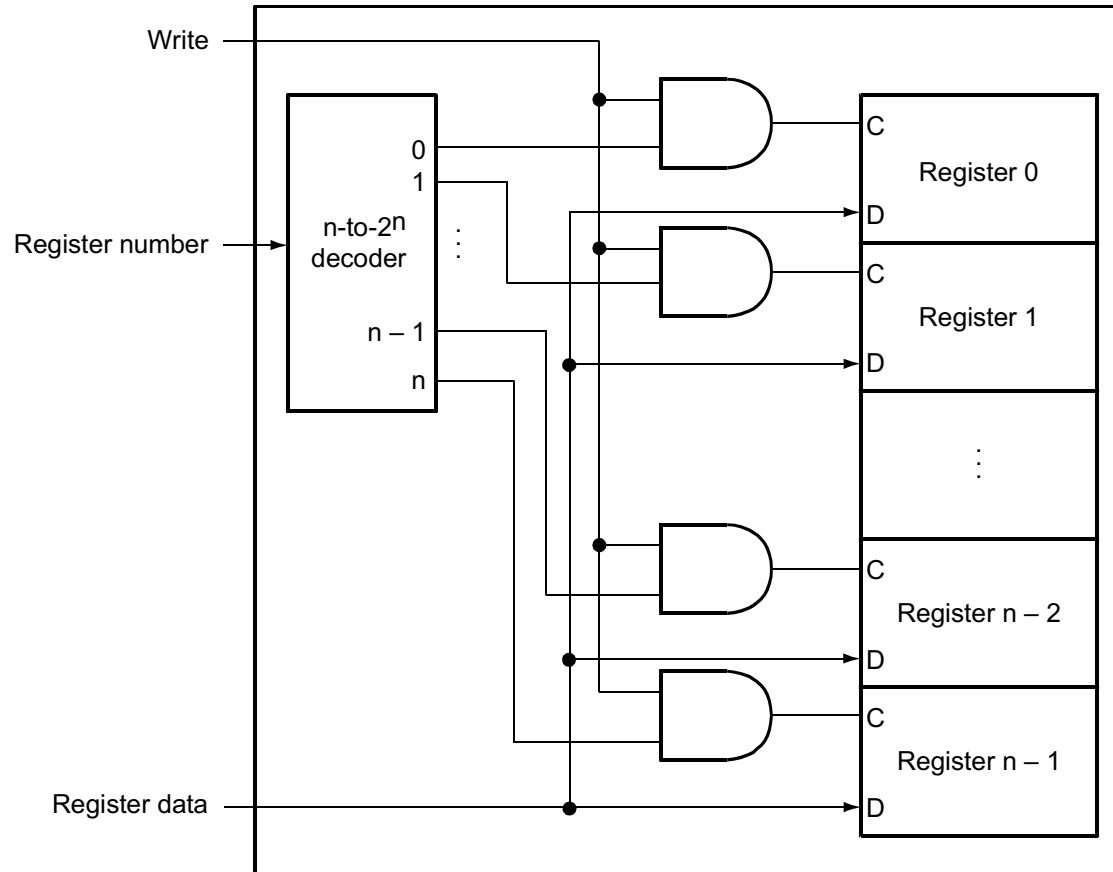
# Register File

- Note: we still use the real clock to determine when to write


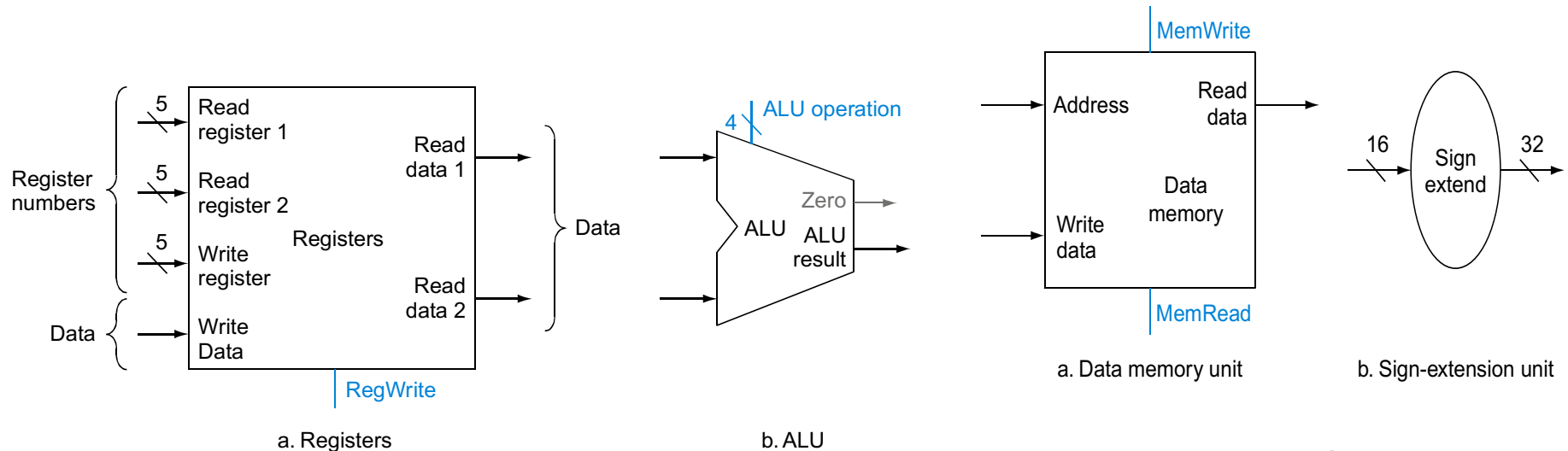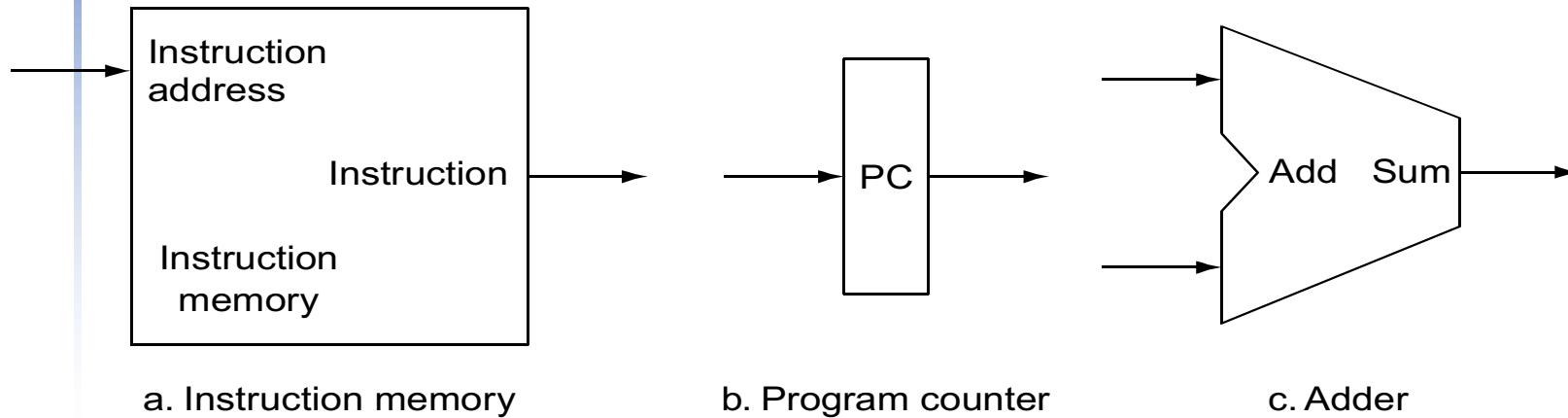
# Simple Implementation


- Include the functional units we need for each instruction



# Building a Datapath

- Datapath
  - Elements that process data and addresses in the CPU
    - Registers, ALUs, mux's, memories, ...
- We will build a MIPS datapath incrementally
  - Refining the overview design


# Instruction Fetch

 



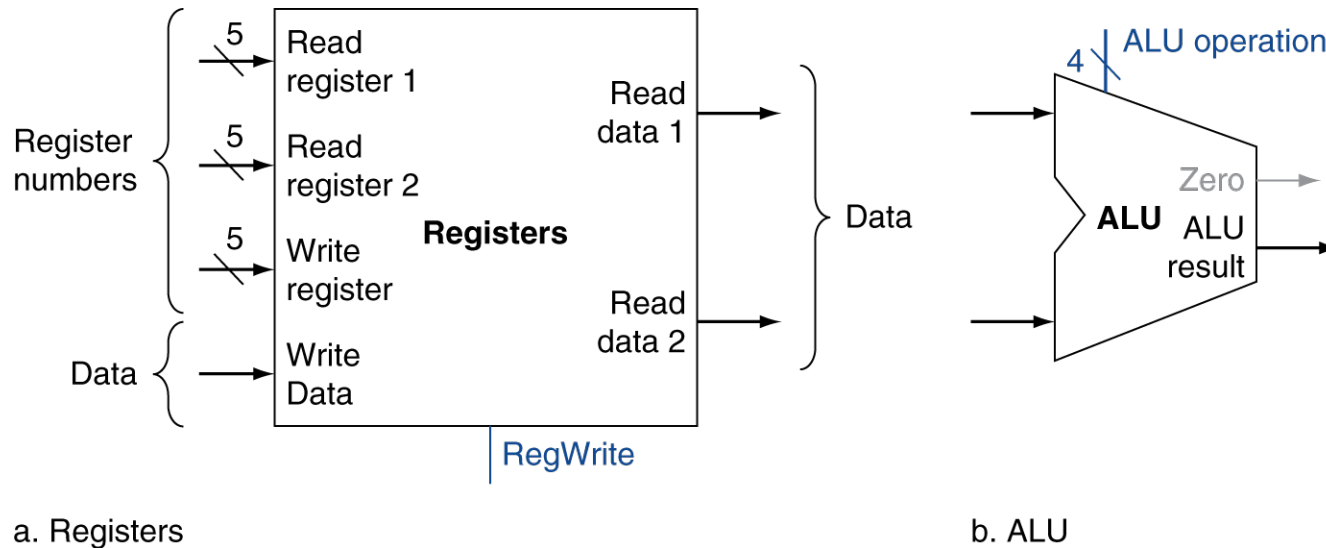
# R-Format Instructions

- Read two register operands
- Perform arithmetic/logical operation
- Write register result


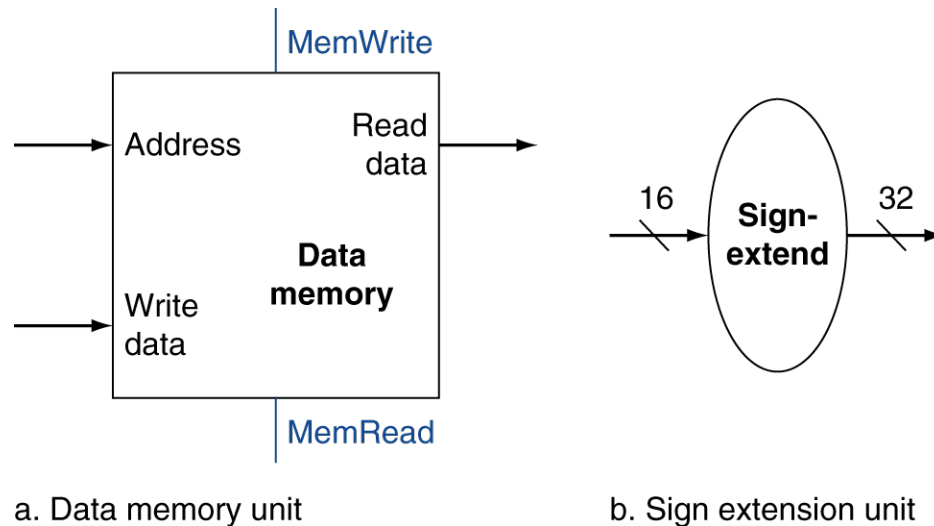
# Load/Store Instructions


- Read register operands
- Calculate address using 16-bit offset
  - Use ALU, but sign-extend offset
- Load: Read memory and update register
- Store: Write register value to memory



# Branch Instructions

- Read register operands
- Compare operands
  - Use ALU, subtract and check Zero output
- Calculate target address
  - Sign-extend displacement
  - Shift left 2 places (word displacement)
  - Add to PC + 4
    - Already calculated by instruction fetch


# Branch Instructions

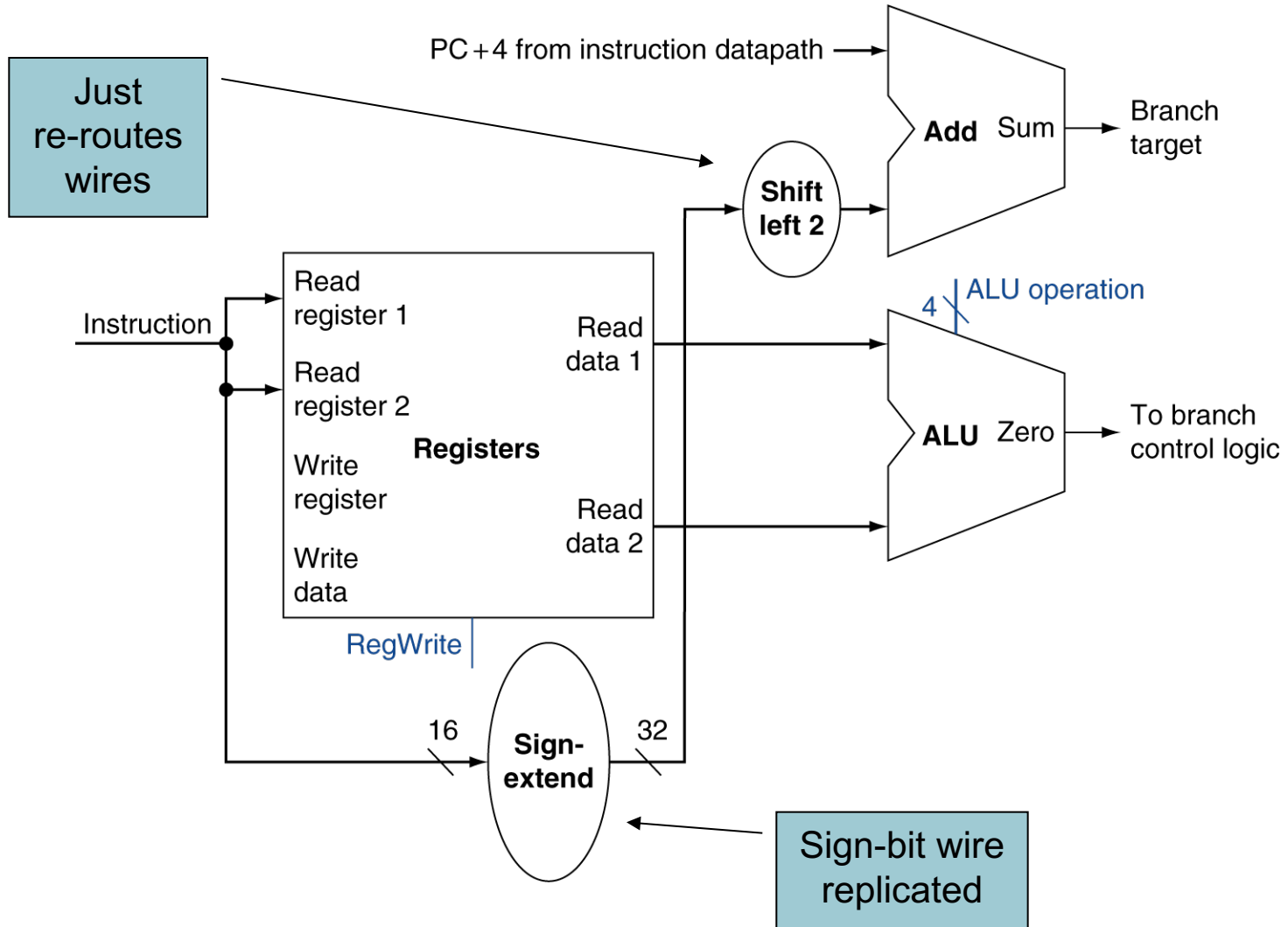

# Composing the Elements

- First-cut data path does an instruction in one clock cycle
  - Each datapath element can only do one function at a time
  - Hence, we need separate instruction and data memories
- Use multiplexers where alternate data sources are used for different instructions

# R-Type/Load/Store Datapath

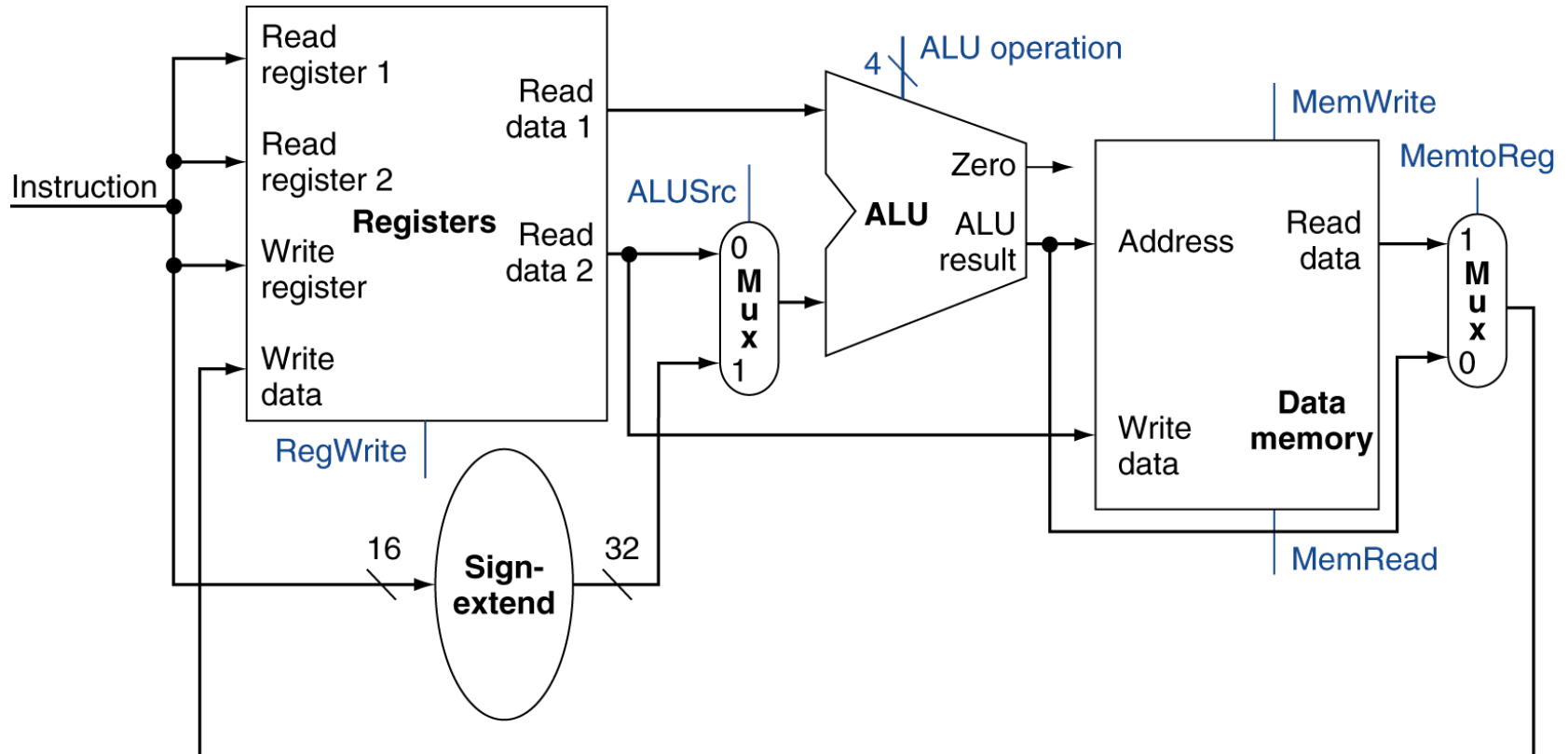

# Full Datapath

