

Reading

Adel S. Sedra and Kenneth C. Smith, **Microelectronic Circuits** 7th Edition, *Oxford University Press*, 2014.

- Chapter 4.1, 4.3, 4.4

Review



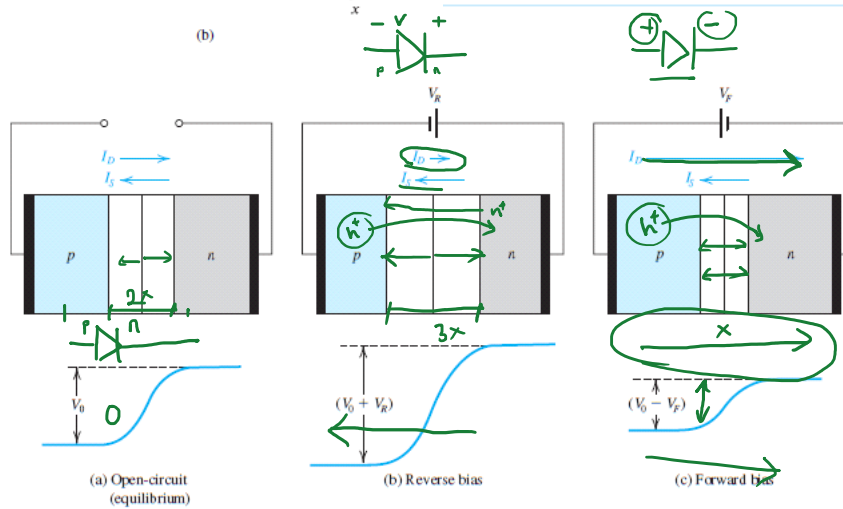
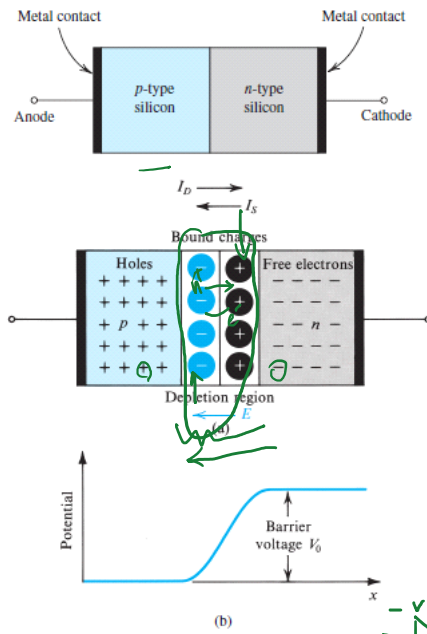


Figure 3.11 The pn junction in: (a) equilibrium; (b) reverse bias; (c) forward bias.

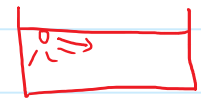


$$\sum_i S_i = \sum_i 10 e^- = 11$$


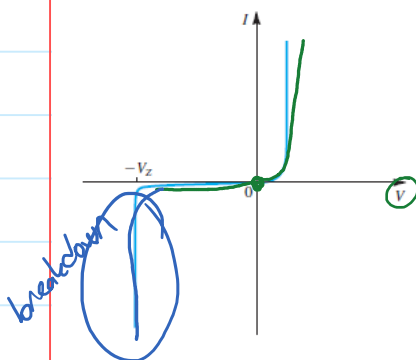


$$I = I_s (e^{V/V_T} - 1)$$



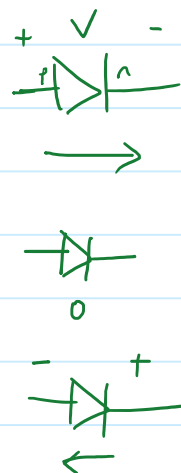
$$I_s = A q n_i^2 \left(\frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right)$$







Operating Regions of Diodes

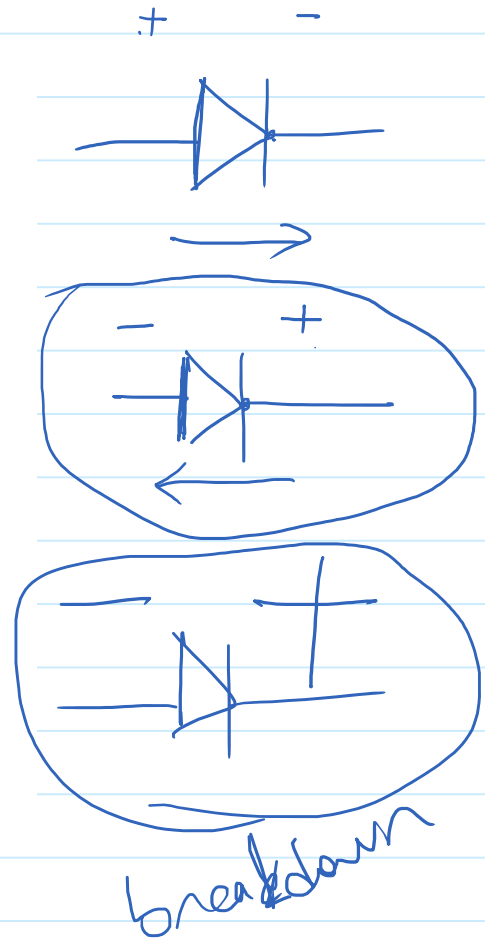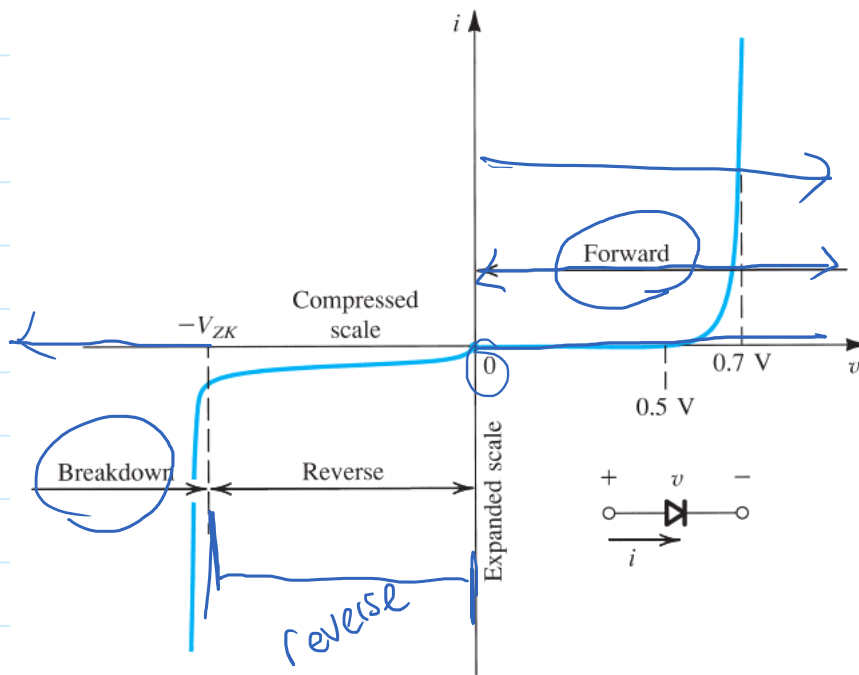

Ideal Diode

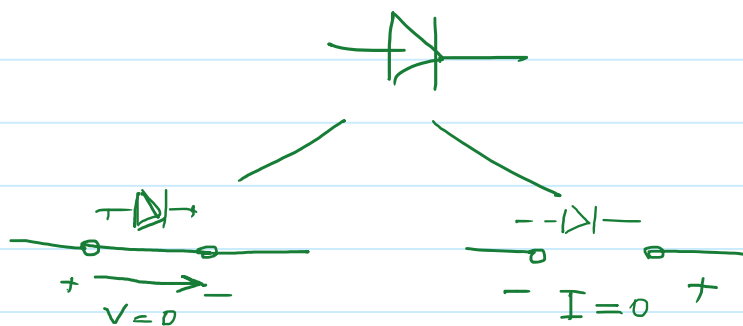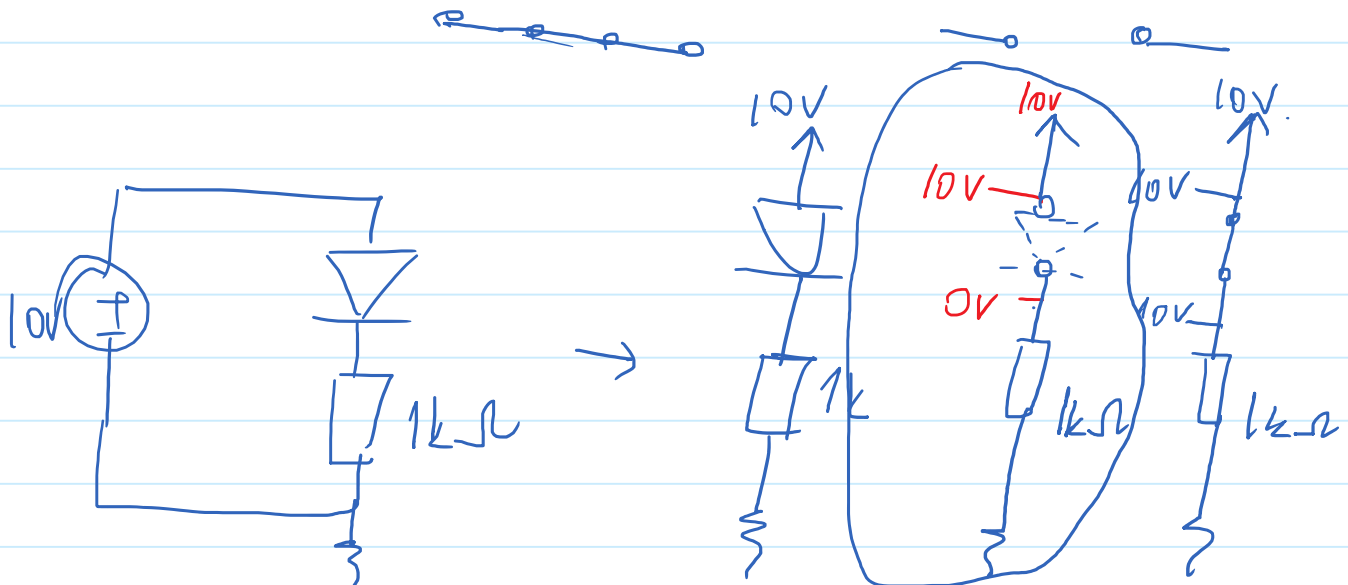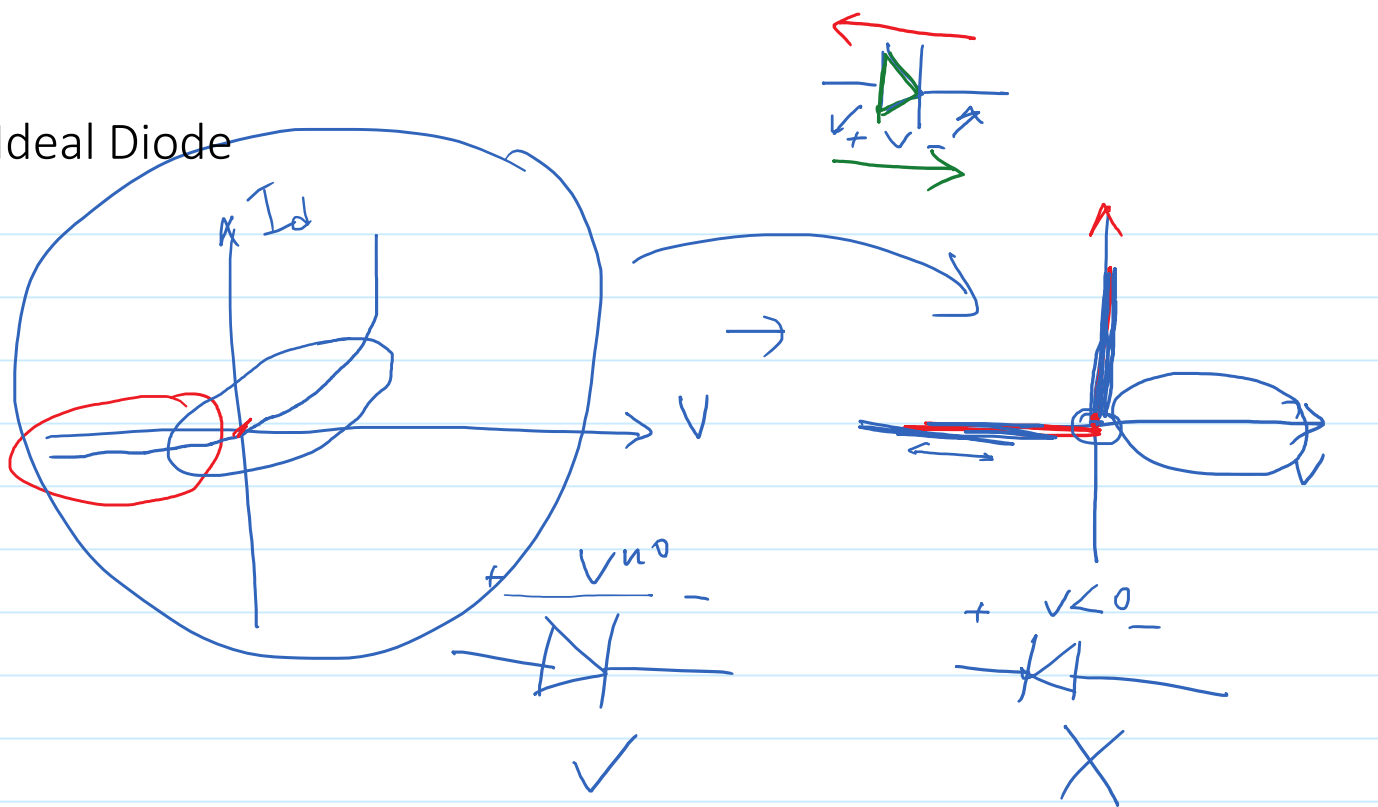

Example

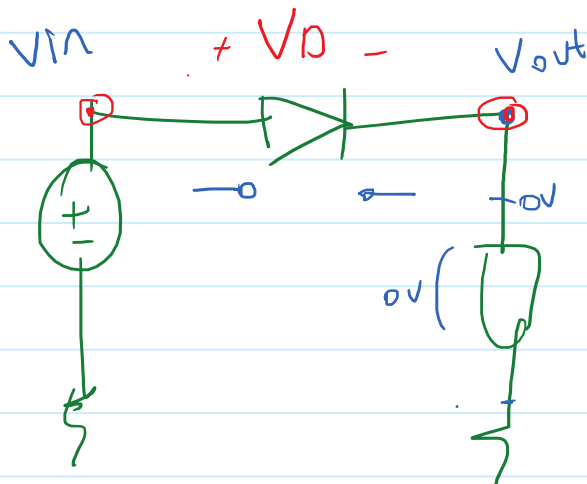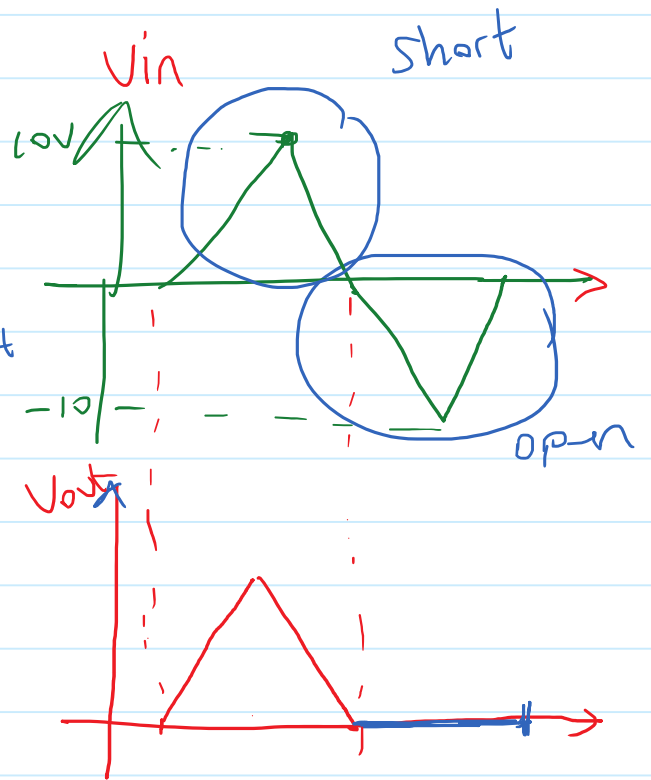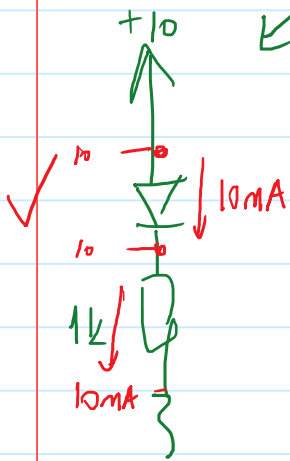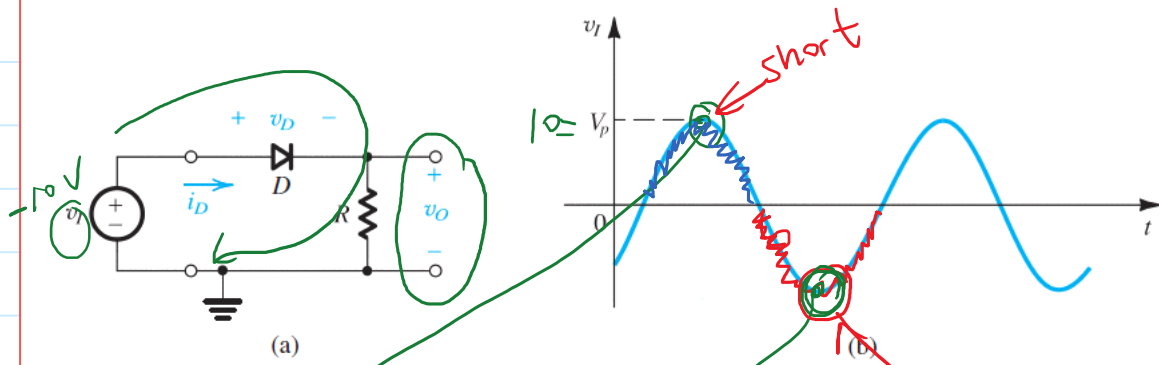

$$V_D = V_{in} - \underbrace{V_{out}}_0$$



Example

Figure 4.4(a) shows a circuit for charging a 12-V battery. If v_s is a sinusoid with 24-V peak amplitude, find the fraction of each cycle during which the diode conducts. Also, find the peak value of the diode current and the maximum reverse-bias voltage that appears across the diode.



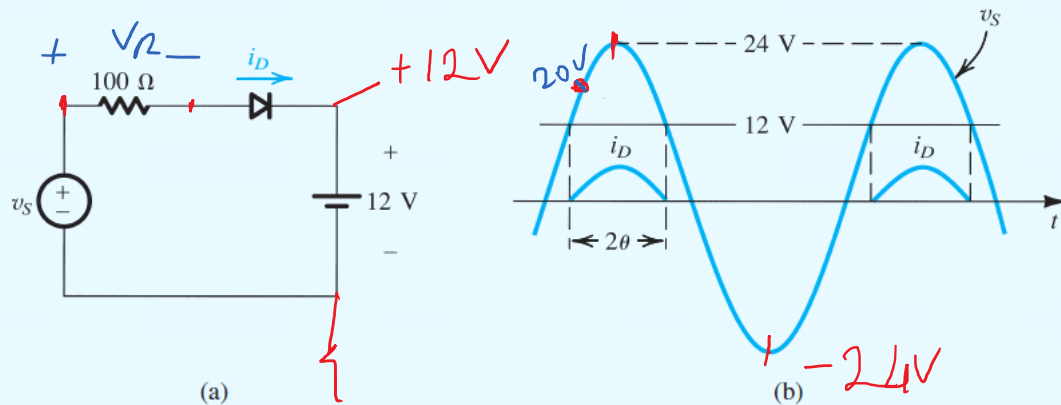
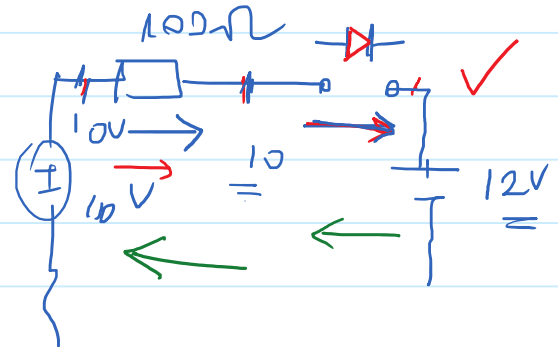


Figure 4.4 Circuit and waveforms for Example 4.1.

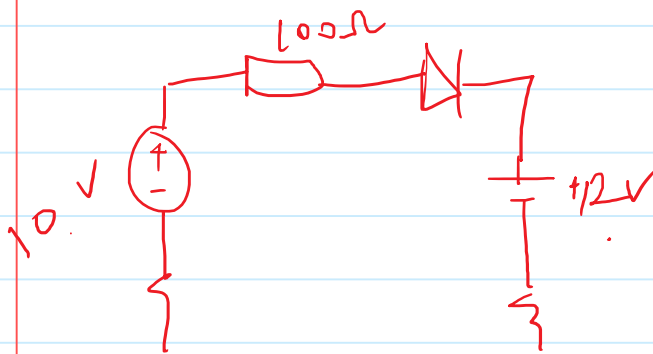
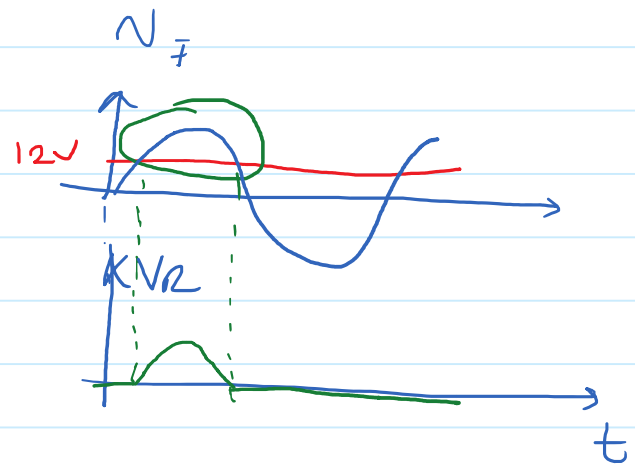
$$\begin{aligned} v_s = 24V &\rightarrow V_R = 12V \\ v_s = 20V &\rightarrow V_R = 8V \\ v_s = 12V &\rightarrow V_R = 0V \\ v_s = 10V &\rightarrow V_R = 0 \end{aligned}$$



Example

Assuming the diodes to be ideal, find the values of I and V in the circuits of Fig. 4.6.



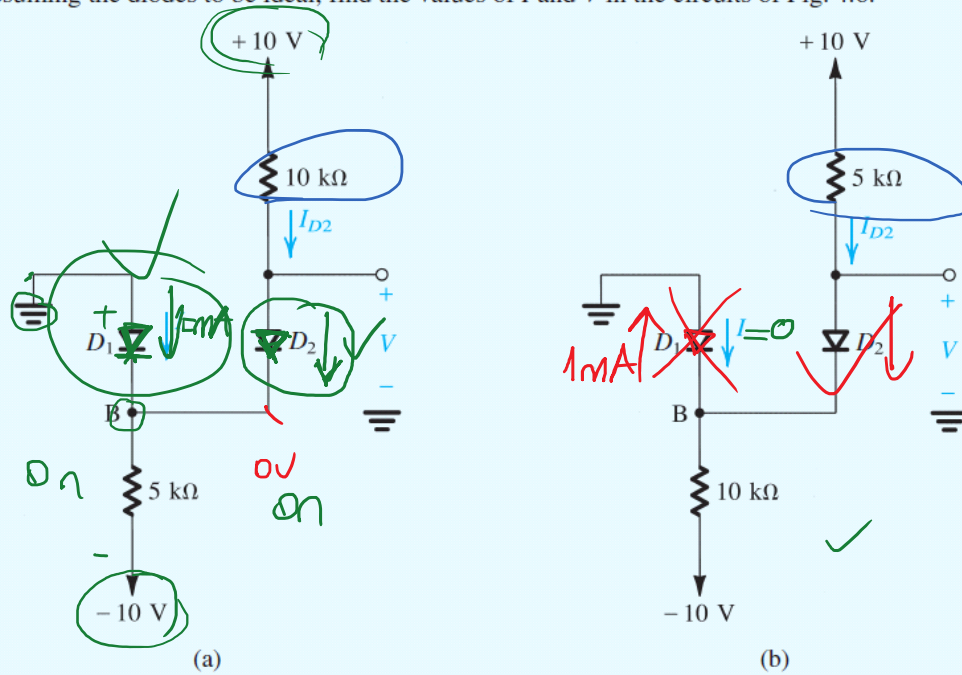
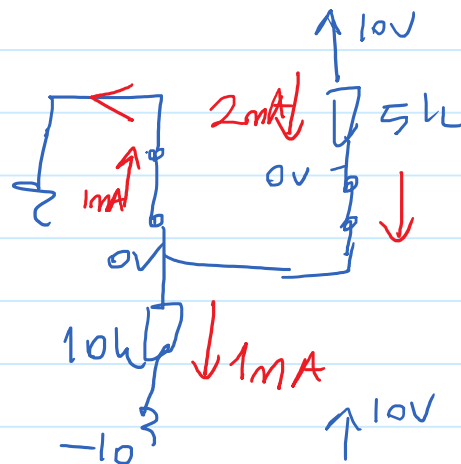


Figure 4.6 Circuits for Example 4.2.

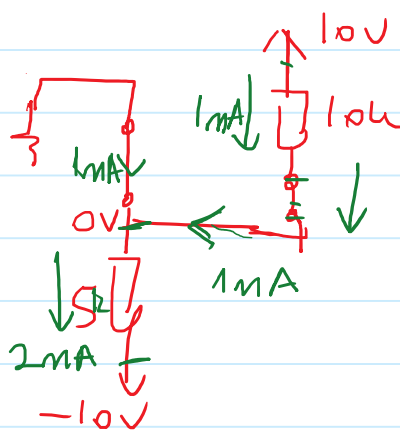

D_1	D_2
off	on
on	on

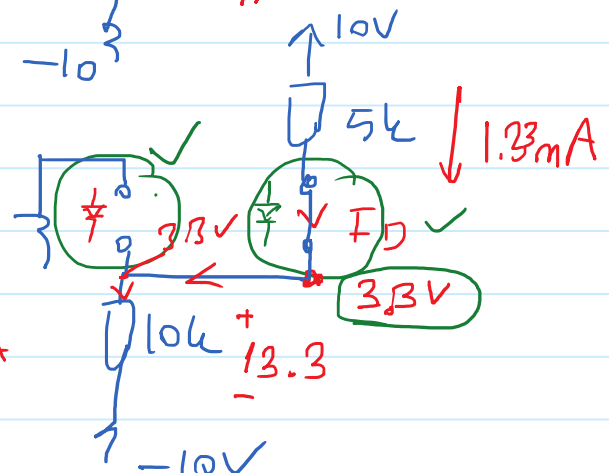
$$I_D = \frac{10 \times 10}{15k} \approx 1.3mA$$



Exponential Model

Constant Voltage Drop Model

Reverse Breakdown - Zener Diodes

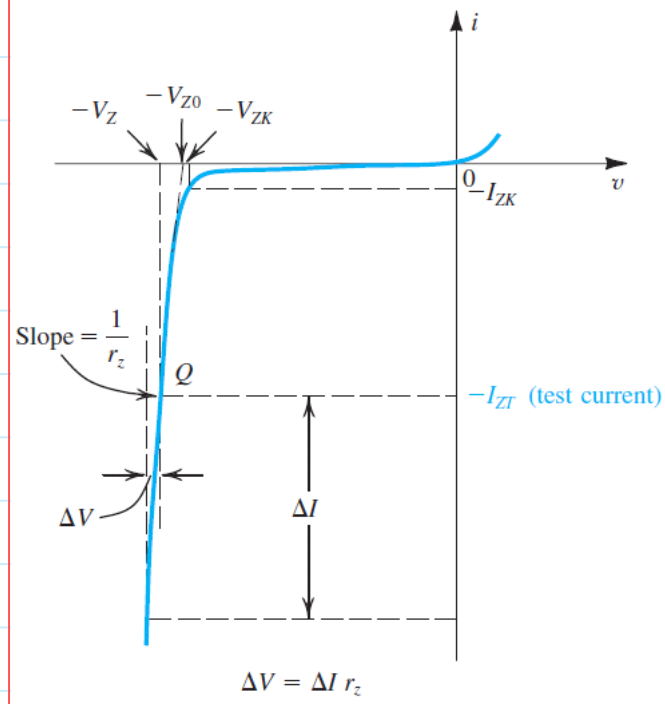

Example

Template