

Reading & Remarks

Charles K. Alexander and Matthew N. O. Sadiku, *Fundamentals of Electric Circuits 5th Edition*, McGrawHill, 2015.


- Chapter 3

Remarks:

- Homework - 1
- Quiz-1

Q1 - ✓
Q2 - ✓
Q3 - ✓


KCL

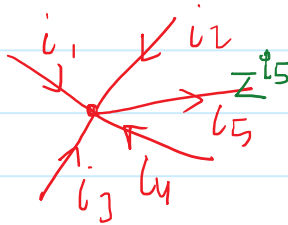

$$i_1 + i_2 + i_3 + i_4 = i_5$$



$$i_1 + i_2 + i_3 + i_4 - i_5 = 0$$

KCL

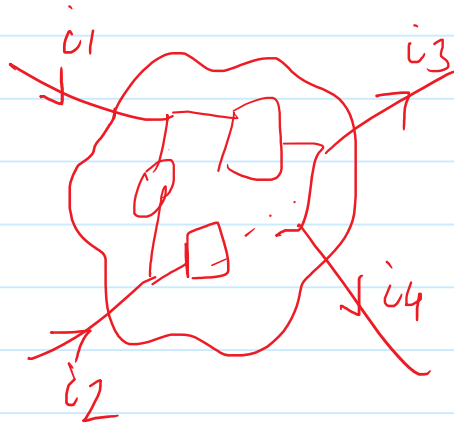


$$i_1 + i_2 = i_3 + i_4$$

KVL

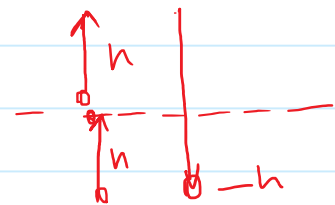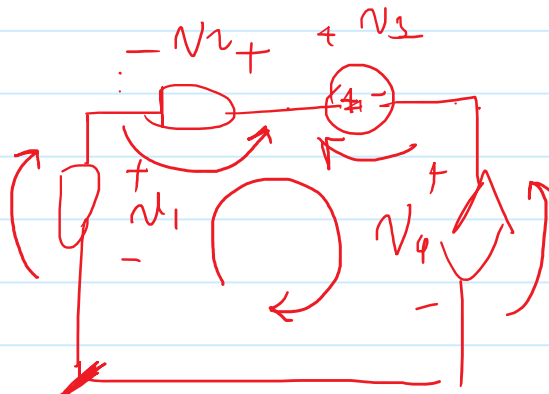

$$v_1 + v_2 - v_3 - v_4 = 0$$



Nodal Analysis

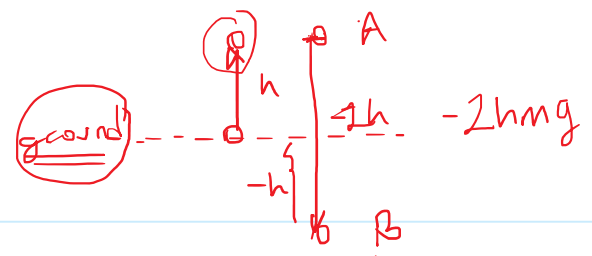

1. Select a node as the reference node. Assign v_1, v_2, \dots, v_{n-1} .
2. Apply KCL to each $n-1$ non-reference node. Use Ohm's law to express branch currents in terms of node voltages.
3. Solve the resulting simultaneous equations to obtain the unknown node voltages.

$$I_2 + \frac{v_1 - v_2}{R_2} = \frac{v_2 - 0}{R_3}$$

$n-1$

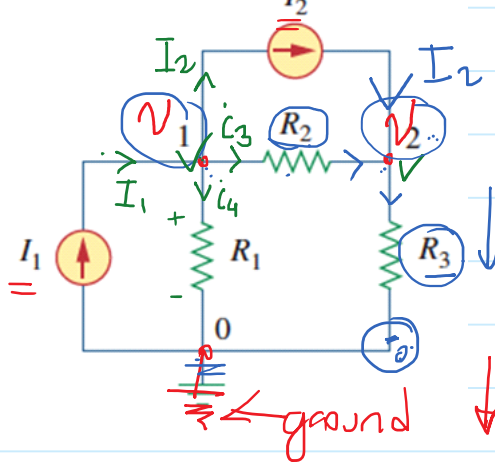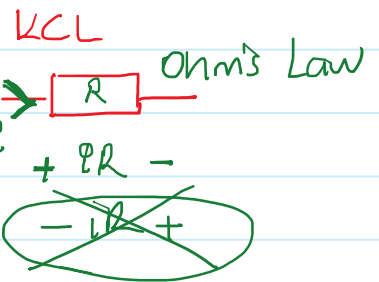

KCL @ node 1

$$I_1 = I_2 + i_3 + i_4$$

$$i_3 \cdot R_2 = v_1 - v_2 \Rightarrow i_3 = \frac{v_1 - v_2}{R_2}$$

$$i_4 \cdot R_1 = v_1 - 0 \Rightarrow i_4 = \frac{v_1}{R_1}$$


$$\textcircled{1} \quad I_1 = I_2 + \frac{v_1 - v_2}{R_2} + \frac{v_1}{R_1}$$

$$\textcircled{2} \quad I_2 + \frac{v_1 - v_2}{R_2} = \frac{v_2}{R_3}$$

$$I_1 = I_2 + \frac{v_1}{R_1} + \frac{v_1 - v_2}{R_2}$$

$$I_2 + \frac{v_1 - v_2}{R_2} = \frac{v_2}{R_3}$$

Example

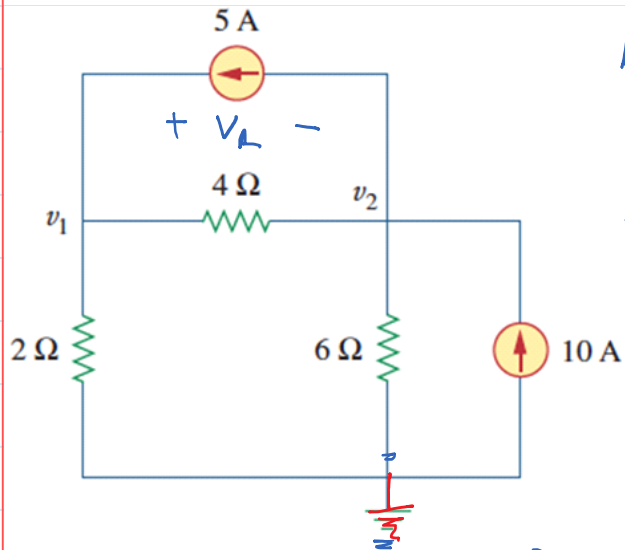

$$\text{KCL 1: } 5 + \frac{v_2 - v_1}{4} = \frac{v_1}{2}$$

(4) 4 2


$$\text{KCL 2: } 10 = 5 + \frac{v_2 - v_1}{4} + \frac{v_2}{6}$$

(12) 4 6 12

$$\textcircled{1} \quad 20 + v_2 - v_1 = 2v_1$$

$$\textcircled{2} \quad 60 = 3v_2 - 3v_1 + 2v_2$$
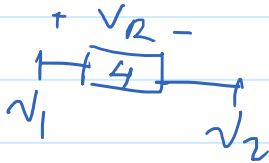
$$v_R = v_1 - v_2 = \frac{40}{3} - 20 = -\frac{20}{3}$$



$$-3v_1 + v_2 = -20$$


$$+3v_1 + 5v_2 = 60$$

$$-4v_2 = -80 \quad v_2 = 20V$$

$$v_1 = 40/3$$

$$v_1 = 40/3V, v_2 = 20V$$

Example

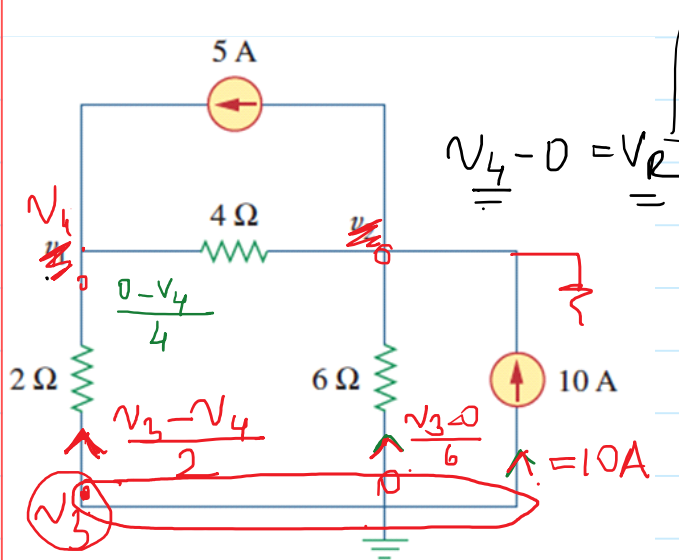

$$v_R = -20/3$$

$$v_4 - 0 = v_R$$

$$5 - \frac{v_4}{4} + \frac{v_3 - v_4}{2} = 0$$

(1) (2)

$$\rightarrow -10 + \frac{v_3}{6} + \frac{v_3 - v_4}{2} = 0$$

(3) (4)

$$\begin{aligned} -20 &= -3v_4 + 2v_3 \\ 60 &= +3v_4 - 4v_3 \end{aligned}$$

\Leftarrow

$$20 - v_4 + 2v_3 - 2v_4 = 0$$


$$60 + v_3 + 3v_3 - 3v_4 = 0$$

$$40 = -2v_3 \quad v_3 = -20$$

$$20 = +3v_4 + 40 \Rightarrow \boxed{-\frac{20}{3} = v_4}$$

$$V_1 = 40/3V, V_2 = 20V$$

Example

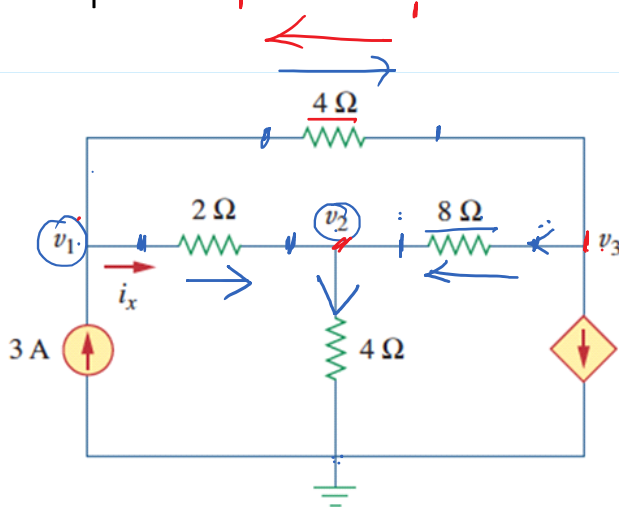

$$\frac{v_3 - v_1}{4} + \frac{v_3 - v_2}{8} = -2 \cdot \left(\frac{v_1 - v_2}{2} \right)$$

$$i_x = \frac{v_1 - v_2}{2}$$

$$\text{KCL: } 3 + \frac{v_3 - v_1}{4} = \frac{v_1 - v_2}{2} \quad (4)$$

$$\text{KCL: } \frac{v_1 - v_2}{2} + \frac{v_3 - v_2}{8} = \frac{v_2}{4} \quad (1)$$

$$\frac{v_1 - v_3}{4} + \frac{v_2 - v_3}{8} = \frac{v_1 - v_2}{2} \quad (2)$$

$$12 + v_3 - v_1 = 2v_1 - 2v_2$$

$$4v_1 - 4v_2 + v_3 - v_2 = 2v_2$$

$$2v_1 - 2v_3 + v_2 - v_3 = 8v_1 - 8v_2$$

$$Ax = b$$

$$x = A^{-1}b$$


$$v_1 = 4.8V, v_2 = 2.4V, v_3 = -2.4V$$

Mesh Analysis

KCL

KVL

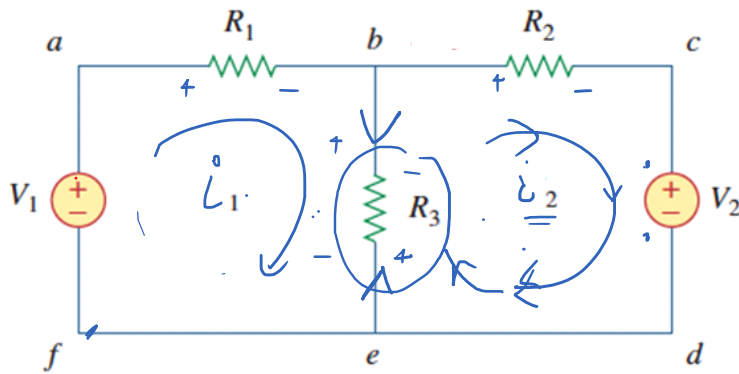- ✓ 1. Assign mesh currents i_1, i_2, \dots, i_n to the n meshes
2. Apply KVL to all meshes. Use Ohm's law to express voltages in terms of mesh currents
3. Solve the resulting n simultaneous equations to get mesh currents



$$0 = V_1 - i_1 R_1 - (i_1 - i_2) R_3$$

$$0 = -V_2 + (i_1 - i_2) R_3 - i_2 R_2$$


$$V_1 - i_1 R_1 - (i_1 - i_2) R_3 = 0$$

$$-V_2 - R_3(i_2 - i_1) - i_2 R_2 = 0$$

$$R_2 i_2 + V_2 + R_3(i_2 - i_1) = 0$$

$$-R_3 i_1 + (R_2 + R_3) i_2 = -V_2$$

Example

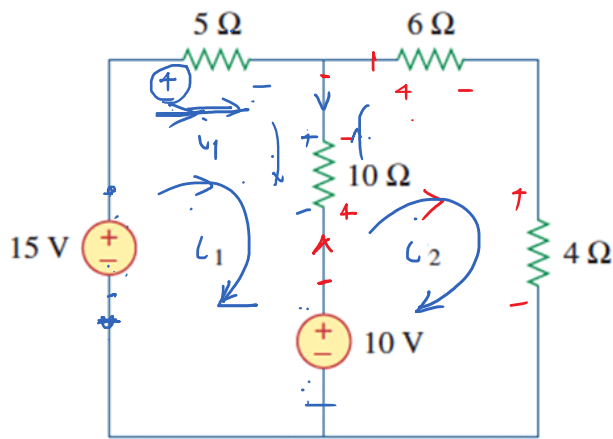

$$15 - 5i_1 - (i_1 - i_2)10 - 10 = 0$$

$$10V - 10(i_2 - i_1) - 6i_2 - 4i_2 = 0$$


$$\begin{aligned} 2/ \quad 5 &= 15i_1 - 10i_2 \\ 10 &= -10i_1 + 20i_2 \end{aligned}$$

$$20 = 20i_1 \Rightarrow i_1 = 1A$$

$$5 = 15 - 10i_2 \Rightarrow i_2 = 1A$$

$$i_1 = 1A \quad i_2 = 1A$$

Example

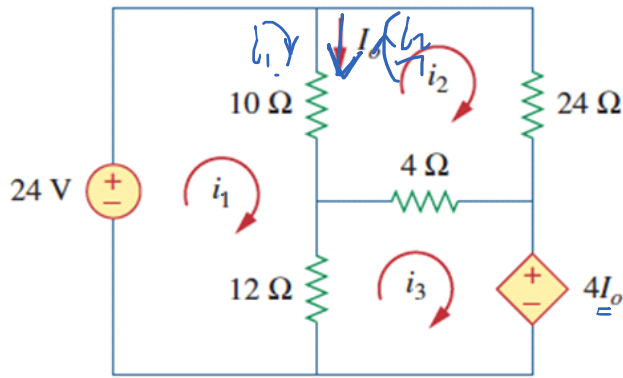

$$24 - 10(i_1 - i_2) - 12(i_1 - i_3) = 0$$

$$-24i_2 - 4(i_2 - i_3) - 10(i_2 - i_1) = 0$$

$$-4I_o - 12(i_3 - i_1) - 4(i_3 - i_2) = 0$$

$$-22i_1 + 10i_2 + 12i_3 = -24$$

$$10i_1 - 38i_2 + 4i_3 = 0$$

$$8i_1 + 8i_2 - 16i_3 = 0$$

$$\rightarrow \begin{bmatrix} -22 & 10 & 12 \\ 10 & -38 & 4 \\ 8 & 8 & -16 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} -24 \\ 0 \\ 0 \end{bmatrix}$$

$$A^{-1} A \cdot x = A^{-1} b$$

$$\underline{\underline{I}} \quad \boxed{x = A^{-1} b}$$

$$\rightarrow \begin{bmatrix} 11 & -5 & -6 \\ -5 & 19 & -2 \\ -1 & -1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix}$$