

Reading & Remarks

Charles K. Alexander and Matthew N. O. Sadiku, *Fundamentals of Electric Circuits 5th Edition*, McGrawHill, 2015.

- Chapter 4




Remarks:

- Quiz - 1 ✓
- Homework - 2 ✓

Linearity

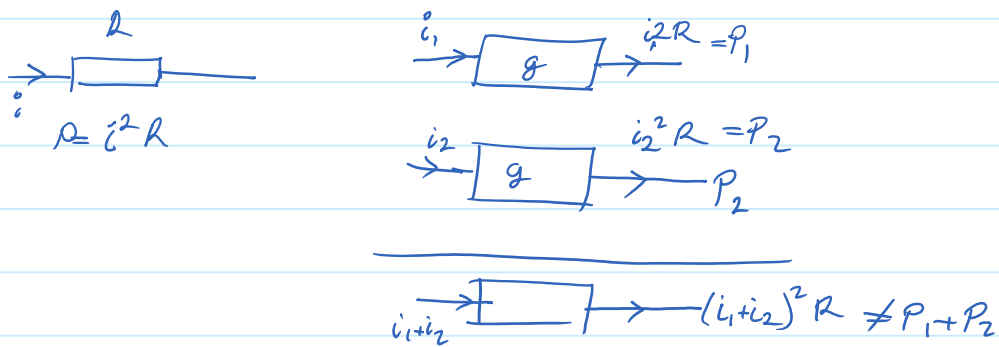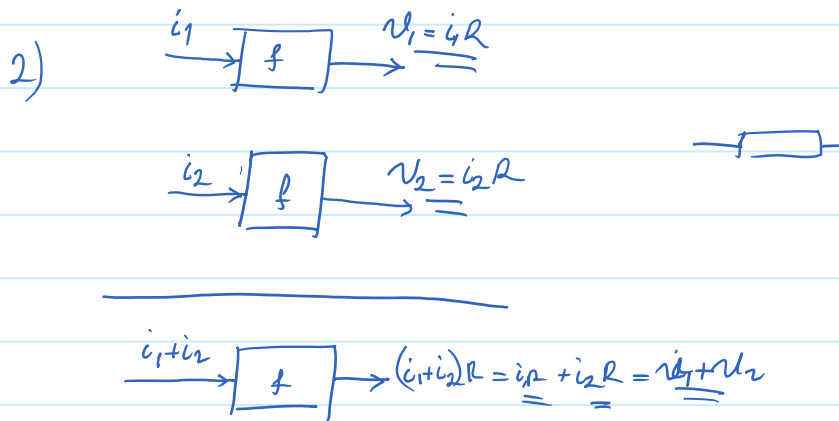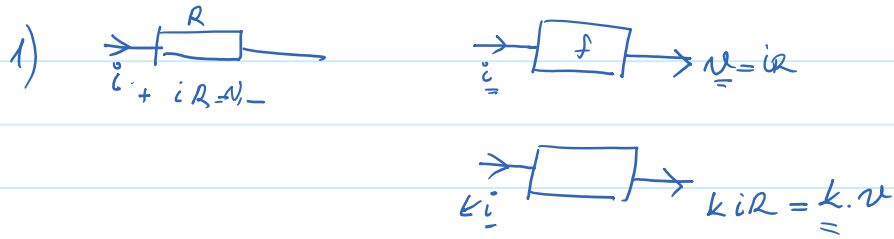
1. Homogeneity
2. Additivity

A resistor is linear. Relation between input current and output power is not linear.



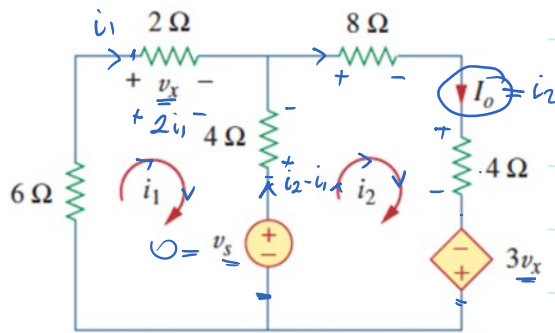Exercise

For the circuit below, find I_o when $v_s = 12V$ and $v_s = 24V$



$$-v_s - 6i_1 - 2i_1 - 4(i_1 - i_2) = 0$$

$$v_s - 4(i_2 - i_1) - 8i_2 - 4i_2 + 6i_1 = 0$$

$$5/ \quad -12i_1 + 4i_2 = 12 = v_s$$

$$6/ \quad 10i_1 - 16i_2 = -12 = -v_s$$

$$-60i_1 + 20i_2 = 60$$

$$60i_1 - 96i_2 = -72$$

$$-76i_2 = -12$$

$$i_2 = \frac{12}{-76} = \frac{6}{38} = \frac{3}{19}$$

$$v_s = 12V$$

$$v_s = 24$$

$$-76i_2 = -24$$


$$i_2 = \frac{12}{38} = \frac{6}{19}$$

$$v_s = 0 \rightarrow i_2 = 0$$

$$I_o = i_2 = \frac{12}{76} A$$


$$I_o = i_2 = \frac{24}{76} A$$

Superposition

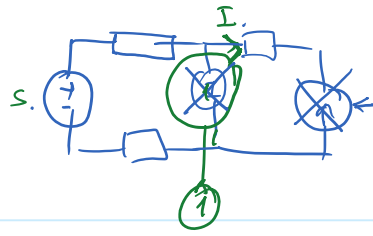


$$\underline{I_1} + \underline{I_2} + \underline{I_3} = \underline{I}$$

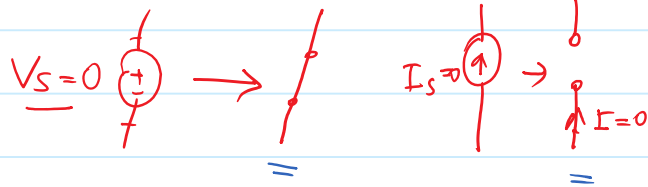- 1) Turn off all independent sources
-> replace voltage source with 0V (short circuit)
-> replace current source with 0A (open circuit)
Find the output (voltage or current) due to that active source
- 2) Repeat step 1 for all independent sources
- 3) Find the total contribution by adding algebraically all the contributions due to independent sources




Exercise

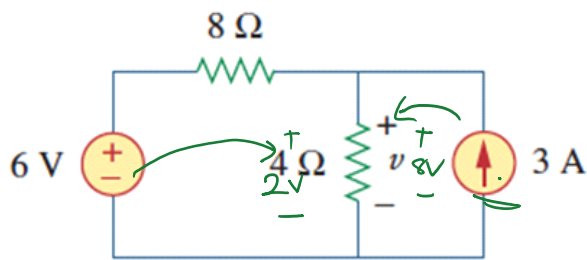


$$v = v_1 + v_2$$
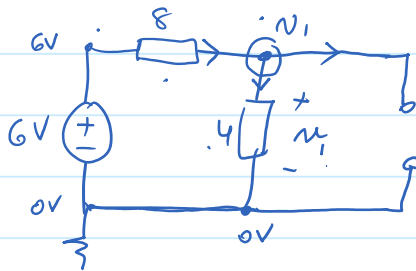
$$= 2 + 8 = \underline{\underline{10V}}$$


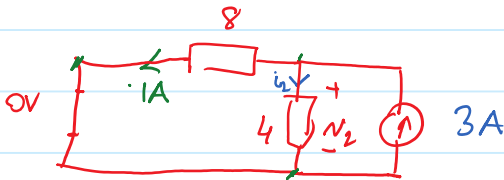
$$v_1 = \frac{6}{8+4} \cdot 4 = \underline{\underline{2V}}$$



$$i_2 = \frac{3}{8+4} \cdot 8 = 2A$$

$$v_2 = i_2 \cdot 4 = 2 \cdot 4 = \underline{\underline{8V}}$$

$$v = v_1 + v_2 = 2 + 8 = 10V$$

Exercise


15 --- 1234 ^{1/3}

1pts Q1* Last four digits of your student ID

Example: $\begin{matrix} & 1 & 2 & 3 & 4 \\ & \downarrow & \downarrow & \downarrow & \downarrow \\ 2 & 1 & 2 & 3 & 4 \\ \hline & 1+2+3 & 3+4+1 & & \end{matrix}$
 $A=6$ $B=8$
 Answer: 68

* if not correct no credits


1pts Q2.

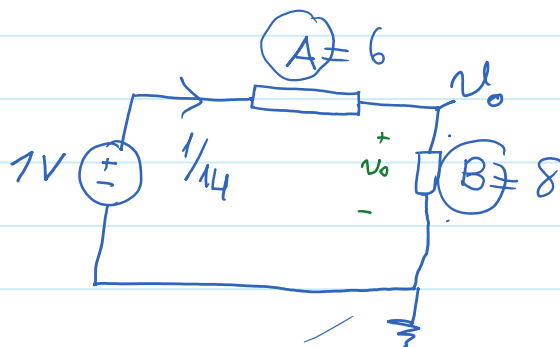

$$v_o = ?$$

$$8 \cdot \frac{1}{14} = \frac{8}{14}$$


1pts Q3.

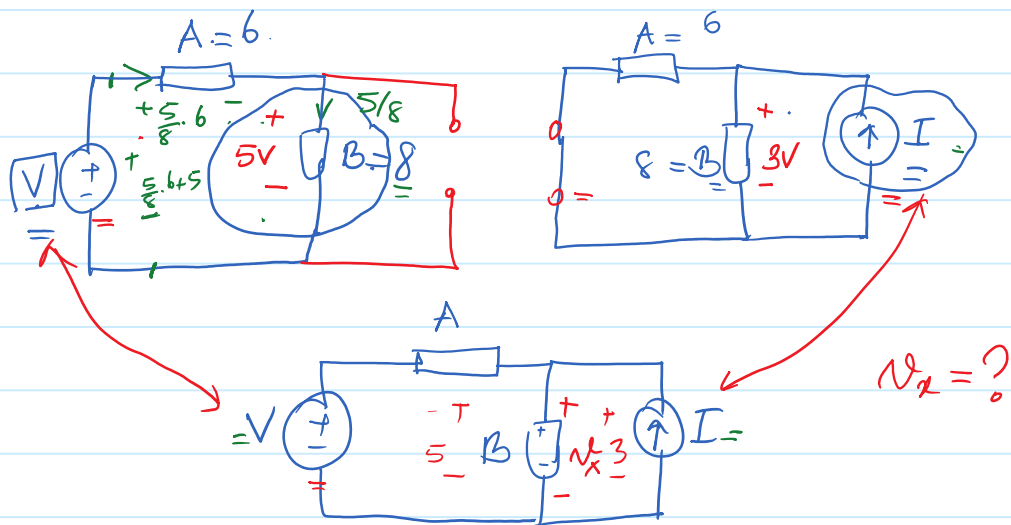

Hint: Use superposition.



$$v_x = 5 + 3 = 8$$

Exercise





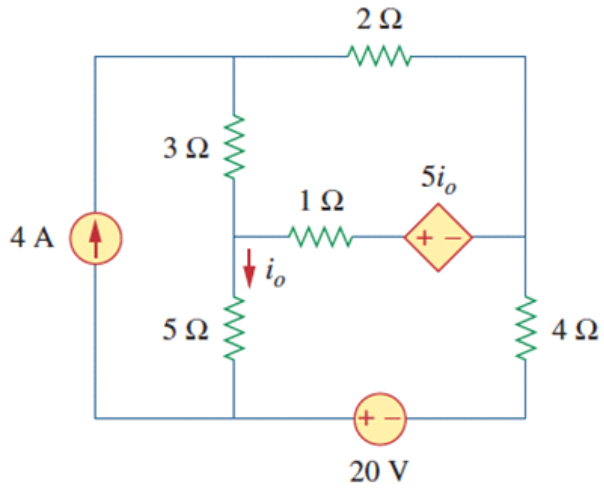


$$i_o = -\frac{8}{17} = -0.4706 \text{ A}$$

Source Transformation


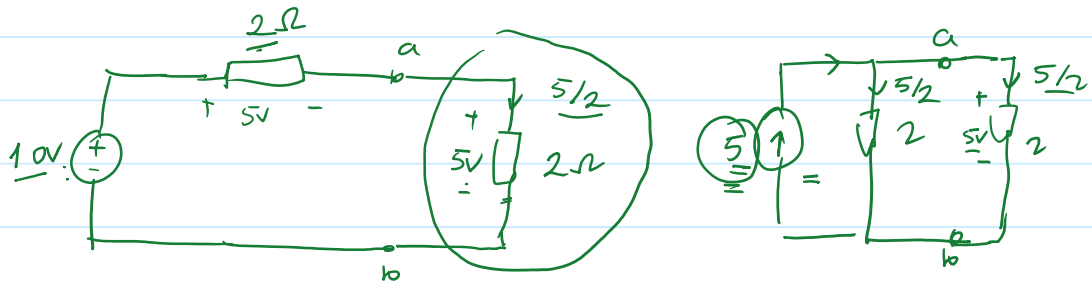
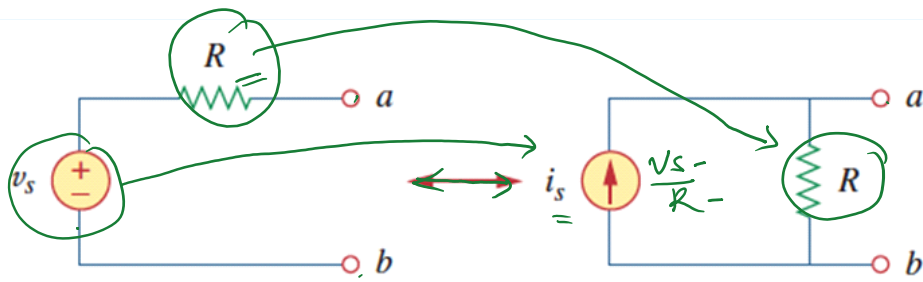


Exercise

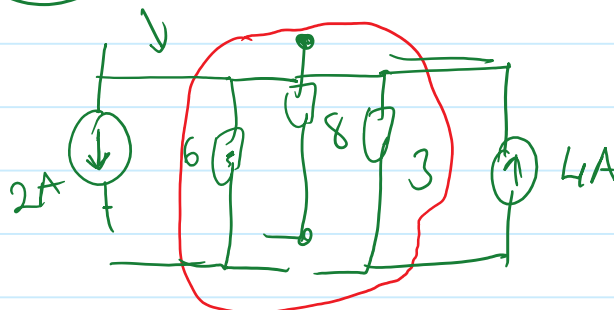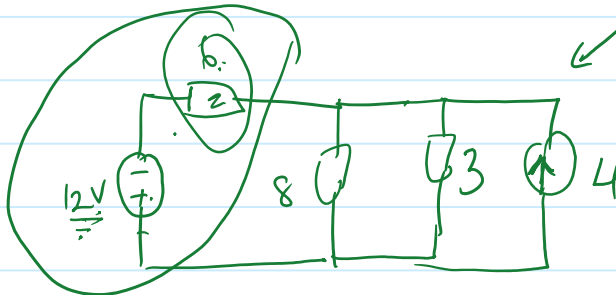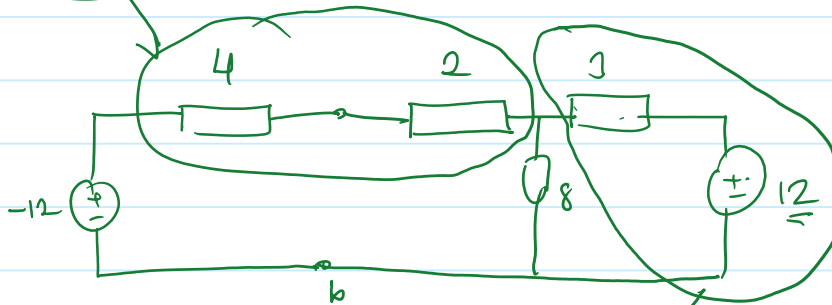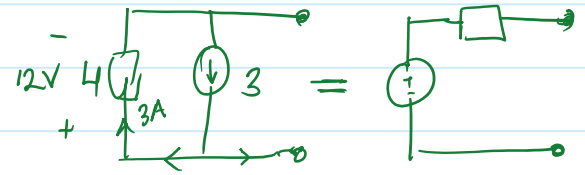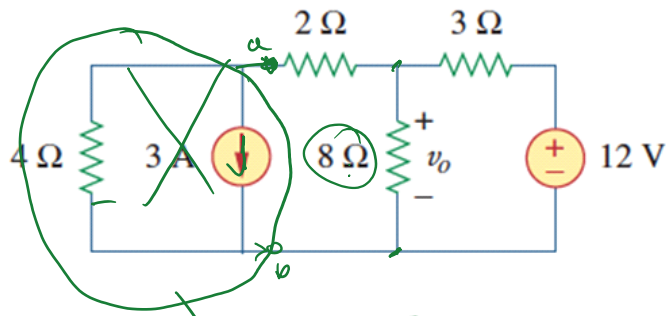



$$\frac{1}{R_{eq}} = \frac{1}{6} + \frac{1}{8} + \frac{1}{3}$$

$$R_{eq} = 1.6 \Omega$$

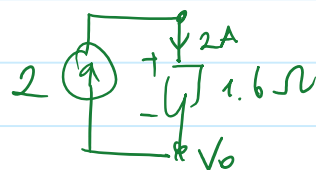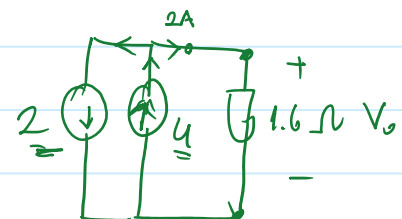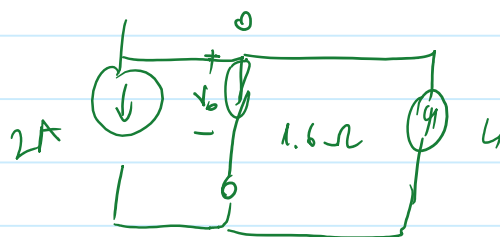

$$1.6 \cdot 2A = 3.2V$$

Exercise

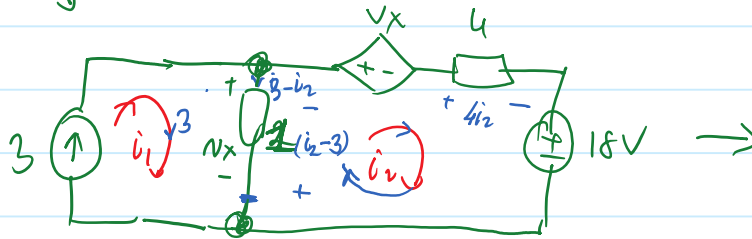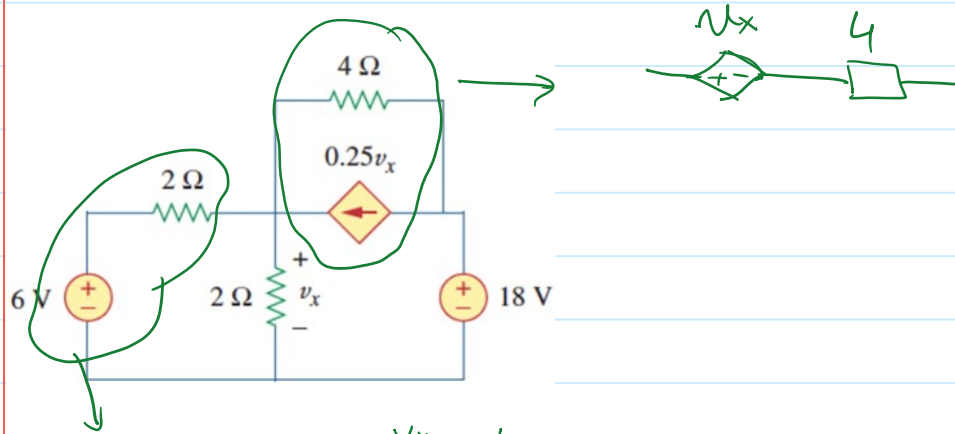

$$v_x = (3 - i_2) = 3 - \left(-\frac{9}{2}\right) = \frac{15}{2}$$




$$\underline{i_1 = 3A}$$

$$-(i_2 - 3)1 - v_x - 4i_2 - 18 = 0$$





$$-i_2 + 3 - 3 + i_2 - 4i_2 - 18 = 0$$

$$i_2 = -\frac{18}{4} = -\frac{9}{2}$$

Thevenin's Theorem

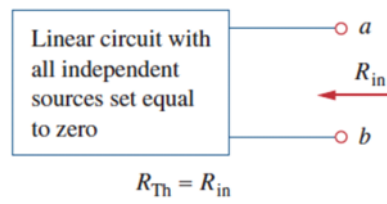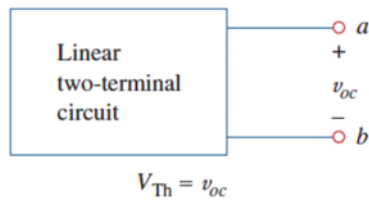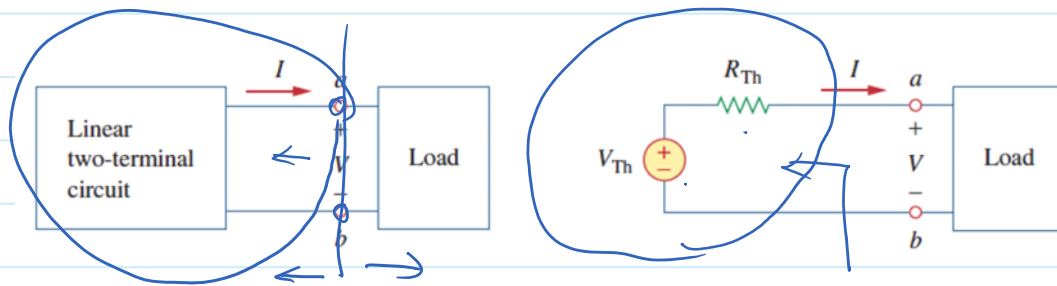




Exercise

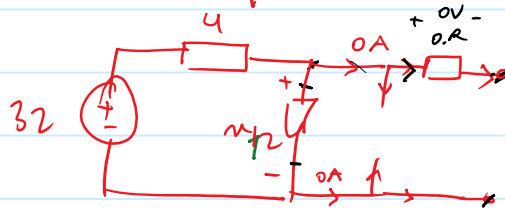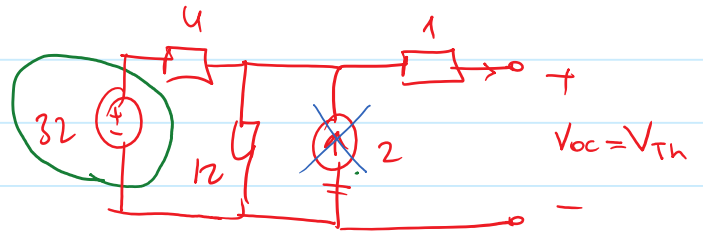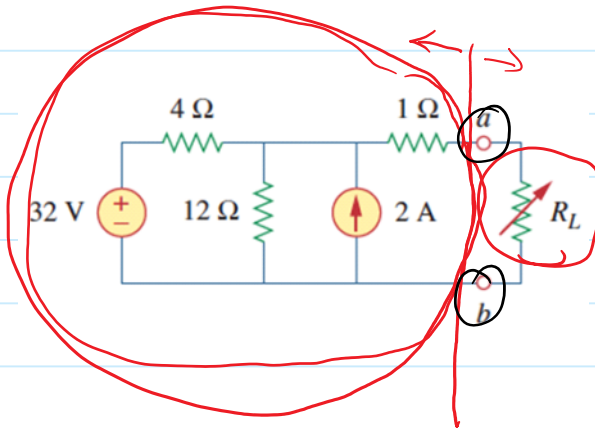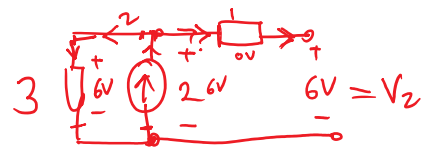

$$= \frac{32 \cdot 12}{4 + 12} = 24V$$



$$V_{oc} = 24V = V_T$$

$$R_{Th}$$

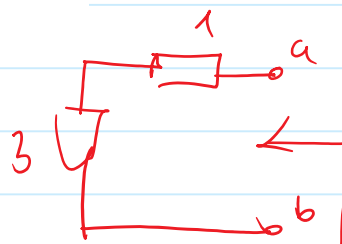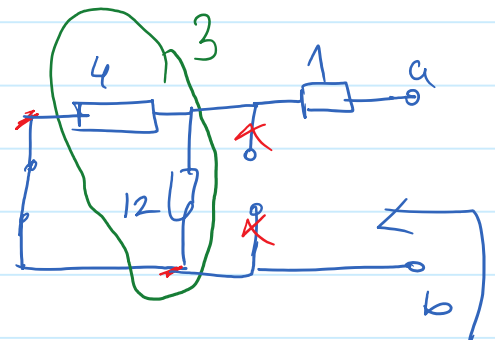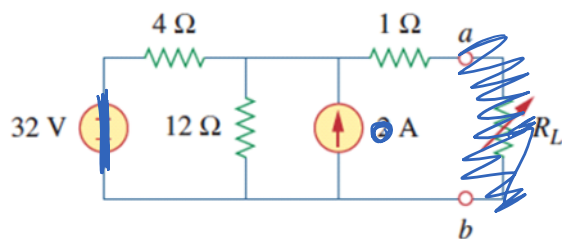

$$R_{Th} = R_{eq}$$

$$R_{eq} = 4\Omega = R_{Th}$$

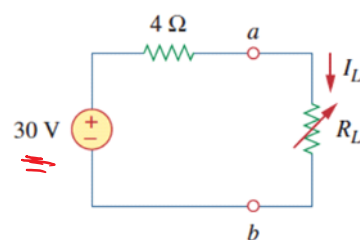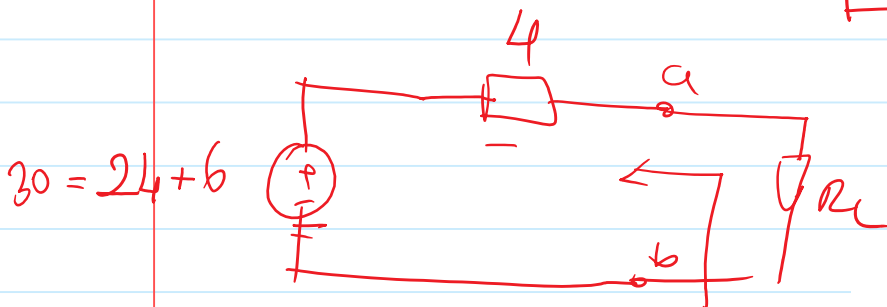

Norton's Theorem

