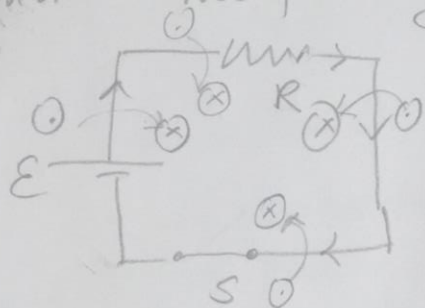


(1)

INDUCTANCE


Consider the following circuit:



When S is closed, a current starts to flow in the circuit. This current creates B (a magnetic field) in the loop, inwards \otimes . This B , which depends on I , increases as I increases & reaches its steady state value:

$I = E/R$. So, I starts from 0 and reaches E/R .

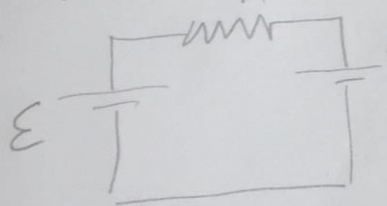During this transitory period, we have a time dependent B ($\frac{dB}{dt} > 0$) hence the flux through the loop increases. We know from Faraday's law that a time dependent flux induces an \mathcal{E} (EMF) in the opposite direction. So we have a \mathcal{E} in the opposite direction.



$$\mathcal{E}_{\text{induced}} = - \frac{d\Phi(t)}{dt} \quad \text{This is called BACK } \mathcal{E}.$$

This back \mathcal{E} exists only until $I = E/R$ and then it disappears. The effect of the \mathcal{E}_{ind} is to delay the increase in the current. This effect is called SELF-INDUCTION.

$$\text{We know that } \mathcal{E}_{\text{ind}} = - \frac{d\Phi(t)}{dt} = - \frac{d(\vec{B} \cdot \vec{A})}{dt}$$

$$B \propto I$$

$$\mathcal{E}_{\text{ind}} \propto \frac{dI}{dt}$$

$$\boxed{\mathcal{E}_L = - L \frac{dI}{dt}}$$


where L is a constant.

(2)

$$\mathcal{E}_L = -N \frac{d\phi}{dt} \quad (\text{for } N \text{ loops}) \quad N \frac{d\phi}{dt} = L \frac{dI}{dt}$$


$$L = \frac{N\phi}{I} = \text{inductance measured in "Henry" (H)}$$

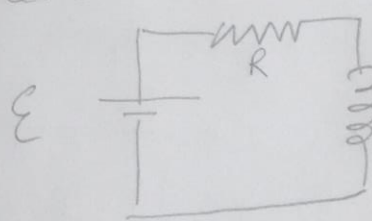Now if we introduce a circuit element like a solenoid in the circuit:



The increased flux will increase the inductance hence the self induced back \mathcal{E} .

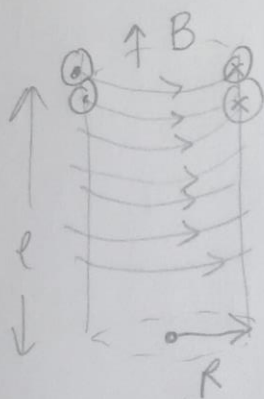Inductance (L) of course depends on the geometry. Let's calculate L for a solenoid of radius R .



$$B = \mu_0 n I \quad \text{or} \quad B = \mu_0 \frac{NI}{l} \quad n = \frac{N}{l}$$


where l is the length of the solenoid and N is the # of windings.

$$\phi = BA = \mu_0 \frac{NI}{l} A \quad \text{where } A = \pi R^2$$

$$L = \frac{N\phi}{I} = \boxed{\frac{\mu_0 N^2 A}{l}}$$

Inductance of a toroid (only half of the toroid is shown in the figure but we have a complete toroid.)

P. 72.

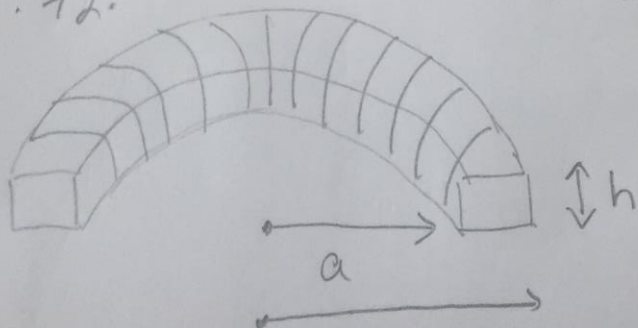

What is the inductance of the toroid?

(3)


We had determined the B for a toroid using Ampere's Law in chapter 30 (Please review) as,

$$B = \frac{\mu_0 N I}{2\pi r}$$

So B inside the toroid is not constant but depends

on r which is the distance from the center.

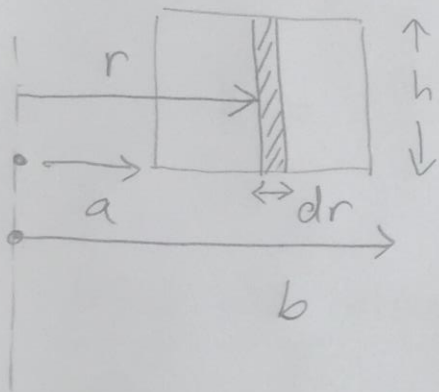We find the flux through one loop (rectangular)



$$d\phi = B dA = \frac{\mu_0 N I}{2\pi r} h dr$$

$$\phi = \int B dA = \int_a^b \frac{\mu_0 N I h}{2\pi r} dr$$


$$\phi = \frac{\mu_0 N I h}{2\pi} \int_a^b \frac{dr}{r} = \frac{\mu_0 N I h}{2\pi} \ln \frac{b}{a}$$

$$L = \frac{N\phi}{I}$$

where N is the total # of turns.

$$L = \frac{\mu_0 N^2 h}{2\pi} \ln \frac{b}{a}$$

Inductance of a coaxial wire:

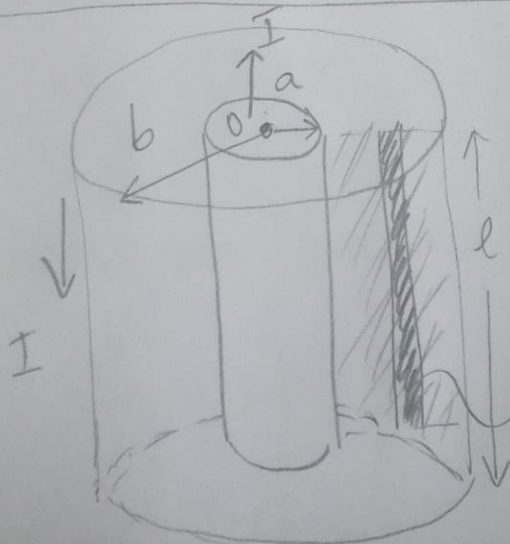

We had determined B in the coaxial region between the conductors (i.e. at $a < r < b$)

$$\text{as: } B = \frac{\mu_0 I}{2\pi r}$$

where r is the distance from O .

B is tangent to the ccw circle.

(4)


We consider the flux through the shaded area. But over that area B is not constant. So we consider $d\phi$ over the small shaded area dA .

$$d\phi = B dA = \frac{\mu_0 I}{2\pi r} \ell dr \quad \begin{array}{l} \text{(Notice that } B \text{ and} \\ dA \text{ are parallel)} \\ \text{(Both } \otimes \text{ in)} \end{array}$$

$$\phi = \int_a^b \frac{\mu_0 I}{2\pi r} \ell dr = \frac{\mu_0 I \ell}{2\pi} \ln \frac{b}{a}$$

$$L = \frac{N\phi}{I} = \frac{\mu_0 \ell}{2\pi} \ln \frac{b}{a} \quad \text{where } N=1$$

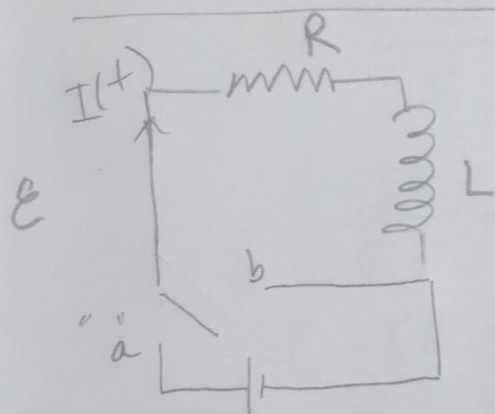Now we consider a circuit with an inductance.



S is brought to "a" at $t=0$. We write the loop equation in the transitory period before the current reaches its final value

$I = \mathcal{E}/R$. Also note that the inductor has no resistance like the connecting wires.

$$\mathcal{E} - I(t)R - L \frac{dI(t)}{dt} = 0$$

Now we want to solve for $I(t)$:

$$\frac{\mathcal{E}}{L} - I(t) \frac{R}{L} - \frac{dI(t)}{dt} = 0$$

(5)

$$\frac{\mathcal{E} - I(t)R}{L} = \frac{dI(t)}{dt}$$

$$\int_0^t \frac{dt}{L} = \int_0^I \frac{dI(t)}{\mathcal{E} - I(t)R}$$

$$\begin{aligned} \text{Let } \mathcal{E} - I(t)R &= u \\ -R dI(t) &= du \\ dI(t) &= -\frac{1}{R} du \end{aligned}$$

$$\int_0^t \frac{dt}{L} = -\frac{1}{R} \int_{\mathcal{E}} \frac{du}{u}$$

$$\frac{t}{L} = -\frac{1}{R} \ln \frac{\mathcal{E} - IR}{\mathcal{E}}$$


$$\ln \frac{\mathcal{E} - IR}{\mathcal{E}} = -\frac{R}{L} t$$

$$\frac{\mathcal{E} - IR}{\mathcal{E}} = e^{-\frac{R}{L} t}$$

$$\mathcal{E} - IR = \mathcal{E} e^{-\frac{R}{L} t}$$

$$I = \frac{\mathcal{E}}{R} (1 - e^{-\frac{R}{L} t})$$
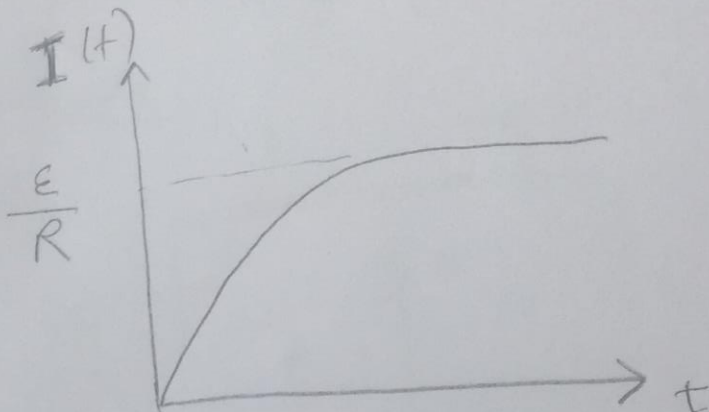
$$\tau = \frac{L}{R} \text{ (Time constant)}$$



when $t = 0$

$$e^{-\frac{R}{L} t} = 1$$

$$I = 0$$

when $t \rightarrow \infty$

$$e^{-\frac{R}{L} t} \rightarrow 0$$

$$I = \frac{\mathcal{E}}{R}$$

(6)

Let us now assume that after the current reaches its steady state value \mathcal{E}/R , we bring the switch S to "b". Now the loop equation:

$$-I(t)R - L \frac{dI(t)}{dt} = 0$$

$$\frac{I(t)R}{L} = - \frac{dI(t)}{dt}$$

$$\frac{dI(t)}{I(t)} = - (dt) \frac{R}{L}$$


$$\int_{\mathcal{E}/R}^{I(t)} \frac{dI(t)}{I(t)} = - \int_0^t \frac{R}{L} dt$$

$$\ln \frac{I(t)}{\mathcal{E}/R} = - \frac{R}{L} t$$

$$I(t) / \mathcal{E}/R = e^{-R/L t}$$


$$I(t) = \frac{\mathcal{E}}{R} e^{-(R/L) t}$$
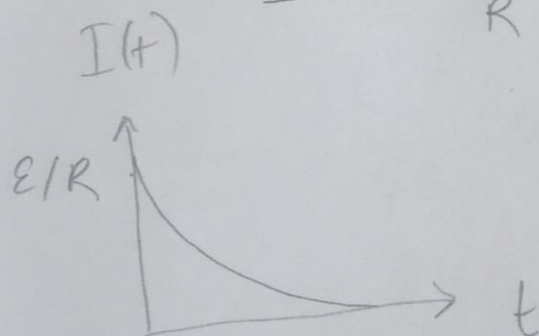
$$= \boxed{\frac{\mathcal{E}}{R} e^{-t/\tau}}$$



Example

P. 26.

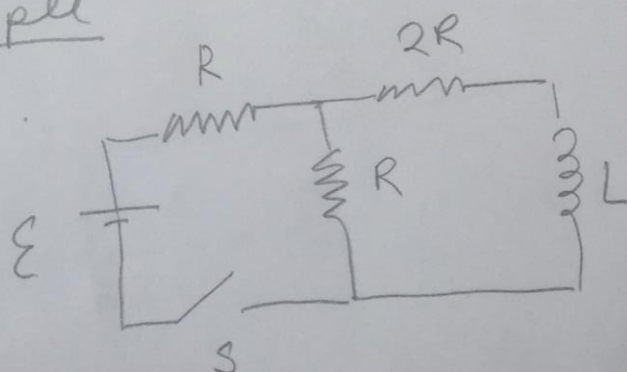


S is closed at

$t=0$. Find the

current in the

inductor L and

the current in the switch S as functions

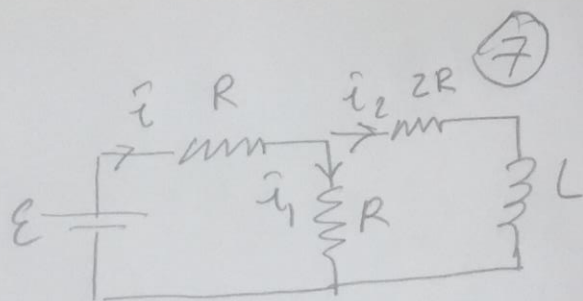

$$i = i_1 + i_2$$

$$E - iR - i_1R = 0$$

$$E - (i_1 + i_2)R - i_1R = 0$$

$$E - 2i_1R - i_2R = 0$$

$$\frac{E - i_2R}{2} = i_1$$

$$-i_2 2R - L \frac{di_2}{dt} + i_1 R = 0$$

$$-i_2 2R - L \frac{di_2}{dt} + \frac{E - i_2 R}{2} = 0$$

$$-4i_2 R - 2L \frac{di_2}{dt} + E - i_2 R = 0$$

$$E - 5i_2 R - 2L \frac{di_2}{dt} = 0$$

$$\frac{E - 5i_2 R}{2L} = \frac{di_2}{dt}$$

$$\int_0^t \frac{dt}{2L} = \int_{E - 5Ri_2(0)}^{E - 5Ri_2(t)} \frac{di_2}{E - 5Ri_2}$$

$$\text{Let } E - 5Ri_2 = u$$

$$-5R di_2 = du$$

$$di_2 = -\frac{du}{5R}$$

$$\frac{t}{2L} = -\frac{1}{5R} \int_E^{E - 5Ri_2(t)} \frac{du}{u}$$

$$\frac{t}{2L} = -\frac{1}{5R} \ln \frac{E - 5Ri_2(t)}{E}$$

$$-t 5R / 2L$$

$$\frac{E - 5Ri_2(t)}{E} = e$$

$$i_2(t) = \frac{E}{5R} (1 - e^{-\frac{5R}{2L} t})$$

$$\frac{E - i_2 R}{2R} = i_1$$

$$i_1 = \frac{E}{2R} - \frac{1}{2} i_2$$

$$i_1(t) = \frac{E}{2R} - \frac{E}{10R} (1 - e^{-5Rt/2L})$$

(8)


$$\hat{i} = \hat{i}_1 + \hat{i}_2 = \frac{\mathcal{E}}{2R} - \frac{\mathcal{E}}{10R} (1 - e^{-5Rt/2L}) + \frac{\mathcal{E}}{5R} (1 - e^{-5Rt/2L})$$

$$\hat{i} = \frac{\mathcal{E}}{2R} + (1 - e^{-5Rt/2L}) \left(\frac{\mathcal{E}}{5R} - \frac{\mathcal{E}}{10R} \right)$$

$$\hat{i} = \frac{\mathcal{E}}{2R} + \frac{\mathcal{E}}{10R} (1 - e^{-t/\tau}) \quad \text{where } \tau = \frac{2L}{5R}$$

Energy Stored in an Inductor

In the circuit, we write the loop eqn:

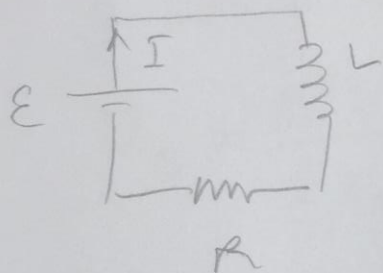

$$\mathcal{E} - L \frac{dI}{dt} - IR = 0$$

Multiply by I

$$\mathcal{E}I - LI \frac{dI}{dt} - I^2 R = 0 \Rightarrow \text{Power eqn.}$$

The power in the inductor must be:

$$LI \frac{dI}{dt} = \frac{dU_B}{dt}$$


\Rightarrow the rate at which energy is stored in the inductor.

$$\int_0^{U_B} du = \int_0^I LI dI$$

$$U_B = L \frac{I^2}{2}$$

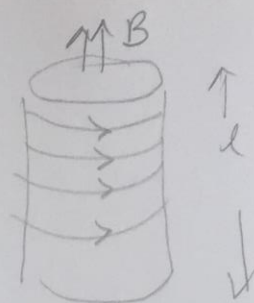(9)

Consider a solenoid of length l and N windings



$$B = \mu_0 n I = \mu_0 \frac{N I}{l} \quad \phi = \mu_0 \frac{N I A}{l}$$

$$L = \frac{N \phi}{I} = \frac{\mu_0 N^2 A}{l} = \frac{\mu_0 N^2 A l}{l^2} = \mu_0 n^2 V$$

where $\frac{N}{l} = n$ and $Al = \text{volume}$.

$$U_B = \frac{L I^2}{2} = \left[\frac{\mu_0 n^2 V I^2}{2} \right] \quad \sigma = \frac{\mu_0^2 n^2 I^2 V}{2 \mu_0}$$

If we write this in terms of B

$$U_B = \frac{B^2 V}{2 \mu_0}$$

and divide by V : energy per volume:

$$u_B = \frac{B^2}{2 \mu_0}$$